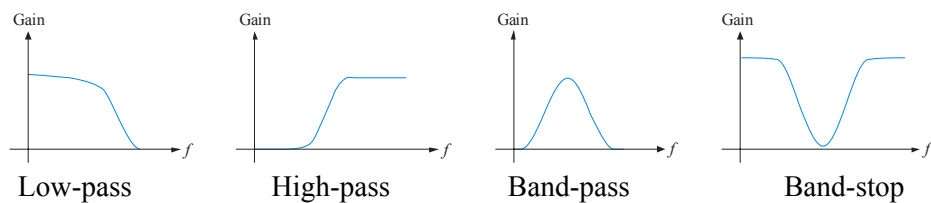


# Chapter 15: Active Filters

## 15.1: Basic filter Responses

- A filter is a circuit that passes certain frequencies and rejects or attenuates all others.
- The **passband** is the range of frequencies allowed to pass through the filter.
- The **critical frequency**,  $f_c$ , defines the end (or ends) of the passband and is normally specified at the point where the response drops -3dB (70.7%) from the passband response.
- Basic filter responses are:



## 15.1: Basic filter Responses



### Low-Pass Filter Response

■ The **low-pass filter** allows frequencies below the critical frequency to pass (from dc to  $f_c$ ) and rejects other. The simplest low-pass filter is a passive  $RC$  circuit with the output taken across  $C$ .

■ → The bandwidth of an ideal low-pass filter is  $BW = f_c$

The critical frequency of a low-pass  $RC$  filter occurs when  $X_C = R$  where

$$f_c = \frac{1}{2\pi RC}$$

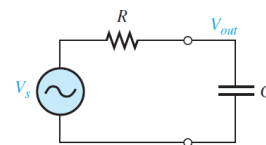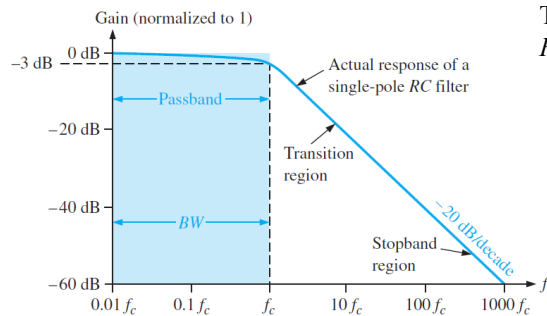

Ideal response (shaded area): ideal low-pass filter; no response for frequencies above  $f_c$

Actual response (curved line): the gain drops rapidly after  $f_c$  with a rate decided by number of poles (number of  $RC$  circuits contained in the filter)


## 15.1: Basic filter Responses

### Low-Pass Filter Response

■ The -20dB roll-off rate is not a particularly good filter characteristic (far from ideal filter) because too much of the unwanted frequencies (beyond the passband) are allowed through the filter

■ In order to produce a more effective filter that has a steeper transition region, it is necessary to add additional poles ( $RC$  circuits) combined with op-amps that have frequency-selective feedback circuits → filters can be designed with roll-off rates of -40dB, -60dB or more dB/decade as shown

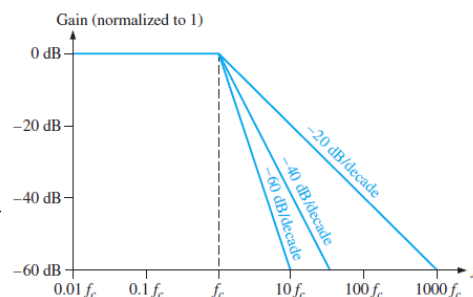
■ Filters that include one or more op-amps in the design are called **active filters**. These filters can optimize the roll-off rate or other attribute (such as phase response) with a particular filter design.



## 15.1: Basic filter Responses
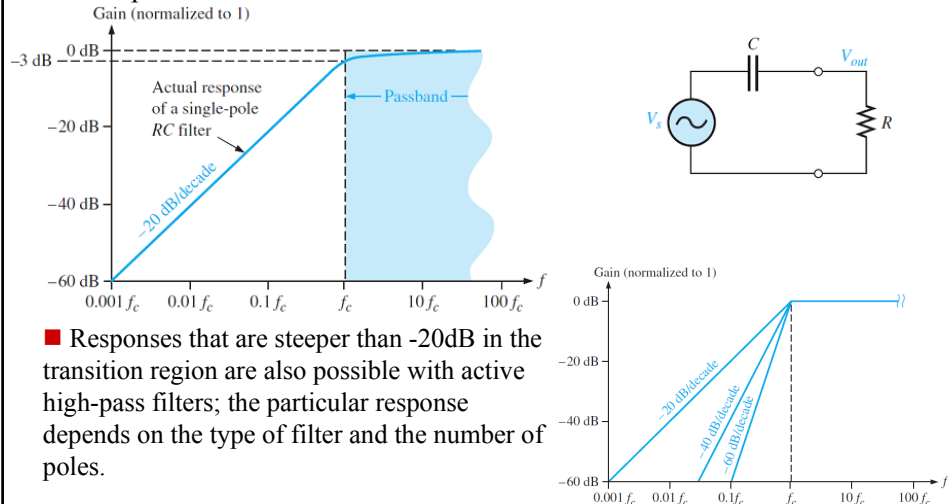
### High-Pass Filter Response

■ The high-pass filter passes all frequencies above a critical frequency and rejects all others. The simplest high-pass filter is a passive RC circuit with the output taken across R.



■ Responses that are steeper than -20dB in the transition region are also possible with active high-pass filters; the particular response depends on the type of filter and the number of poles.

## 15.1: Basic filter Responses

### Band-Pass Filter Response

■ A **band-pass filter** passes all frequencies between two critical frequencies. The **bandwidth** is defined as the difference between the two critical frequencies. The band-pass filter can be obtained by joining the high-pass filter with low-pass filter or by RLC circuit (not described in this chapter)

■ The bandwidth is  $BW = f_{c2} - f_{c1}$


■ The center frequency  $f_0$  about which the bandpass is centered can be calculated from  $f_0 = \sqrt{f_{c1}f_{c2}}$

■ The **quality factor (Q)** of a band-pass filter is the ratio of the center frequency to the bandwidth.  $Q = \frac{f_0}{BW}$

The lower the Q the better the band selection

■ If  $Q > 10 \rightarrow$  narrow band-pass filter If  $Q < 10 \rightarrow$  wide bandpass filter

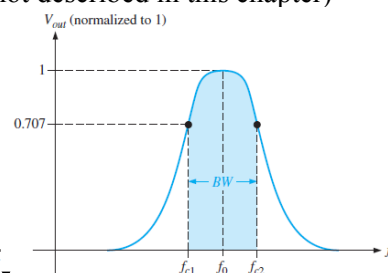■ The quality factor (Q) can also be expressed in terms of the damping factor (DF) of the filter as  $Q = \frac{1}{DF}$



## 15.1: Basic filter Responses

### Band-Stop Filter Response

■ A **band-stop filter** rejects frequencies between two critical frequencies; the bandwidth is measured between the critical frequencies. The band-pass filter can be obtained by joining the low-pass filter with high-pass filter or by RLC circuit (not described in this chapter)

■ The bandwidth is


$$BW = f_{c2} - f_{c1}$$

■ The center frequency  $f_0$  is

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

■ quality factor ( $Q$ )


$$Q = \frac{f_0}{BW}$$

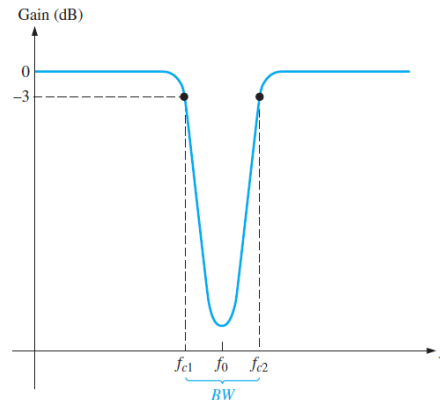
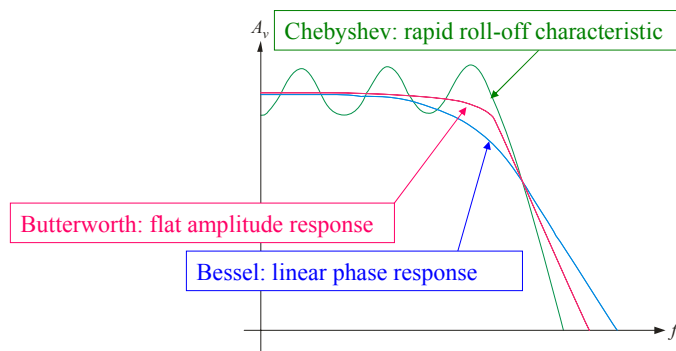
## 15.2: Filter Response Characteristics

■ **Active filters:** include one or more op-amps in the design. These filters can provide much better responses than the passive filters illustrated before. Active filter designs optimize various parameters such as amplitude response, roll-off rate, or phase response.

■ Each type of filter response (low-pass, high-pass, band-pass, or band-stop) can be tailored by circuit component values to have either a Butterworth, Chebyshev, or Bessel characteristic.




## 15.2: Filter Response Characteristics

### The Damping Factor

- The damping factor primarily determines if the filter will have a Butterworth, Chebyshev, or Bessel response.
- The damping factor in the shown general diagram of active filter is determined by the feedback resistors  $R_1$  and  $R_2$  and is defined by:

$$DF = 2 - \frac{R_1}{R_2}$$

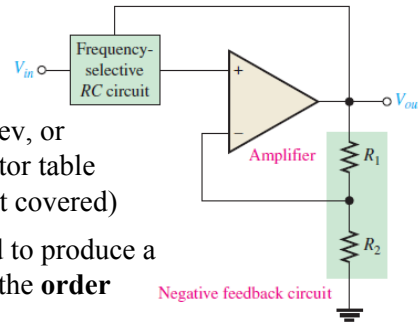

- Every filter type (Butterworth, Chebyshev, or Bessel response) has its own damping factor table derived using advanced mathematics (not covered)
- The value of the damping factor required to produce a desired response characteristic depends on the **order** (number of poles) of the filter.
- A **pole** is simply a circuit with one resistor and one capacitor. The more poles a filter has, the faster its roll-off rate is.

## 15.2: Filter Response Characteristics

### The Damping Factor

- Because of its maximally flat response, the Butterworth characteristic is the most widely used → we will limit our coverage to the Butterworth response
- Parameters for Butterworth filters up to four poles are given in the following table. (See text for larger order filters).

Table for Butterworth filter values

Order	Roll-off dB/decade	1 <sup>st</sup> stage			2 <sup>nd</sup> stage		
		Poles	DF	$R_1/R_2$	Poles	DF	$R_1/R_2$
1	-20	1	Optional				
2	-40	2	1.414	0.586			
3	-60	2	1.00	1.00	1	1.00	1.00
4	-80	2	1.848	0.152	2	0.765	1.235


For example, To achieve a second-order Butterworth response → damping factor must be 1.414. →  $\frac{R_1}{R_2} = 2 - DF = 2 - 1.414 = 0.586$

→ The gain  $A_{cl(NI)} = \frac{R_1}{R_2} + 1 = 0.586 + 1 = 1.586$  which is 1 more than the resistor ratio

## 15.2: Filter Response Characteristics
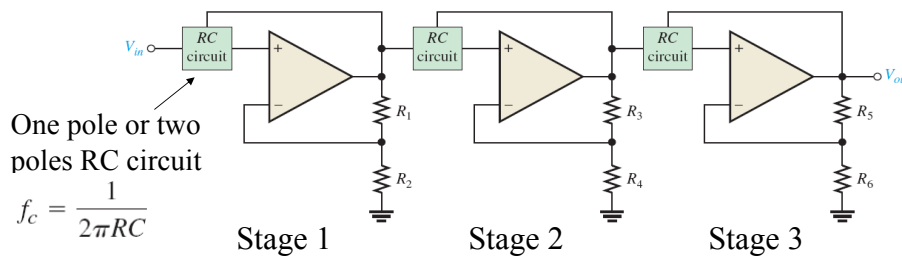
### Critical Frequency and Roll-Off Rate

- the **order** number is the number of poles ( $RC$  circuits) that must be included in the circuit of the active filter
- The number of poles determines the roll-off rate of the filter. A Butterworth response produces  $-20$  dB/decade/pole  $\rightarrow$  a first-order (one-pole) filter has a roll-off of  $-20$  dB/decade; a second-order (two-pole) filter has a roll-off rate of  $-40$  dB/decade; a third-order (three-pole) filter has a roll-off  $-60$  dB/decade and so on.
- Generally, to obtain a filter with three poles or more, **one-pole** or **two-pole** filters are cascaded in stages as shown.




## 15.3: Active Low-Pass Filters

- Filters that use op-amps as the active element provide several advantages over passive filters ( $R$ ,  $L$ , and  $C$  elements only). The op-amp provides gain, so the signal is not attenuated as it passes through the filter.
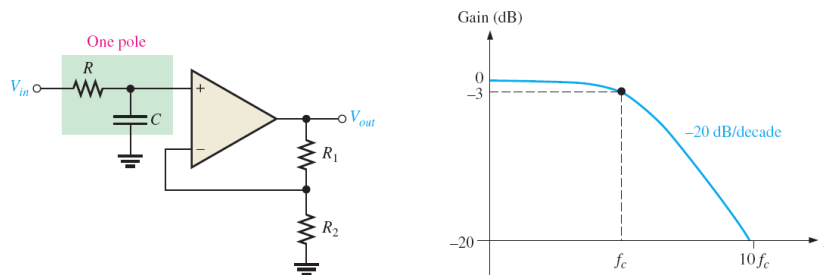
### A Single-Pole Low-Pass Filter

- active filter with a single low-pass  $RC$  frequency-selective circuit that provides a roll-off of  $-20$  dB/decade



- The critical frequency  $f_c = \frac{1}{2\pi RC}$
- The closed-loop voltage gain  $A_{cl(NI)} = \frac{R_1}{R_2} + 1$

### 15.3: Active Low-Pass Filters

#### The Sallen-Key Low-Pass Filter (Double-Pole Low-Pass Filter)

■ The Sallen-Key is one of the most common configurations for a second-order (two-pole) filter.

■ It is an active filter with a two low-pass  $RC$  circuits that provides a roll-off of -40 dB/decade


■ The critical frequency

$$f_c = \frac{1}{2\pi \sqrt{R_A R_B C_A C_B}}$$

If we choose  $R_A = R_B = R$  and  $C_A = C_B = C$ .

→ critical frequency simplifies to  $f_c = \frac{1}{2\pi RC}$

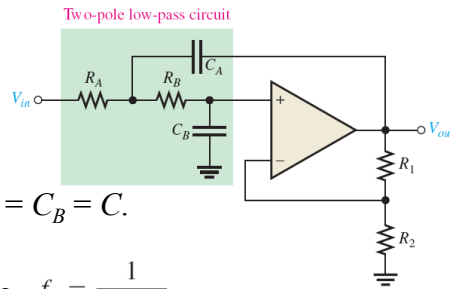■ The closed-loop voltage gain  $A_{cl(NI)} = \frac{R_1}{R_2} + 1$




### 15.3: Active Low-Pass Filters

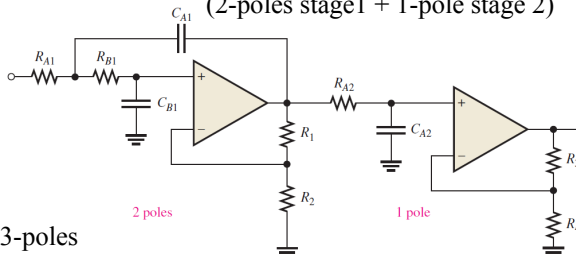
#### Cascaded Low-Pass Filters

■ Third-order or higher low-pass response (-60 dB/decade or lower) can be done by cascading a single pole and/or two-pole low-pass filter

Third order configuration; 3-poles (2-poles stage1 + 1-pole stage 2)




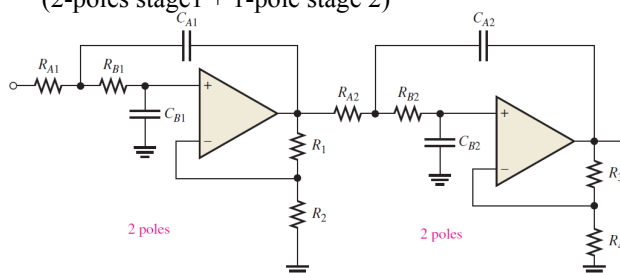Fourth order configuration; 3-poles (2-poles stage1 + 1-pole stage 2)


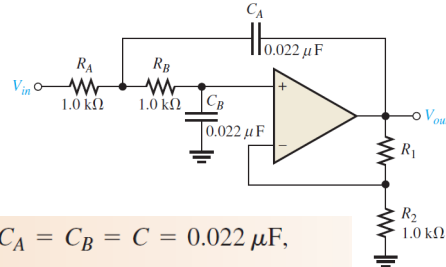
### 15.3: Active Low-Pass Filters: Example

■ Determine the critical frequency of the Sallen-Key low-pass filter in Figure, and set the value of  $R_1$  for an approximate Butterworth response.



Since  $R_A = R_B = R = 1.0 \text{ k}\Omega$  and  $C_A = C_B = C = 0.022 \text{ }\mu\text{F}$ ,

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.0 \text{ k}\Omega)(0.022 \text{ }\mu\text{F})} = 7.23 \text{ kHz}$$

For a Butterworth response,  $R_1/R_2 = 0.586$ .

$$R_1 = 0.586R_2 = 0.586(1.0 \text{ k}\Omega) = 586 \text{ }\Omega$$

### 15.3: Active Low-Pass Filters: Example

For the four-pole filter in Figure before in cascaded filters determine the capacitance values required to produce a critical frequency of 2680 Hz if all the resistors in the RC low-pass circuits are 1.8 kΩ. Also select values for the feedback resistors to get a Butterworth response

Both stages must have the same  $f_c$ . Assuming equal-value capacitors,

$$f_c = \frac{1}{2\pi RC}$$

$$C = \frac{1}{2\pi R f_c} = \frac{1}{2\pi(1.8 \text{ k}\Omega)(2680 \text{ Hz})} = 0.033 \text{ }\mu\text{F}$$

$$C_{A1} = C_{B1} = C_{A2} = C_{B2} = 0.033 \text{ }\mu\text{F}$$

Also select  $R_2 = R_4 = 1.8 \text{ k}\Omega$  for simplicity. Refer to Table 15-1. For a Butterworth response in the first stage,  $DF = 1.848$  and  $R_1/R_2 = 0.152$ . Therefore,

$$R_1 = 0.152R_2 = 0.152(1800 \text{ }\Omega) = 274 \text{ }\Omega$$

Choose  $R_1 = 270 \text{ }\Omega$ .

In the second stage,  $DF = 0.765$  and  $R_3/R_4 = 1.235$ . Therefore,

$$R_3 = 1.235R_4 = 1.235(1800 \text{ }\Omega) = 2.22 \text{ k}\Omega$$


Choose  $R_3 = 2.2 \text{ k}\Omega$ .



## 15.4: Active High-Pass Filters
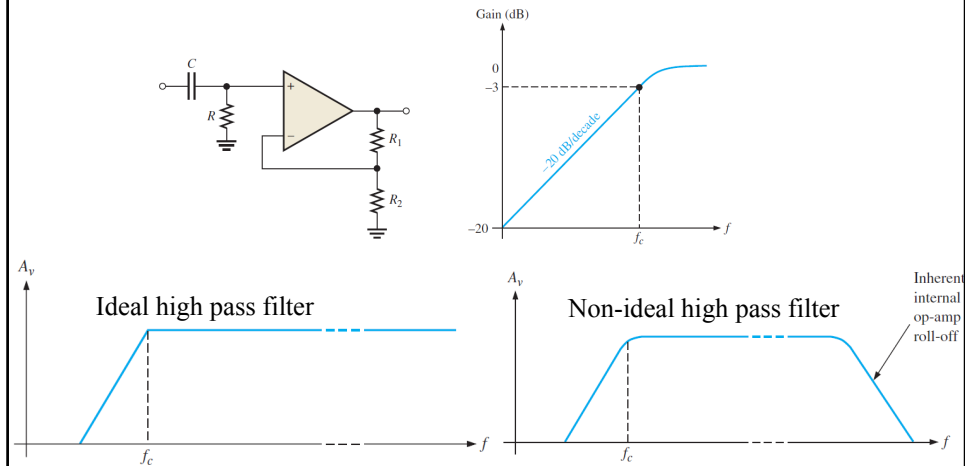
### A Single-Pole Filter


■ A high-pass active filter with a roll-off -20 dB/decade is shown in Figure. Notice that the input circuit is a single high-pass  $RC$  circuit. The negative feedback circuit is the same as for the low-pass filters previously discussed. The high-pass response curve is shown in Figure 15–13(b).




## 15.4: Active High-Pass Filters
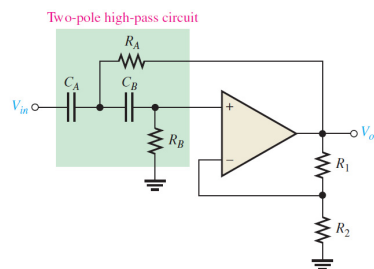
### The Sallen-Key High-Pass Filter (Double-Pole High-Pass Filter)

■ It is an active filter with a two high-pass  $RC$  circuits that provides a roll-off of -40 dB/decade



### Cascading High-Pass Filters

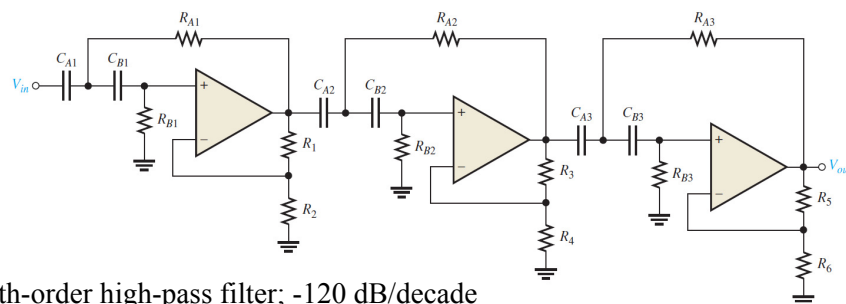



Sixth-order high-pass filter; -120 dB/decade

## 15.5: Active Band-Pass Filters

■ As mentioned, band-pass filters pass all frequencies bounded by a lower-frequency limit and an upper-frequency limit and reject all others lying outside this specified band
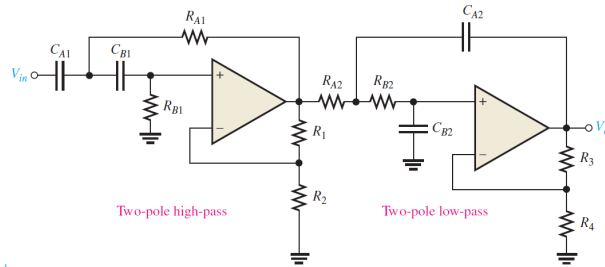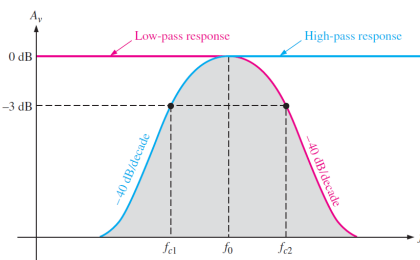
### Cascaded High-Pass and Low-Pass Filters

■ implementing a band-pass filter can be done by cascading arrangement of a high-pass filter and a low-pass filter, as shown in Figure



$$f_{c1} = \frac{1}{2\pi\sqrt{R_{A1}R_{B1}C_{A1}C_{B1}}}$$

$$f_{c2} = \frac{1}{2\pi\sqrt{R_{A2}R_{B2}C_{A2}C_{B2}}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$