

TEST #1

Date: March 22, 2021

1 . The average load voltage produced by a power supply is measured using a(n) _____.

- ☐ Oscilloscope
 - ☐ DC voltmeter
 - ☐ AC voltmeter
-

2 . The use of a capacitive filter causes the PIV of a _____ rectifier to increase.

- ☐ Half-wave
 - ☐ Full-wave
 - ☐ Bridge
-

3 . Power rectifiers have extremely high _____ ratings.

- ☐ Reverse voltage
 - ☐ Efficiency
 - ☐ Average forward current
-

4 . The average load voltage produced by a filtered full-wave rectifier with a $36\text{-}V_{ac}$ transformer is approximately _____. [\[Hint\]](#)

- ☐ 25.5 V
 - ☐ 50.9 V
 - ☐ 16.2 V
-

5 . The average load voltage produced by a full-wave rectifier with an $18\text{-}V_{ac}$ transformer is approximately equal to the average load voltage produced by a half-wave rectifier with a(n) _____ transformer. [\[Hint\]](#)

- ☐ $18\text{ }V_{ac}$
- ☐ $36\text{ }V_{ac}$
- ☐ $9\text{ }V_{ac}$

6 . The output from a rectifier is normally connected to a _____.

- ☐ Filter
 - ☐ Voltage regulator
 - ☐ Transformer
-

7 . A _____ converts ac to a single-polarity output by converting the positive alternations to negative alternations, or vice versa. [\[Hint\]](#)

- ☐ Half-wave rectifier
 - ☐ Voltage regulator
 - ☐ Full-wave rectifier
-

8 . _____ is a measure of the ability of a power supply to maintain a constant output voltage despite variations in load current demand. [\[Hint\]](#)

- ☐ Line regulation
 - ☐ Load regulation
 - ☐ Current regulation
-

9 . _____ provide the best overall protection from power supply surge currents and excessive output ripple. [\[Hint\]](#)

- ☐ Capacitive filters
 - ☐ RC filters
 - ☐ LC filters
-

10 . As load resistance varies (within specified limits), a zener regulator maintains a constant _____. [\[Hint\]](#)

- ☐ Load voltage
- ☐ Load current
- ☐ Line current

11 When a pn junction's depletion layer is narrowed and the device acts as a nearly perfect conductor it is

- (a) forward-biased
- (b) reverse-biased
- (c) unbiased
- (d) none of the above

12. The maximum reverse bias potential that can be applied to a zener diode before it enters the zener region is called the

- (a) threshold voltage
- (b) PIV
- (c) barrier voltage
- (d) depletion voltage
- (e) none of the above

13. When a pn junction is reverse-biased, the depletion layer is _____ and the device acts as a near-perfect _____.

- (a) narrowed, conductor
- (b) narrowed, insulator
- (c) widened, conductor
- (d) widened, insulator
- (e) none of the above

14. The electrode with n-type material of a diode is called the

- (a) anode
- (b) cathode
- (c) depletion region
- (d) zender region
- (e) none of the above

15. Determine the static resistance of a diode whose $V(D) = 0.8 \text{ V}$ and $I(D) = 4 \text{ mA}$.

- (a) 4 Ohms
- (b) 80 Ohms
- (c) 200 Ohms
- (d) 1000 Ohms
- (e) none of the above

16. The steeper the slope of the diode characteristic curve:

- (a) the greater the ac resistance
- (b) the greater diode's capacitance
- (c) the less the diode's ac resistance
- (d) the less diode's breakdown voltage
- (e) all of the above

17. The model of the diode represents the device as

- (a) an ideal diode
- (b) in series with a battery
- (c) in series with a battery and a resistor
- (d) an ideal diode and a switch
- (e) a switch and a battery

18. When tested with an ohmmeter, a diode should have a relatively high resistance for _____ condition.

- (a) the reverse-biased
- (b) the forward-biased
- (c) both reverse- and forward-bias
- (d) none-biased
- (e) none of the above

19. The point of intersection between the characteristic curve of the diode and the resistor's loadline is known as:

- (a) the point of operation
- (b) the Q-point
- (c) the quiescent point
- (d) all of the above

20. Given a series silicon diode circuit with the resistor $R = 2\text{K ohms}$ and an applied voltage of 10 volts, what is $I(DQ)$?

- (a) 4.65 mA
- (b) 1.0 mA
- (c) 10 mA
- (d) 0.5 mA