

Test #2

Transistor biasing

1. The three terminals of a bipolar junction transistor are called

- A. input, output, ground
- B. base, emitter, collector
- C. p,n,p
- D. n,p,n

2. In a pnp transistor, the p-region are

- A. base and emitter
- B. base and collector
- C. emitter and collector

3. For operation as an amplifier, the base of a npn transistor must be

- A. 0 V
- B. negative with respect to the emitter
- C. positive with respect to the collector
- D. positive with respect to the emitter

4. The emitter current is always

- A. greater than the base current
- B. less than the collector current
- C. greater than the collector current
- A. answer a and c

5. The β_{DC} of a transistor is its

- A. internal resistance
- B. power gain
- C. voltage gain
- D. current gain

6. If I_C is 50 times larger than I_B , then β_{DC} is
- A. 500 B. 0.02
C. 100 D. 50
7. The approximate voltage across the forward-biased base emitter junction of a silicon BJT is
- A. 0.3 V B. 0.7 V
C. 0 V D. V_{BB}
8. The bias condition for a transistor to be used as linear amplifier is called
- A. reverse-reverse B. forward-reverse
C. collector bias D. forward-forward
9. If the output of a transistor amplifier is 5 V rms and the input is 100 mV rms, the voltage gain is
- A. 50 B. 500
C. 5 D. 100
10. When operated in cutoff and saturation, the transistor acts like
- A. a switch B. a linear amplifier
C. a variable capacitor D. a variable resistor

11. In cutoff, V_{CE} is
- A. 0 V
 - B. minimum
 - C. maximum
 - D. equal to V_{CC}
 - E. answer a and b
 - F. answer c and d

12. In saturation, V_{CE} is
- A. 0.7 V
 - B. equal to V_{CC}
 - C. maximum
 - D. minimum

13. To saturate a BJT,
- A. $I_B > I_{C(sat)}/\beta_{DC}$
 - B. $I_B = I_{C(sat)}$
 - C. V_{CC} must be at least 10 V
 - D. the emitter must be grounded

14. Once in saturation, a further increase in base current will
- A. not affected the collector current
 - B. cause the collector current to decrease
 - C. cause the collector current to increase
 - D. turn the transistor off

15. If the base-emitter junction is open, the collector voltage is
- A. floating
 - B. V_{CC}
 - C. 0 V
 - D. 0.2 V

16. The maximum value of collector current in a biased transistor is
- A. $\beta_{DC} I_B$ B. $I_{C(sat)}$
C. greater than I_E D. $I_E - I_B$
17. Ideally, a dc load line is a straight line drawn on the collector characteristics curves between
- A. the Q-point and saturation B. $V_{CE(cut\ off)}$ and $I_{C(sat)}$
C. the Q-point and cut-off D. $I_B = 0$ and $I_B = I_C / \beta_{DC}$
18. If a sinusoidal voltage is applied to the base of a biased npn transistor and the resulting sinusoidal collector voltage is clipped near zero volts, the transistor is
- A. being driven into saturation B. being driven into cut off
C. operating nonlinearly D. answer a and c
E. answer b and c
19. The input resistance at the base of a biased transistor depends mainly on
- A. β_{DC} B. β_{DC} and R_E
C. R_B D. R_E
20. In a certain voltage-divider biased npn transistor, V_B is 2.95 V. The dc emitter voltage is approximately
- A. 2.95 V B. 2.25 V
C. 0.7 V D. 3.65 V