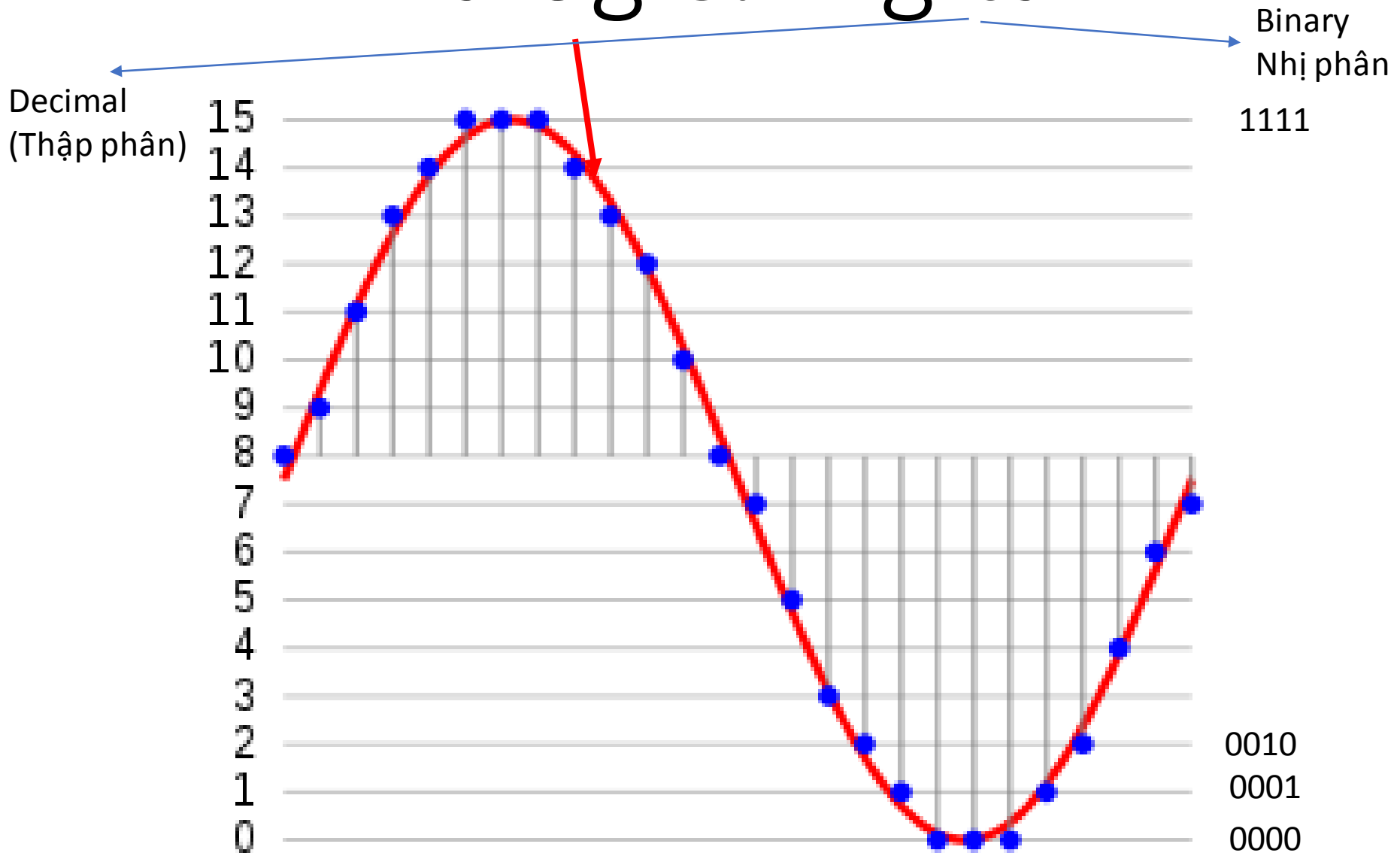


Digital Electronics

- What
- Why
- How

Analog & Digital




4 Bit Binary Adder

Ex: 0110



+

0101

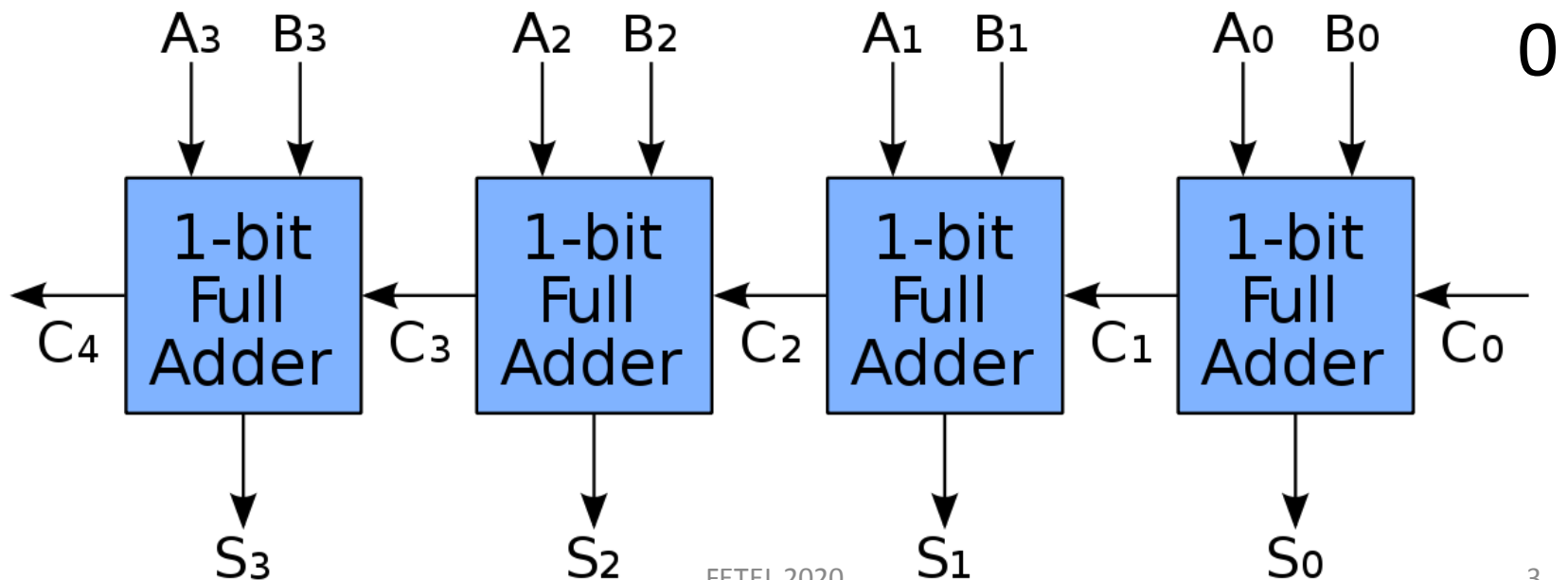


Logic 0 and Logic 1

Acceptable TTL gate input signal levels

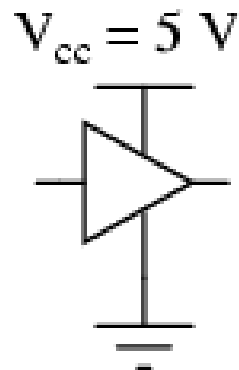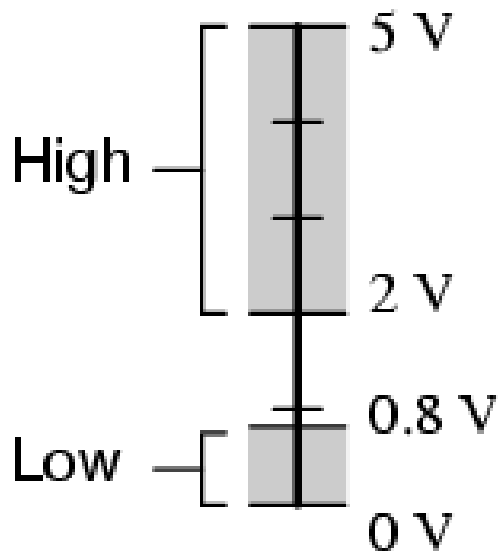

Acceptable TTL gate output signal levels

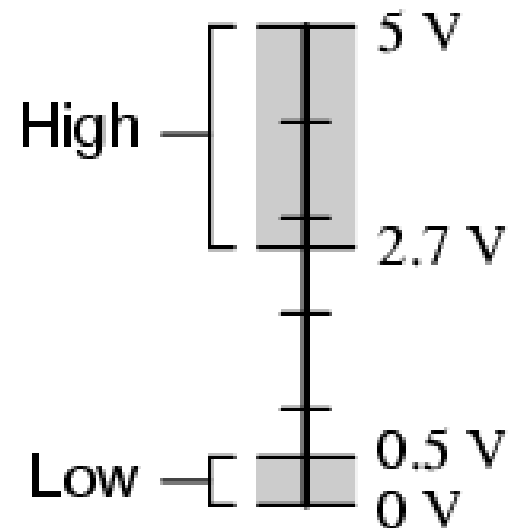


In this example, the range of input voltage (V_{IH}) can represent a HIGH (logic 1) is from 2 V to 5 V for the 5 V logic.....


Noise Margin


*Acceptable TTL gate
input signal levels*

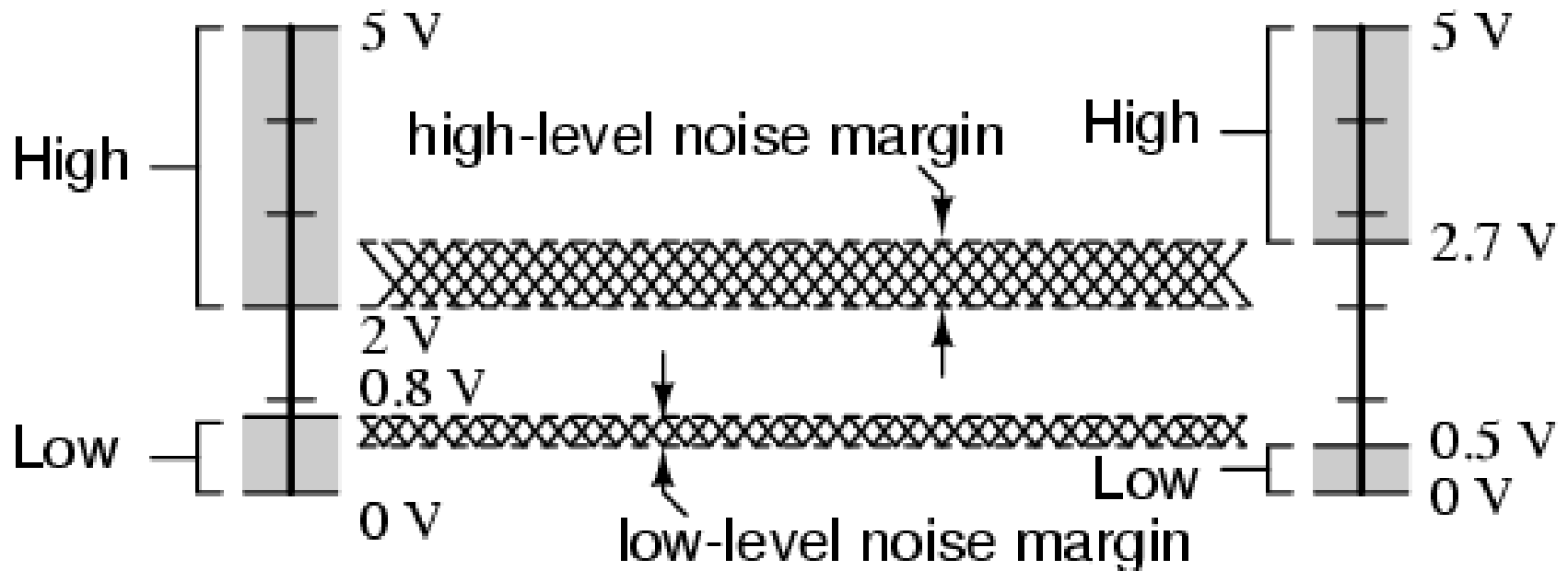*Acceptable TTL gate
output signal levels*



CMOS inverter

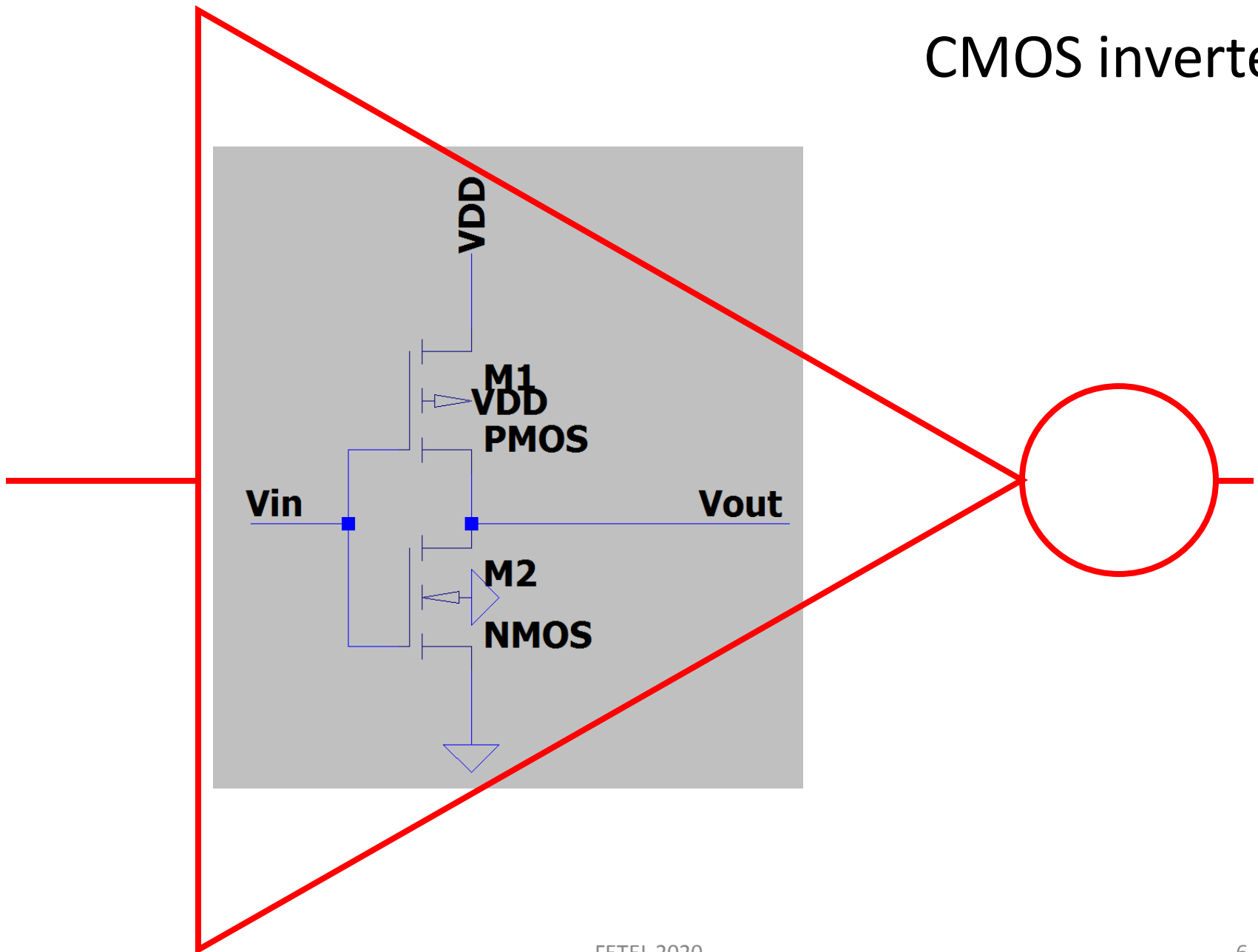

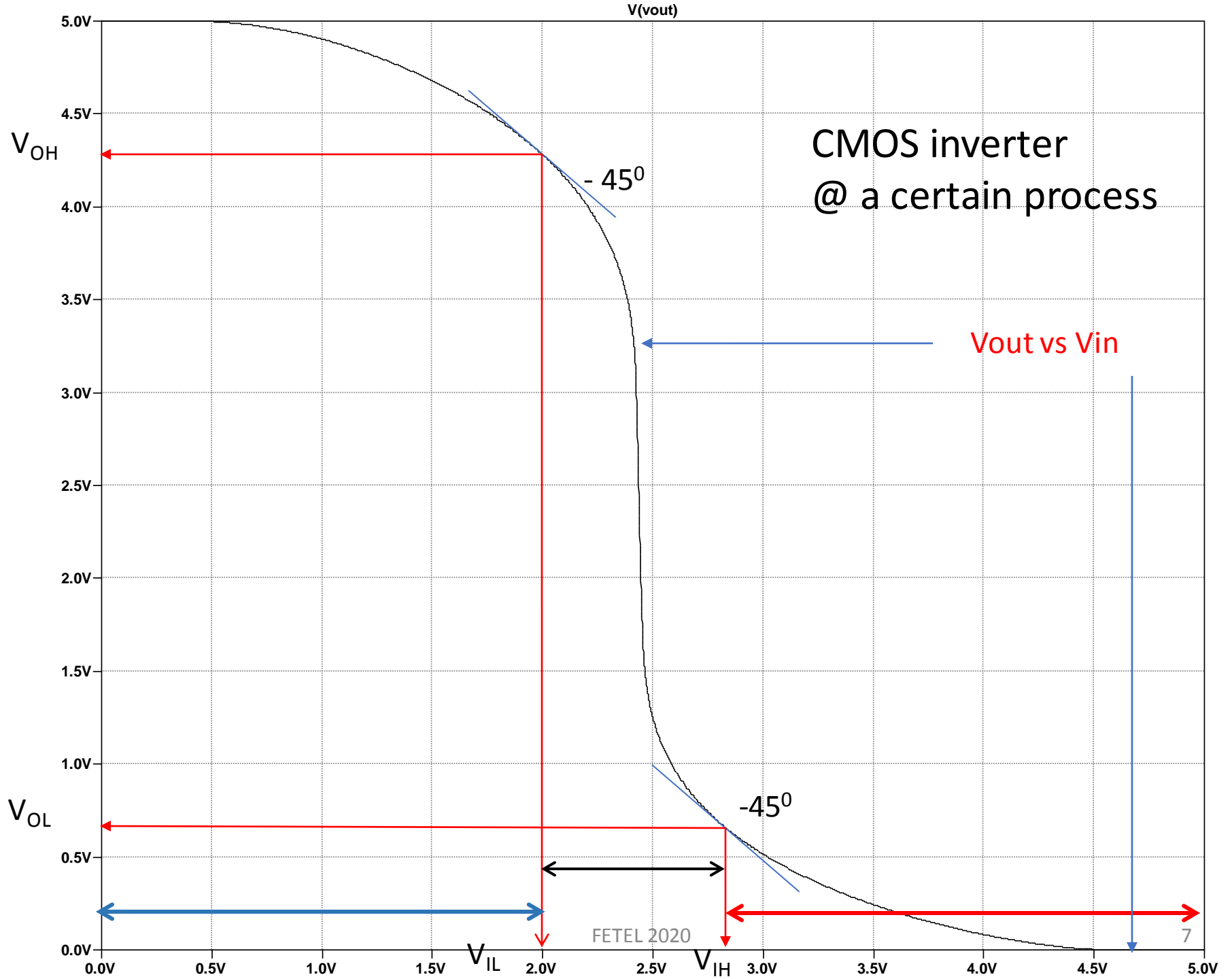

How to find V_{IH} , V_{IL} , V_{OH} , V_{OL}

➔ Datasheet

- Dependable Texas Instruments Quality and Reliability


description/ordering information

These devices contain six independent inverters.

SN5404, SN54LS04, SN54S04, SN7404, SN74LS04, SN74S04 HEX INVERTERS

SDLS029C – DECEMBER 1983 – REVISED JANUARY 2004

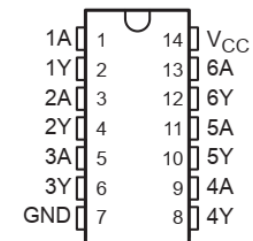
SN5404 . . . J PACKAGE
SN54LS04, SN54S04 . . . J OR W PACKAGE
SN7404, SN74S04 . . . D, N, OR NS PACKAGE
SN74LS04 . . . D, DB, N, OR NS PACKAGE
(TOP VIEW)






		SN54LS04			SN74LS04			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V_{CC}	Supply voltage	4.5	5	5.5	4.75	5	5.25	V
V_{IH}	High-level input voltage	2			2			V
V_{IL}	Low-level input voltage			0.7			0.8	V

PARAMETER	TEST CONDITIONS†			SN54LS04			SN74LS04			UNIT
				MIN	TYP‡	MAX	MIN	TYP‡	MAX	
V_{IK}	$V_{CC} = \text{MIN},$	$I_I = -18 \text{ mA}$				-1.5			-1.5	V
V_{OH}	$V_{CC} = \text{MIN},$	$V_{IL} = \text{MAX},$	$I_{OH} = -0.4 \text{ mA}$	2.5	3.4		2.7	3.4		V
V_{OL}	$V_{CC} = \text{MIN},$	$V_{IH} = 2 \text{ V}$	$I_{OL} = 4 \text{ mA}$		0.25	0.4			0.4	V
			$I_{OL} = 8 \text{ mA}$					0.25	0.5	

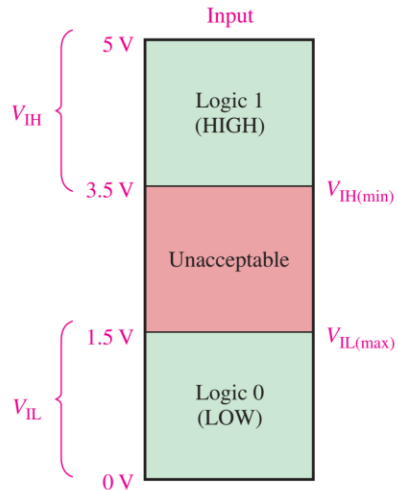
$V_{IH}, V_{IL}, V_{OH}, V_{OL}$ of some technologies




(a) +5 V CMOS

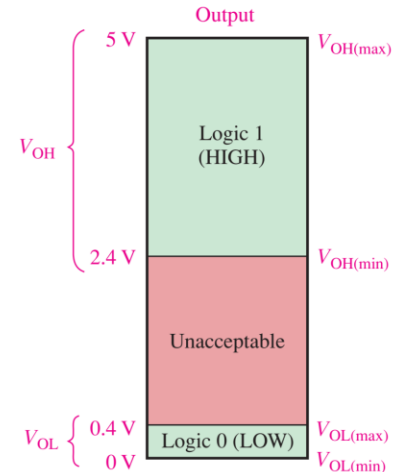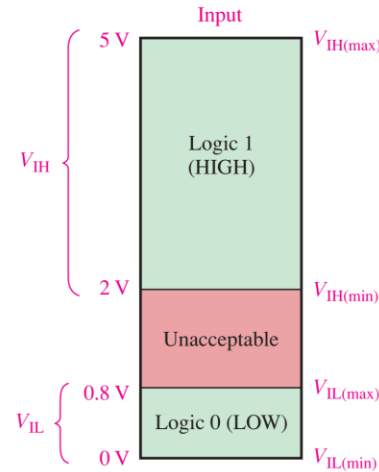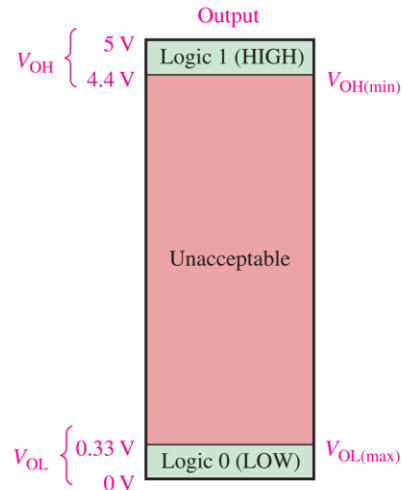

Input and output logic levels for TTL

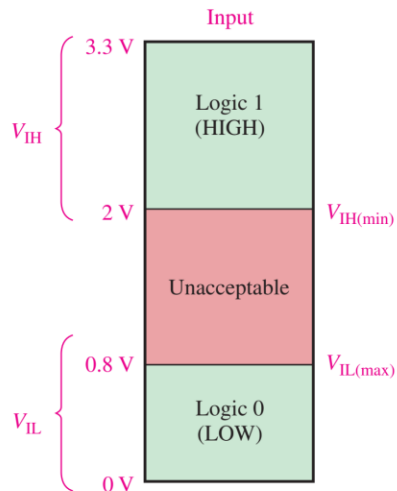


(b) +3.3 V CMOS

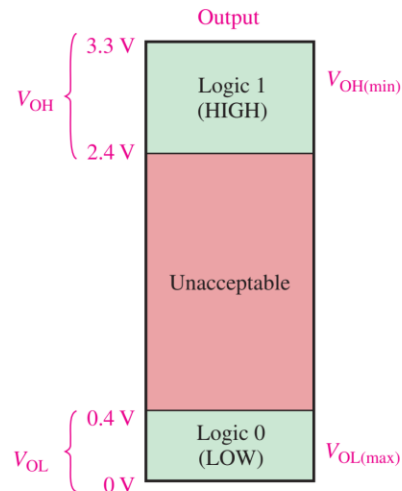


Input and output logic levels for CMOS

Demo

- <http://www.falstad.com/circuit/circuitjs.html>

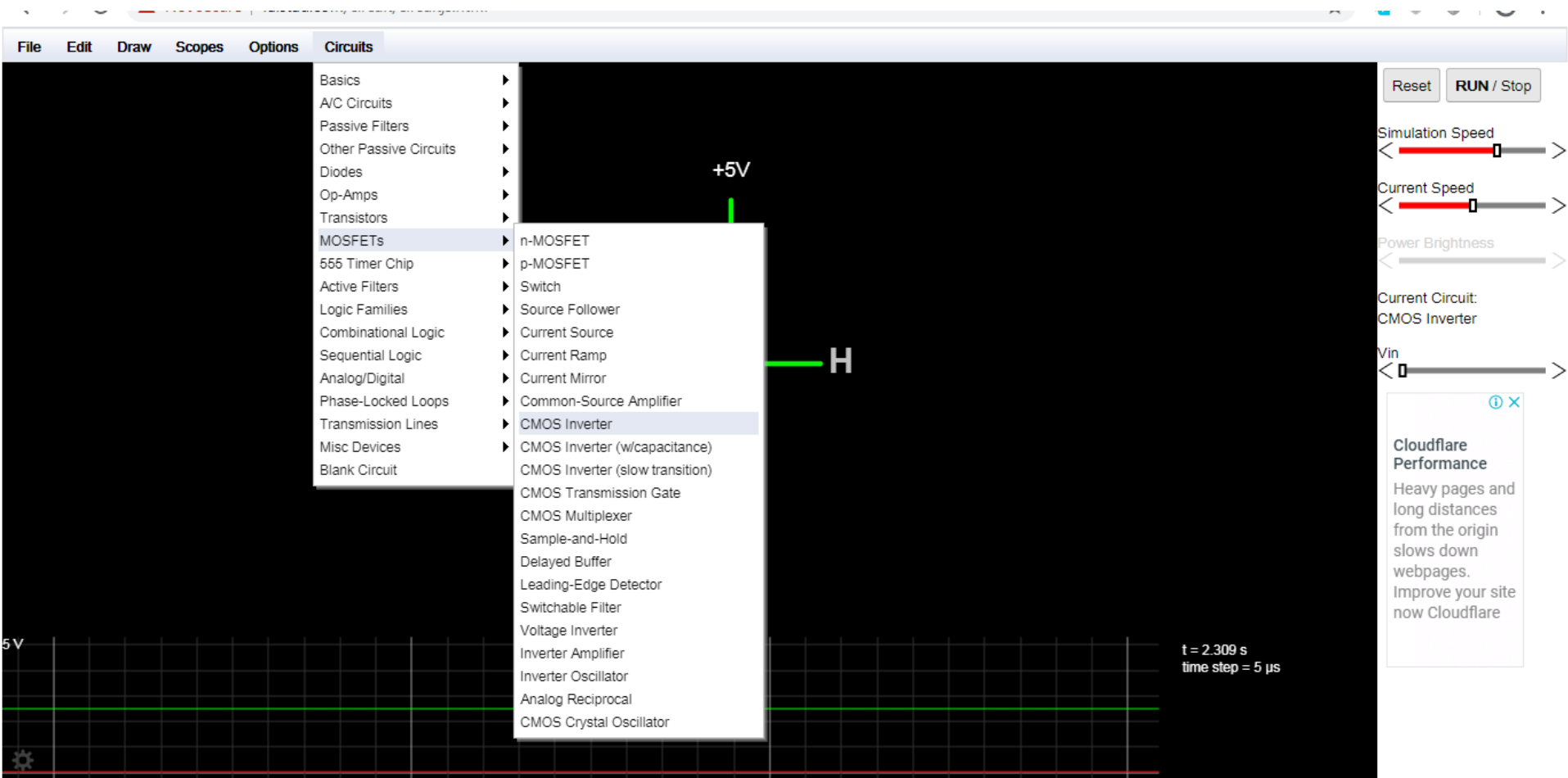

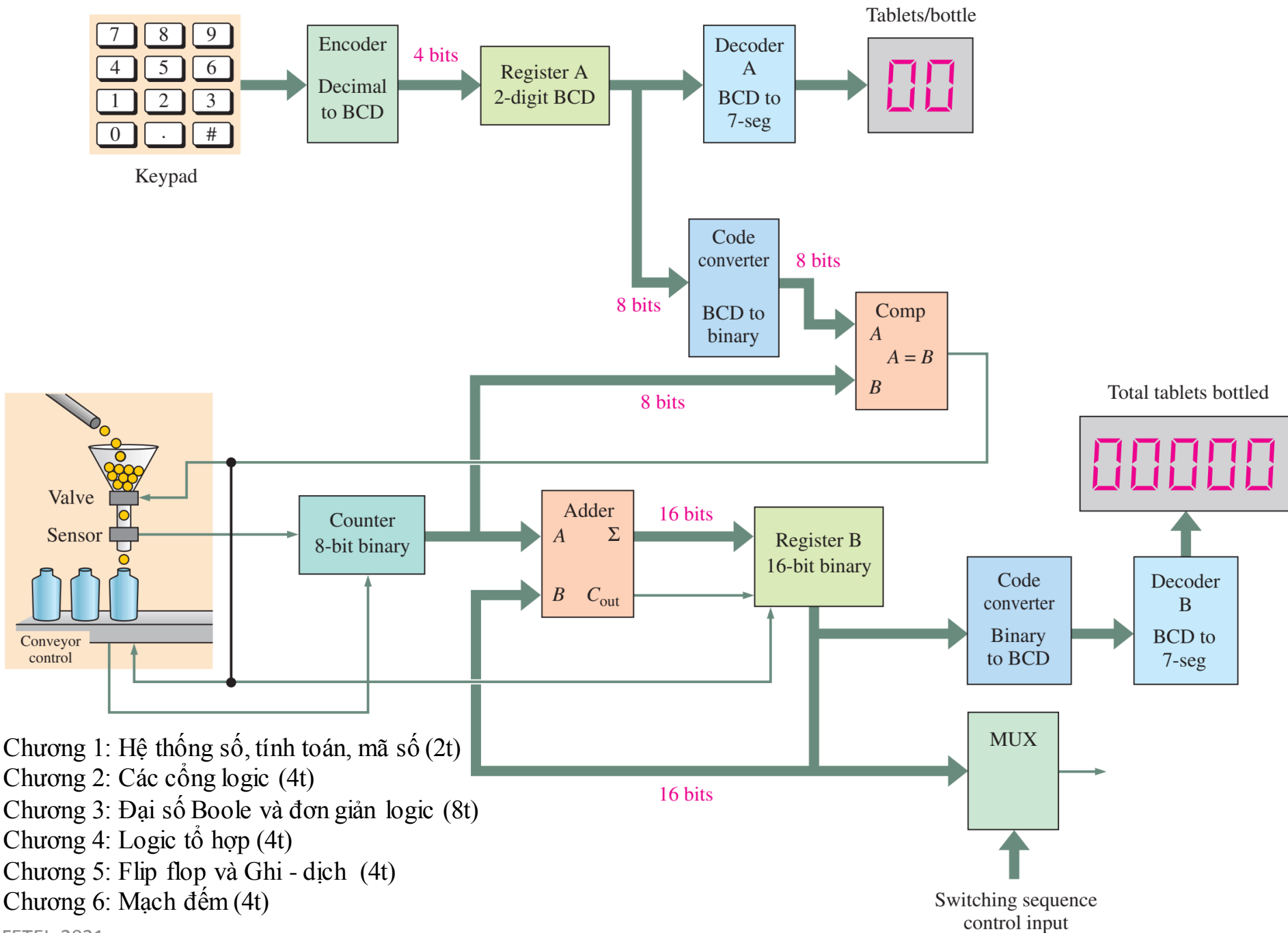

Chương 1: Hệ thống số, tính toán, mã số (2t)

Chương 2: Các cổng logic (4t)

Chương 3: Đại số Boole và đơn giản logic (8t)

Chương 4: Logic tổ hợp (4t)

Chương 5: Flip flop và Ghi - dịch (4t)

Chương 6: Mạch đếm (4t)

