

Sequential Statements

cuu duong than cong . com

cuu duong than cong . com

Outline

1. VHDL process
2. Sequential signal assignment statement
3. Variable assignment statement
4. If statement
5. Case statement
6. Simple for loop statement

1. VHDL Process

- Contains a set of sequential statements to be executed sequentially
- The whole process is a concurrent statement
- Can be interpreted as a circuit part enclosed inside of a black box
- May or may not be able to be mapped to physical hardware

- Two types of process
 - A process with a sensitivity list
 - A process with wait statement

cuu duong than cong . com

cuu duong than cong . com

A process with a sensitivity list

- Syntax

process(sensitivity_list)

declarations;

begin

sequential statement;

sequential statement;

...

end process;

- A process is like a circuit part, which can be
 - active (known *activated*)
 - inactive (known as *suspended*).
- A process is activated when a signal in the sensitivity list changes its value
- Its statements will be executed sequentially until the end of the process

- E.g, 3-input and circuit

```
signal a,b,c,y: std_logic;
```

```
process(a,b,c)
```

```
begin
```

```
    y <= a and b and c;
```

```
end process;
```

- How to interpret this:

```
process(a)
```

```
begin
```

```
    y <= a and b and c;
```

```
end process;
```

- For a combinational circuit, all input should be included in the sensitivity list

A process with wait statement

- Process has no sensitivity list
- Process continues the execution until a wait statement is reached and then suspended
- Forms of wait statement:
 - **wait on** signals;
 - **wait until** boolean_expression;
 - **wait for** time_expression;

- E.g, 3-input and circuit
process
begin
 $y \leq a \text{ and } b \text{ and } c;$
 wait on a, b, c;
end process;

- A process can has multiple wait statements
- Process with sensitivity list is preferred for synthesis

2. Sequential signal assignment statement

- Syntax
 `signal_name <= value_expression;`
- Syntax is identical to the simple concurrent signal assignment
- Caution:
 - Inside a process, a signal can be assigned multiple times, but only the last assignment takes effect

- E.g.,

```

process(a,b,c,d)
begin
    y <= a or c;
    y <= a and b;
    y <= c and d;
end process;

```

```

-- yentry := y
-- yexit := a or c;
-- yexit := a and b;
-- yexit := c and d;
-- y <= yexit

```
- It is same as

```

process(a,b,c,d)
begin
    y <= c and d;
end process;

```
- What happens if the 3 statements are concurrent statements?

3. Variable assignment statement

- Syntax

variable_name := value_expression;

- Assignment takes effect immediately
- No time dimension (i.e., no delay)
- Behave like variables in C
- Difficult to map to hardware (depending on context)

- E.g.,

```
process(a,b,c)
```

```
    variable tmp: std_logic;
```

```
begin
```

```
    tmp := '0';
```

```
    tmp := tmp or a;
```

```
    tmp := tmp or b;
```

```
    y <= tmp;
```

```
end process;
```

- interpretation:

process(a,b,c)

variable tmp0, tmp1, tmp2: std_logic;

begin


tmp0 := '0';

tmp1 := tmp0 **or** a;

tmp2 := tmp1 **or** b;

y <= tmp2;

end process;

 

- What happens if signal is used?

```
process(a,b,c,tmp)
```

```
begin
```

```
-- tmpentry := tmp
```

```
tmp <= '0';
```

```
-- tmpexit := '0';
```

```
tmp <= tmp or a; -- tmpexit := tmpentry or a;
```

```
tmp <= tmp or b; -- tmpexit := tmpentry or b;
```

```
end process;
```

```
-- tmp <= tmpexit
```

- Same as:

```
process(a,b,c,tmp)
```

```
begin
```

```
tmp <= tmp or b;
```

```
end process;
```

4. IF statement

- Syntax
- Examples
- Comparison to conditional signal assignment
- Incomplete branch and incomplete signal assignment
- Conceptual Implementation

Syntax

```
if boolean_expr_1 then  
    sequential_statements;  
elsif boolean_expr_2 then  
    sequential_statements;  
elsif boolean_expr_3 then  
    sequential_statements;  
...  
else  
    sequential_statements;  
end if;
```

E.g., 4-to-1 mux

```
architecture if_arch of mux4 is
begin
    process (a,b,c,d,s)
    begin
        if (s="00") then
            x <= a;
        elsif (s="01") then
            x <= b;
        elsif (s="10") then
            x <= c;
        else
            x <= d;
        end if;
    end process;
end if_arch;
```

input	output
s	x
0 0	a
0 1	b
1 0	c
1 1	d

E.g., 2-to- 2^2 binary decoder

```
architecture if_arch of decoder4 is
begin
```

```
    process (s)
```

```
    begin
```

```
        if (s="00") then
```

```
            x <= "0001";
```

```
        elsif (s="01") then
```

```
            x <= "0010";
```

```
        elsif (s="10") then
```

```
            x <= "0100";
```

```
        else
```

```
            x <= "1000";
```

```
        end if;
```

```
    end process;
```

```
end if_arch;
```

<hr/>	
input	output
s	x
<hr/>	
0 0	0001
0 1	0010
1 0	0100
1 1	1000
<hr/>	

E.g., 4-to-2 priority encoder

architecture if_arch of prio_encoder42 is
begin

process (r)

begin

if (r(3)='1') **then**

 code <= "11";

elsif (r(2)='1') **then**

 code <= "10";

elsif (r(1)='1') **then**

 code <= "01";

else

 code <= "00";

end if;

end process;

 active <= r(3) **or** r(2) **or** r(1) **or** r(0);

end if_arch;

input		output	
r		code	active
1---		11	1
01--		10	1
001-		01	1
0001		00	1
0000		00	0

Comparison to conditional signal assignment

- Two statements are the same if there is only one output signal in if statement
- If statement is more flexible
- Sequential statements can be used in then, elsif and else branches:
 - Multiple statements
 - Nested if statements

```

sig <= value_expr_1 when boolean_expr_1 else
    value_expr_2 when boolean_expr_2 else
    value_expr_3 when boolean_expr_3 else
        . . .
    value_expr_n;

```

It can be written as

```

process (...)
    if boolean_expr_1 then
        sig <= value_expr_1;
    elsif boolean_expr_2 then
        sig <= value_expr_2;
    elsif boolean_expr_3 then
        sig <= value_expr_3;
        . . .
    else
        sig <= value_expr_n;
    end if;
end process

```

e.g., find the max of a, b, c

```
if (a > b) then  
    if (a > c) then  
        max <= a;    --  $a > b$  and  $a > c$   
    else  
        max <= c;    --  $a > b$  and  $c \geq a$   
    end if;  
  
else  
    if (b > c) then  
        max <= b;    --  $b \geq a$  and  $b > c$   
    else  
        max <= c;    --  $b \geq a$  and  $c \geq b$   
    end if;  
end if;
```

e.g., 2 conditional sig assignment codes

```
signal ac_max, bc_max: std_logic;  
.  
.  
.  
ac_max <= a when (a > c) else c;  
bc_max <= b when (b > c) else c;  
max <= ac_max when (a > b) else bc_max;
```

```
max <= a when ((a > b) and (a > c)) else  
      c when (a > b) else  
      b when (b > c) else  
      c;
```


- 2 conditional sig assign implementations

```
signal ac_max, bc_max: std_logic;  
.  
.  
.  
ac_max <= a when (a > c) else c;  
bc_max <= b when (b > c) else c;  
max <= ac_max when (a > b) else bc_max;
```

```
max <= a when ((a > b) and (a > c)) else  
      c when (a > b) else  
      b when (b > c) else  
      c;
```

e.g., “sharing” boolean condition

```
if (a > b and op="00") then  
    y <= a - b;  
    z <= a - 1;  
    status <= '0';  
else  
    y <= b - a;  
    z <= b - 1;  
    status <= '1';  
end if;
```

```
y <= a-b when (a > b and op="00") else  
    b-a;  
z <= a-1 when (a > b and op="00") else  
    b-1;  
status <= '0' when (a > b and op="00") else  
    '1';
```

Incomplete branch and incomplete signal assignment

- According to VHDL definition:
 - Only the “then” branch is required; “elsif” and “else” branches are optional
 - Signals do not need to be assigned in all branch
 - When a signal is unassigned due to omission, it keeps the “previous value” (implying “memory”)

Incomplete branch

- E.g.,

```
process (a , b)
begin
    if (a=b) then
        eq <= '1' ;
    end if ;
end process ;
```

- It implies

```
process (a , b)
begin
    if (a=b) then
        eq <= '1' ;
    else
        eq <= eq ;
    end if ;
end process
```

- fix

```
process (a , b)
begin
    if (a=b) then
        eq <= '1' ;
    else
        eq <= '0' ;
    end if ;
end process
```

Incomplete signal assignment

- E.g.,

```
process (a, b)
begin
    if (a > b) then
        gt <= '1';
    elsif (a = b) then
        eq <= '1';
    else
        lt <= '1';
    end if;
end process;
```

- **Fix #1:**

```

process (a , b)
begin
    if (a>b) then
        gt <= '1';
        eq <= '0';
        lt <= '0';
    elsif (a=b) then
        gt <= '0';
        eq <= '1';
        lt <= '0';
    else
        gt <= '0';
        eq <= '0';
        lt <= '1';
    end if;
end process;

```

- **Fix #2**

```

process (a , b)
begin
    gt <= '0';
    eq <= '0';
    lt <= '0';
    if (a>b) then
        gt <= '1';
    elsif (a=b) then
        eq <= '1';
    else
        lt <= '1';
    end if;
end process;


```


Conceptual implementation

- Same as conditional signal assignment statement if the if statement consists of
 - One output signal
 - One sequential signal assignment in each branch
- Multiple sequential statements can be constructed recursively



e.g.
 
```
if boolean_expr then
  sig_a <= value_expr_a_1;
  sig_b <= value_expr_b_1;
else
  sig_a <= value_expr_a_2;
  sig_b <= value_expr_b_2;
end if;
```



e.g.
  
```
if boolean_expr_1 then
    if boolean_expr_2 then
        signal_a <= value_expr_1;
    else
        signal_a <= value_expr_2;
    end if;
else
    if boolean_expr_3 then
        signal_a <= value_expr_3;
    else
        signal_a <= value_expr_4;
    end if;
end if;
```



5. Case statement

- Syntax
- Examples
- Comparison to selected signal assignment statement
- Incomplete signal assignment
- Conceptual Implementation

Syntax

case case_expression **is**

when choice_1 =>

 sequential statements;

when choice_2 =>

 sequential statements;

 . . .

when choice_n =>

 sequential statements;

end case;

E.g., 4-to-1 mux

**architecture case_arch of mux4 is
begin**

process (a,b,c,d,s)

begin

case s is

when "00" =>

x <= a;

when "01" =>

x <= b;

when "10" =>

x <= c;

when others =>

x <= d;

end case;

end process;

end case_arch;

input	output
s	x
0 0	a
0 1	b
1 0	c
1 1	d

E.g., 2-to-2² binary decoder

architecture case_arch of decoder4 is
begin

 proc1:

 process(s)

 begin

 case s is

 when "00" =>

 x <= "0001";

 when "01" =>

 x <= "0010";

 when "10" =>

 x <= "0100";

 when others =>

 x <= "1000";

 end case;

 end process;

END case_arch;

input	output
s	x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

E.g., 4-to-2 priority encoder

```
architecture case_arch of prio_encoder42 is
begin
    process (r)
    begin
        case r is
            when "1000" | "1001" | "1010" | "1011" |
                 "1100" | "1101" | "1110" | "1111" =>
                code <= "11";
            when "0100" | "0101" | "0110" | "0111" =>
                code <= "10";
            when "0010" | "0011" =>
                code <= "01";
            when others =>
                code <= "00";
        end case;
    end process;
    active <= r(3) or r(2) or r(1) or r(0);
end case_arch;
```

input r	output	
	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

Comparison to selected signal assignment

- Two statements are the same if there is only one output signal in case statement
- Case statement is more flexible
- Sequential statements can be used in choice branches

```

with sel_exp select
    sig <= value_expr_1 when choice_1 ,
        value_expr_2 when choice_2 ,
        value_expr_3 when choice_3 ,
        . . .
        value_expr_n when choice_n;

```

It can be rewritten as:

```

case sel_exp is
    when choice_1 =>
        sig <= value_expr_1;
    when choice_2 =>
        sig <= value_expr_2;
    when choice_3 =>
        sig <= value_expr_3;
    . . .

    when choice_n =>
        sig <= value_expr_n;
end case;

```

Incomplete signal assignment

- According to VHDL definition:
 - Signals do not need to be assigned in all choice branch
 - When a signal is unassigned, it keeps the “previous value” (implying “memory”)

Incomplete signal assignment

- E.g.,

```
process (a)
  case a is
    when "100" | "101" | "110" | "111" =>
      high <= '1';
    when "010" | "011" =>
      middle <= '1';
    when others =>
      low <= '1';
  end case;
end process;
```

- **Fix #1:**

```
process(a)
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
      middle <= '0';
      low <= '0';
    when "010"|"011" =>
      high <= '0';
      middle <= '1';
      low <= '0';
    when others =>
      high <= '0';
      middle <= '0';
      low <= '1';
  end case;
end process;
```

- **Fix #2:**


```
process (a)
    high <= '0';
    middle <= '0';
    low <= '0';
    case a is
        when "100" | "101" | "110" | "111" =>
            high <= '1';
        when "010" | "011" =>
            middle <= '1';
        when others =>
            low <= '1';
    end case;
end process;
```

Conceptual implementation

- Same as selected signal assignment statement if the case statement consists of
 - One output signal
 - One sequential signal assignment in each branch
- Multiple sequential statements can be constructed recursively

e.g.
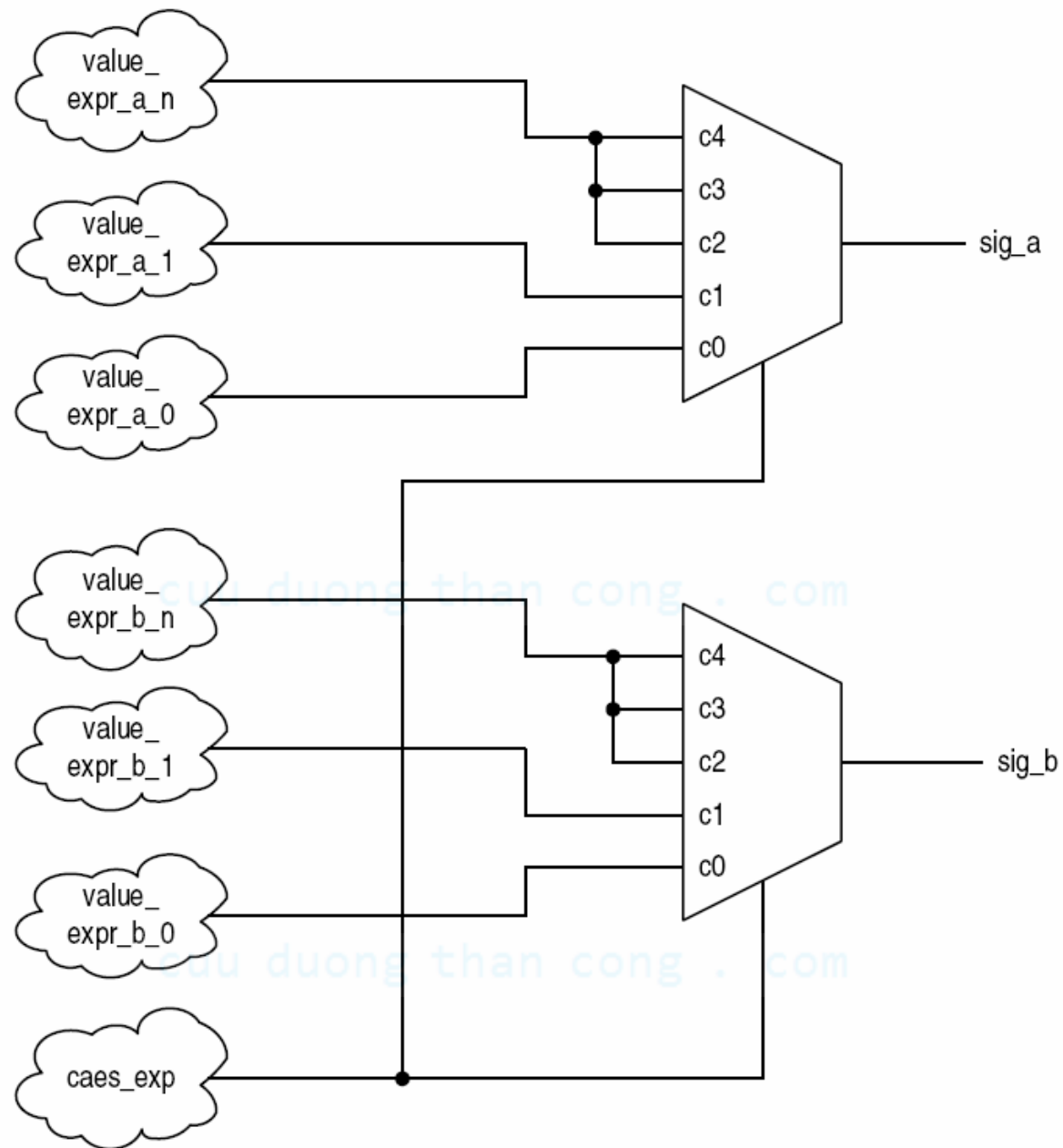
```
case case_exp is  
  when c0 =>  
    sig_a <= value_expr_a_0;  
    sig_b <= value_expr_b_0;  
  when c1 =>  
    sig_a <= value_expr_a_1;  
    sig_b <= value_expr_b_1;  
  when others =>  
    sig_a <= value_expr_a_n;  
    sig_b <= value_expr_b_n;  
end case;
```



6. Simple for loop statement

- Syntax
- Examples
- Conceptual Implementation

cuu duong than cong . com

cuu duong than cong . com

- VHDL provides a variety of loop constructs
- Only a restricted form of loop can be synthesized
- Syntax of simple for loop:
 for index **in** loop_range **loop**
 sequential statements;
 end loop;
- loop_range must be static
- Index assumes value of loop_range from left to right

- E.g., bit-wide xor

```
library ieee;
use ieee.std_logic_1164.all;

entity wide_xor is
    port(
        a, b: in std_logic_vector(3 downto 0);
        y: out std_logic_vector(3 downto 0)
    );
end wide_xor;

architecture demo_arch of wide_xor is
    constant WIDTH: integer := 4;
begin
    process(a, b)
    begin
        for i in (WIDTH-1) downto 0 loop
            y(i) <= a(i) xor b(i);
        end loop;
    end process;
end demo_arch;
```

- E.g., reduced-xor

```
library ieee;
use ieee.std_logic_1164.all;

entity reduced_xor_demo is
  port(
    a: in std_logic_vector(3 downto 0);
    y: out std_logic
  );
end reduced_xor_demo;

architecture demo_arch of reduced_xor_demo is
  constant WIDTH: integer := 4;
  signal tmp: std_logic_vector(WIDTH-1 downto 0);
begin
  process(a, tmp)
  begin
    tmp(0) <= a(0);    -- boundary bit
    for i in 1 to (WIDTH-1) loop
      tmp(i) <= a(i) xor tmp(i-1);
    end loop;
  end process;
  y <= tmp(WIDTH-1);
end demo_arch;
```

Conceptual implementation

- “Unroll” the loop
- For loop should be treated as “shorthand” for repetitive statements
- E.g., bit-wise xor

```
y (3)  <=  a (3)  xor  b (3) ;  
y (2)  <=  a (2)  xor  b (2) ;  
y (1)  <=  a (1)  xor  b (1) ;  
y (0)  <=  a (0)  xor  b (0) ;
```

- E.g., reduced-xor

```
tmp(0)  <=  a(0);  
tmp(1)  <=  a(1)  xor  tmp(0);  
tmp(2)  <=  a(2)  xor  tmp(1);  
tmp(3)  <=  a(3)  xor  tmp(2);  
y  <=  tmp(3);
```


Synthesis of sequential statements

- Concurrent statements
 - Modeled after hardware
 - Have clear, direct mapping to physical structures
- Sequential statements
 - Intended to describe “behavior”
 - Flexible and versatile
 - Can be difficult to be realized in hardware
 - Can be easily abused

- Think hardware
- Designing hardware is not converting a C program to a VHDL program