

CONTENTS

Preface	xix
Acknowledgments	xxiii
1 Introduction to Digital System Design	1
1.1 Introduction	1
1.2 Device technologies	2
1.2.1 Fabrication of an IC	2
1.2.2 Classification of device technologies	2
1.2.3 Comparison of technologies	5
1.3 System representation	8
1.4 Levels of Abstraction	9
1.4.1 Transistor-level abstraction	10
1.4.2 Gate-level abstraction	10
1.4.3 Register-transfer-level (RT-level) abstraction	11
1.4.4 Processor-level abstraction	12
1.5 Development tasks and EDA software	12
1.5.1 Synthesis	13
1.5.2 Physical design	14
1.5.3 Verification	14
1.5.4 Testing	16
1.5.5 EDA software and its limitations	16
	vii

1.6	Development flow	17
1.6.1	Flow of a medium-sized design targeting FPGA	17
1.6.2	Flow of a large design targeting FPGA	19
1.6.3	Flow of a large design targeting ASIC	19
1.7	Overview of the book	20
1.7.1	Scope	20
1.7.2	Goal	20
1.8	Bibliographic notes	21
	Problems	22
2	Overview of Hardware Description Languages	23
2.1	Hardware description languages	23
2.1.1	Limitations of traditional programming languages	23
2.1.2	Use of an HDL program	24
2.1.3	Design of a modern HDL	25
2.1.4	VHDL	25
2.2	Basic VHDL concept via an example	26
2.2.1	General description	27
2.2.2	Structural description	30
2.2.3	Abstract behavioral description	33
2.2.4	Testbench	35
2.2.5	Configuration	37
2.3	VHDL in development flow	38
2.3.1	Scope of VHDL	38
2.3.2	Coding for synthesis	40
2.4	Bibliographic notes	40
	Problems	41
3	Basic Language Constructs of VHDL	43
3.1	Introduction	43
3.2	Skeleton of a basic VHDL program	44
3.2.1	Example of a VHDL program	44
3.2.2	Entity declaration	44
3.2.3	Architecture body	46
3.2.4	Design unit and library	46
3.2.5	Processing of VHDL code	47
3.3	Lexical elements and program format	47
3.3.1	Lexical elements	47
3.3.2	VHDL program format	49
3.4	Objects	51
3.5	Data types and operators	53

3.5.1	Predefined data types in VHDL	53
3.5.2	Data types in the IEEE std_logic_1164 package	56
3.5.3	Operators over an array data type	58
3.5.4	Data types in the IEEE numeric_std package	60
3.5.5	The std_logic_arith and related packages	64
3.6	Synthesis guidelines	65
3.6.1	Guidelines for general VHDL	65
3.6.2	Guidelines for VHDL formatting	66
3.7	Bibliographic notes	66
	Problems	66
4	Concurrent Signal Assignment Statements of VHDL	69
4.1	Combinational versus sequential circuits	69
4.2	Simple signal assignment statement	70
4.2.1	Syntax and examples	70
4.2.2	Conceptual implementation	70
4.2.3	Signal assignment statement with a closed feedback loop	71
4.3	Conditional signal assignment statement	72
4.3.1	Syntax and examples	72
4.3.2	Conceptual implementation	76
4.3.3	Detailed implementation examples	78
4.4	Selected signal assignment statement	85
4.4.1	Syntax and examples	85
4.4.2	Conceptual implementation	88
4.4.3	Detailed implementation examples	90
4.5	Conditional signal assignment statement versus selected signal assignment statement	93
4.5.1	Conversion between conditional signal assignment and selected signal assignment statements	93
4.5.2	Comparison between conditional signal assignment and selected signal assignment statements	94
4.6	Synthesis guidelines	95
4.7	Bibliographic notes	95
	Problems	95
5	Sequential Statements of VHDL	97
5.1	VHDL process	97
5.1.1	Introduction	97
5.1.2	Process with a sensitivity list	98
5.1.3	Process with a wait statement	99
5.2	Sequential signal assignment statement	100

5.3	Variable assignment statement	101
5.4	If statement	103
5.4.1	Syntax and examples	103
5.4.2	Comparison to a conditional signal assignment statement	105
5.4.3	Incomplete branch and incomplete signal assignment	107
5.4.4	Conceptual implementation	109
5.4.5	Cascading single-branched if statements	110
5.5	Case statement	112
5.5.1	Syntax and examples	112
5.5.2	Comparison to a selected signal assignment statement	114
5.5.3	Incomplete signal assignment	115
5.5.4	Conceptual implementation	116
5.6	Simple for loop statement	118
5.6.1	Syntax	118
5.6.2	Examples	118
5.6.3	Conceptual implementation	119
5.7	Synthesis of sequential statements	120
5.8	Synthesis guidelines	120
5.8.1	Guidelines for using sequential statements	120
5.8.2	Guidelines for combinational circuits	121
5.9	Bibliographic notes	121
	Problems	121
6	Synthesis Of VHDL Code	125
6.1	Fundamental limitations of EDA software	125
6.1.1	Computability	126
6.1.2	Computation complexity	126
6.1.3	Limitations of EDA software	128
6.2	Realization of VHDL operators	129
6.2.1	Realization of logical operators	129
6.2.2	Realization of relational operators	129
6.2.3	Realization of addition operators	130
6.2.4	Synthesis support for other operators	130
6.2.5	Realization of an operator with constant operands	130
6.2.6	An example implementation	131
6.3	Realization of VHDL data types	133
6.3.1	Use of the <code>std_logic</code> data type	133
6.3.2	Use and realization of the 'Z' value	133
6.3.3	Use of the '-' value	137
6.4	VHDL synthesis flow	139
6.4.1	RT-level synthesis	139
6.4.2	Module generator	141

6.4.3	Logic synthesis	142
6.4.4	Technology mapping	143
6.4.5	Effective use of synthesis software	148
6.5	Timing considerations	149
6.5.1	Propagation delay	150
6.5.2	Synthesis with timing constraints	154
6.5.3	Timing hazards	156
6.5.4	Delay-sensitive design and its dangers	158
6.6	Synthesis guidelines	160
6.7	Bibliographic notes	160
	Problems	160
7	Combinational Circuit Design: Practice	163
7.1	Derivation of efficient HDL description	163
7.2	Operator sharing	164
7.2.1	Sharing example 1	165
7.2.2	Sharing example 2	166
7.2.3	Sharing example 3	168
7.2.4	Sharing example 4	169
7.2.5	Summary	170
7.3	Functionality sharing	170
7.3.1	Addition–subtraction circuit	171
7.3.2	Signed–unsigned dual-mode comparator	173
7.3.3	Difference circuit	175
7.3.4	Full comparator	177
7.3.5	Three-function barrel shifter	178
7.4	Layout-related circuits	180
7.4.1	Reduced-xor circuit	181
7.4.2	Reduced-xor-vector circuit	183
7.4.3	Tree priority encoder	187
7.4.4	Barrel shifter revisited	192
7.5	General circuits	196
7.5.1	Gray code incrementor	196
7.5.2	Programmable priority encoder	199
7.5.3	Signed addition with status	201
7.5.4	Combinational adder-based multiplier	203
7.5.5	Hamming distance circuit	206
7.6	Synthesis guidelines	208
7.7	Bibliographic notes	208
	Problems	208
8	Sequential Circuit Design: Principle	213

8.1	Overview of sequential circuits	213
8.1.1	Sequential versus combinational circuits	213
8.1.2	Basic memory elements	214
8.1.3	Synchronous versus asynchronous circuits	216
8.2	Synchronous circuits	217
8.2.1	Basic model of a synchronous circuit	217
8.2.2	Synchronous circuits and design automation	218
8.2.3	Types of synchronous circuits	219
8.3	Danger of synthesis that uses primitive gates	219
8.4	Inference of basic memory elements	221
8.4.1	D latch	221
8.4.2	D FF	222
8.4.3	Register	225
8.4.4	RAM	225
8.5	Simple design examples	226
8.5.1	Other types of FFs	226
8.5.2	Shift register	229
8.5.3	Arbitrary-sequence counter	232
8.5.4	Binary counter	233
8.5.5	Decade counter	236
8.5.6	Programmable mod- m counter	237
8.6	Timing analysis of a synchronous sequential circuit	239
8.6.1	Synchronized versus unsynchronized input	239
8.6.2	Setup time violation and maximal clock rate	240
8.6.3	Hold time violation	243
8.6.4	Output-related timing considerations	243
8.6.5	Input-related timing considerations	244
8.7	Alternative one-segment coding style	245
8.7.1	Examples of one-segment code	245
8.7.2	Summary	250
8.8	Use of variables in sequential circuit description	250
8.9	Synthesis of sequential circuits	253
8.10	Synthesis guidelines	253
8.11	Bibliographic notes	253
	Problems	254
9	Sequential Circuit Design: Practice	257
9.1	Poor design practices and their remedies	257
9.1.1	Misuse of asynchronous signals	258
9.1.2	Misuse of gated clocks	260
9.1.3	Misuse of derived clocks	262
9.2	Counters	265

9.2.1	Gray counter	265
9.2.2	Ring counter	266
9.2.3	LFSR (linear feedback shift register)	269
9.2.4	Decimal counter	272
9.2.5	Pulse width modulation circuit	275
9.3	Registers as temporary storage	276
9.3.1	Register file	276
9.3.2	Register-based synchronous FIFO buffer	279
9.3.3	Register-based content addressable memory	287
9.4	Pipelined design	293
9.4.1	Delay versus throughput	294
9.4.2	Overview on pipelined design	294
9.4.3	Adding pipeline to a combinational circuit	297
9.4.4	Synthesis of pipelined circuits and retiming	307
9.5	Synthesis guidelines	308
9.6	Bibliographic notes	309
	Problems	309
10	Finite State Machine: Principle and Practice	313
10.1	Overview of FSMs	313
10.2	FSM representation	314
10.2.1	State diagram	315
10.2.2	ASM chart	317
10.3	Timing and performance of an FSM	321
10.3.1	Operation of a synchronous FSM	321
10.3.2	Performance of an FSM	324
10.3.3	Representative timing diagram	325
10.4	Moore machine versus Mealy machine	325
10.4.1	Edge detection circuit	326
10.4.2	Comparison of Moore output and Mealy output	328
10.5	VHDL description of an FSM	329
10.5.1	Multi-segment coding style	330
10.5.2	Two-segment coding style	333
10.5.3	Synchronous FSM initialization	335
10.5.4	One-segment coding style and its problem	336
10.5.5	Synthesis and optimization of FSM	337
10.6	State assignment	338
10.6.1	Overview of state assignment	338
10.6.2	State assignment in VHDL	339
10.6.3	Handling the unused states	341
10.7	Moore output buffering	342
10.7.1	Buffering by clever state assignment	342

10.7.2	Look-ahead output circuit for Moore output	344
10.8	FSM design examples	348
10.8.1	Edge detection circuit	348
10.8.2	Arbiter	353
10.8.3	DRAM strobe generation circuit	358
10.8.4	Manchester encoding circuit	363
10.8.5	FSM-based binary counter	367
10.9	Bibliographic notes	369
	Problems	369
11	Register Transfer Methodology: Principle	373
11.1	Introduction	373
11.1.1	Algorithm	373
11.1.2	Structural data flow implementation	374
11.1.3	Register transfer methodology	375
11.2	Overview of FSM	376
11.2.1	Basic RT operation	376
11.2.2	Multiple RT operations and data path	378
11.2.3	FSM as the control path	379
11.2.4	ASMD chart	379
11.2.5	Basic FSM block diagram	380
11.3	FSM design of a repetitive-addition multiplier	382
11.3.1	Converting an algorithm to an ASMD chart	382
11.3.2	Construction of the FSM	385
11.3.3	Multi-segment VHDL description of an FSM	386
11.3.4	Use of a register value in a decision box	389
11.3.5	Four- and two-segment VHDL descriptions of FSM	391
11.3.6	One-segment coding style and its deficiency	394
11.4	Alternative design of a repetitive-addition multiplier	396
11.4.1	Resource sharing via FSM	396
11.4.2	Mealy-controlled RT operations	400
11.5	Timing and performance analysis of FSM	404
11.5.1	Maximal clock rate	404
11.5.2	Performance analysis	407
11.6	Sequential add-and-shift multiplier	407
11.6.1	Initial design	408
11.6.2	Refined design	412
11.6.3	Comparison of three ASMD designs	417
11.7	Synthesis of FSM	417
11.8	Synthesis guidelines	418
11.9	Bibliographic notes	418
	Problems	418

12 Register Transfer Methodology: Practice	421
12.1 Introduction	421
12.2 One-shot pulse generator	422
12.2.1 FSM implementation	422
12.2.2 Regular sequential circuit implementation	424
12.2.3 Implementation using RT methodology	425
12.2.4 Comparison	427
12.3 SRAM controller	430
12.3.1 Overview of SRAM	430
12.3.2 Block diagram of an SRAM controller	434
12.3.3 Control path of an SRAM controller	436
12.4 GCD circuit	445
12.5 UART receiver	455
12.6 Square-root approximation circuit	460
12.7 High-level synthesis	469
12.8 Bibliographic notes	470
Problems	470
 13 Hierarchical Design in VHDL	 473
13.1 Introduction	473
13.1.1 Benefits of hierarchical design	474
13.1.2 VHDL constructs for hierarchical design	474
13.2 Components	475
13.2.1 Component declaration	475
13.2.2 Component instantiation	477
13.2.3 Caveats in component instantiation	480
13.3 Generics	481
13.4 Configuration	485
13.4.1 Introduction	485
13.4.2 Configuration declaration	486
13.4.3 Configuration specification	488
13.4.4 Component instantiation and configuration in VHDL 93	488
13.5 Other supporting constructs for a large system	489
13.5.1 Library	489
13.5.2 Subprogram	491
13.5.3 Package	492
13.6 Partition	495
13.6.1 Physical partition	495
13.6.2 Logical partition	496
13.7 Synthesis guidelines	497
13.8 Bibliographic notes	497

Problems	497
14 Parameterized Design: Principle	499
14.1 Introduction	499
14.2 Types of parameters	500
14.2.1 Width parameters	500
14.2.2 Feature parameters	501
14.3 Specifying parameters	501
14.3.1 Generics	501
14.3.2 Array attribute	502
14.3.3 Unconstrained array	503
14.3.4 Comparison between a generic and an unconstrained array	506
14.4 Clever use of an array	506
14.4.1 Description without fixed-size references	507
14.4.2 Examples	509
14.5 For generate statement	512
14.5.1 Syntax	513
14.5.2 Examples	513
14.6 Conditional generate statement	517
14.6.1 Syntax	517
14.6.2 Examples	518
14.6.3 Comparisons with other feature-selection methods	525
14.7 For loop statement	528
14.7.1 Introduction	528
14.7.2 Examples of a simple for loop statement	528
14.7.3 Examples of a loop body with multiple signal assignment statements	530
14.7.4 Examples of a loop body with variables	533
14.7.5 Comparison of the for generate and for loop statements	536
14.8 Exit and next statements	537
14.8.1 Syntax of the exit statement	537
14.8.2 Examples of the exit statement	537
14.8.3 Conceptual implementation of the exit statement	539
14.8.4 Next statement	540
14.9 Synthesis of iterative structure	541
14.10 Synthesis guidelines	542
14.11 Bibliographic notes	542
Problems	542
15 Parameterized Design: Practice	545
15.1 Introduction	545

15.2	Data types for two-dimensional signals	546
15.2.1	Genuine two-dimensional data type	546
15.2.2	Array-of-arrays data type	548
15.2.3	Emulated two-dimensional array	550
15.2.4	Example	552
15.2.5	Summary	554
15.3	Commonly used intermediate-sized RT-level components	555
15.3.1	Reduced-xor circuit	555
15.3.2	Binary decoder	558
15.3.3	Multiplexer	560
15.3.4	Binary encoder	564
15.3.5	Barrel shifter	566
15.4	More sophisticated examples	569
15.4.1	Reduced-xor-vector circuit	570
15.4.2	Multiplier	572
15.4.3	Parameterized LFSR	586
15.4.4	Priority encoder	588
15.4.5	FIFO buffer	591
15.5	Synthesis of parameterized modules	599
15.6	Synthesis guidelines	599
15.7	Bibliographic notes	600
	Problems	600
16	Clock and Synchronization: Principle and Practice	603
16.1	Overview of a clock distribution network	603
16.1.1	Physical implementation of a clock distribution network	603
16.1.2	Clock skew and its impact on synchronous design	605
16.2	Timing analysis with clock skew	606
16.2.1	Effect on setup time and maximal clock rate	606
16.2.2	Effect on hold time constraint	609
16.3	Overview of a multiple-clock system	610
16.3.1	System with derived clock signals	611
16.3.2	GALS system	612
16.4	Metastability and synchronization failure	612
16.4.1	Nature of metastability	613
16.4.2	Analysis of $MTBF(T_r)$	614
16.4.3	Unique characteristics of $MTBF(T_r)$	616
16.5	Basic synchronizer	617
16.5.1	The danger of no synchronizer	617
16.5.2	One-FF synchronizer and its deficiency	617
16.5.3	Two-FF synchronizer	619
16.5.4	Three-FF synchronizer	620

16.5.5 Proper use of a synchronizer	621
16.6 Single enable signal crossing clock domains	623
16.6.1 Edge detection scheme	623
16.6.2 Level-alternation scheme	627
16.7 Handshaking protocol	630
16.7.1 Four-phase handshaking protocol	630
16.7.2 Two-phase handshaking protocol	637
16.8 Data transfer crossing clock domains	639
16.8.1 Four-phase handshaking protocol data transfer	641
16.8.2 Two-phase handshaking data transfer	650
16.8.3 One-phase data transfer	651
16.9 Data transfer via a memory buffer	652
16.9.1 FIFO buffer	652
16.9.2 Shared memory	660
16.10 Synthesis of a multiple-clock system	661
16.11 Synthesis guidelines	662
16.11.1 Guidelines for general use of a clock	662
16.11.2 Guidelines for a synchronizer	662
16.11.3 Guidelines for an interface between clock domains	662
16.12 Bibliographic notes	663
Problems	663
References	665
Topic Index	667