

Chương 5: Mạch lọc

cuu duong than cong . com

Th.S. Nguyễn Thanh Tuấn



Bộ môn Viễn thông (B3)

cuu duong than cong . com





nttbk97@yahoo.com

Nội dung

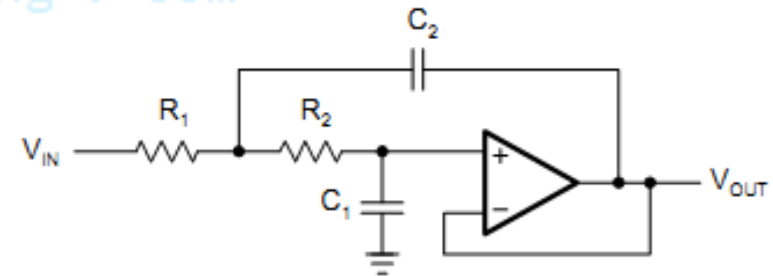
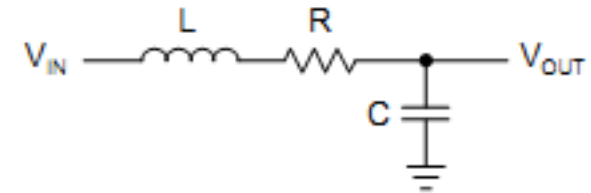
- Phân loại mạch lọc theo linh kiện.
 - Thụ động (RLC)
 - Tích cực (RC & OpAmp)
- Phân loại mạch lọc theo đáp ứng tần số
 - Mạch lọc thông thấp.
 - Mạch lọc thông cao.
 - Mạch lọc thông dải.
 - Mạch lọc chắn dải.
 - Mạch lọc toàn dải (dịch pha tuyến tính).
- Thiết kế mạch lọc Butterworth.



Phân loại mạch lọc (lý tưởng)

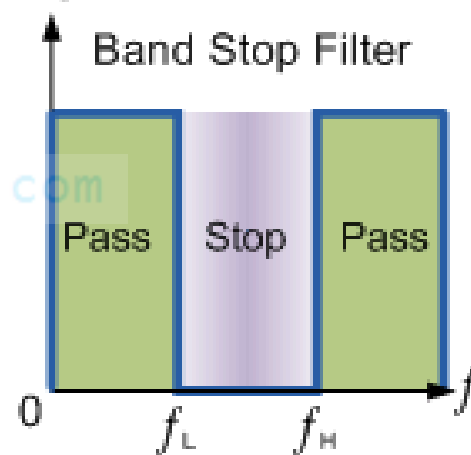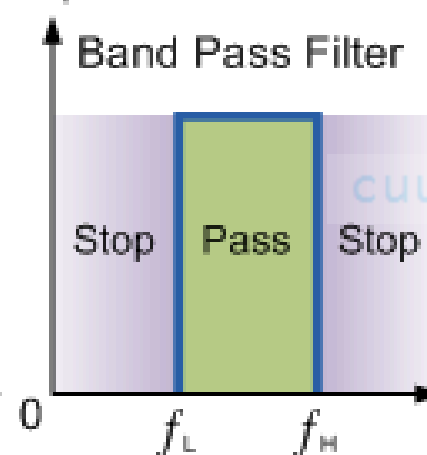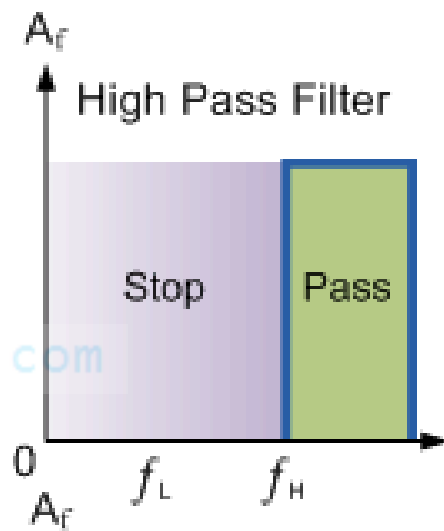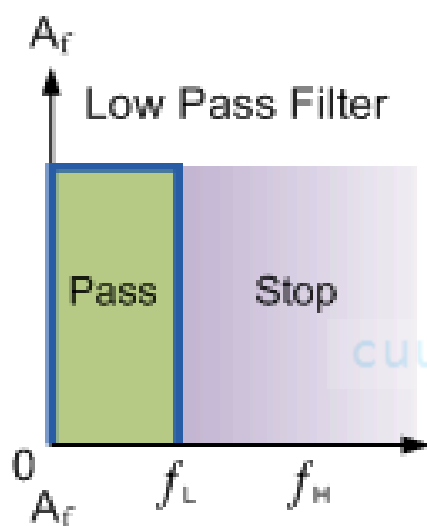

Đáp ứng bộ lọc thực tế

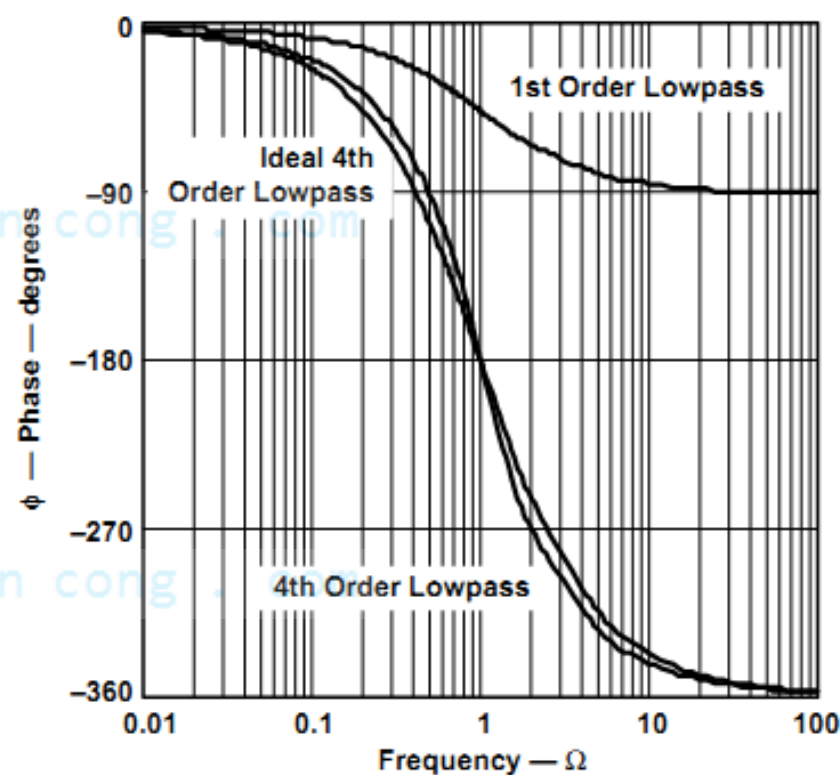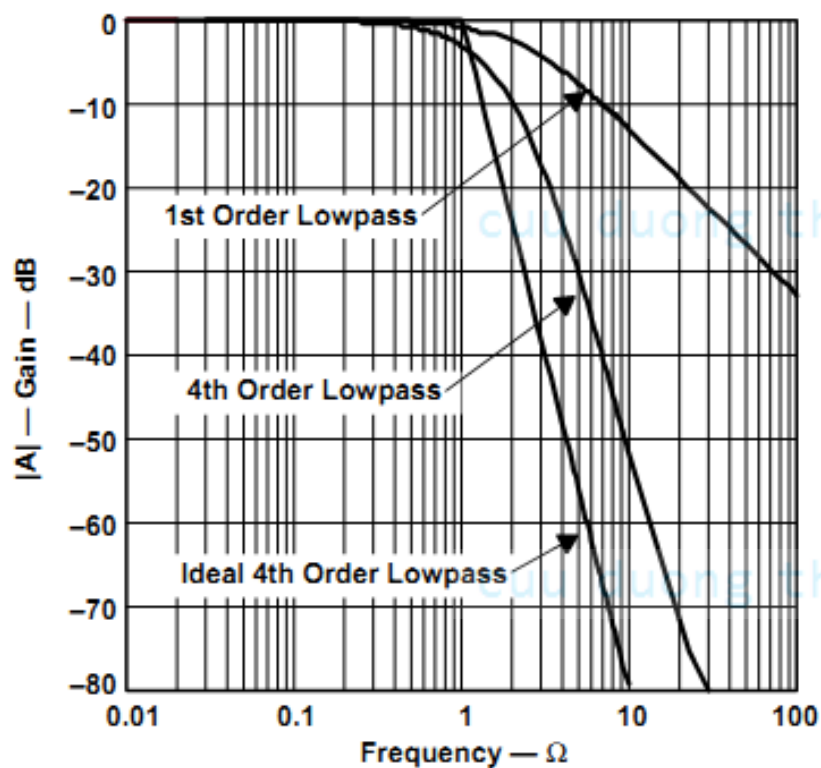

Tiêu chuẩn tối ưu


- Dải thông phẳng cực đại \rightarrow Butterworth
- Khoảng dịch chuyển dải thông-dải chắn nhỏ \rightarrow Tschhebyscheff
- Pha tuyến tính \rightarrow Bessel

$$\frac{A_0}{\prod_i (1 + a_i s + b_i s^2)}$$

$$Q = \frac{f_m}{(f_2 - f_1)}$$

$$Q = \frac{\sqrt{b_i}}{a_i}$$


Thiết kế bộ lọc Butterworth

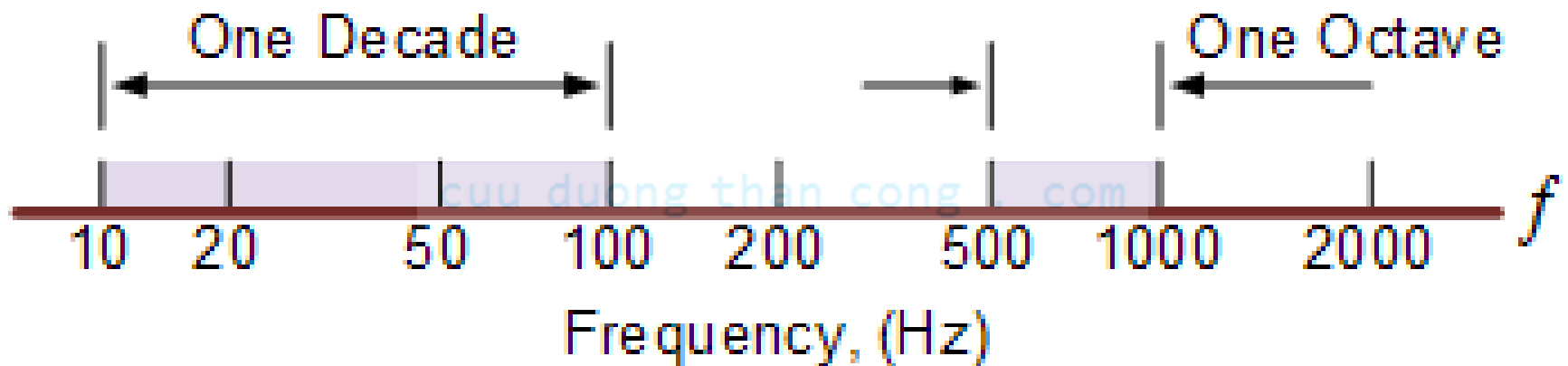


$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

capacitor values should be on the order of magnitude of $(10/f_c) \mu\text{F}$

Độ dốc bộ lọc ghép liên tầng

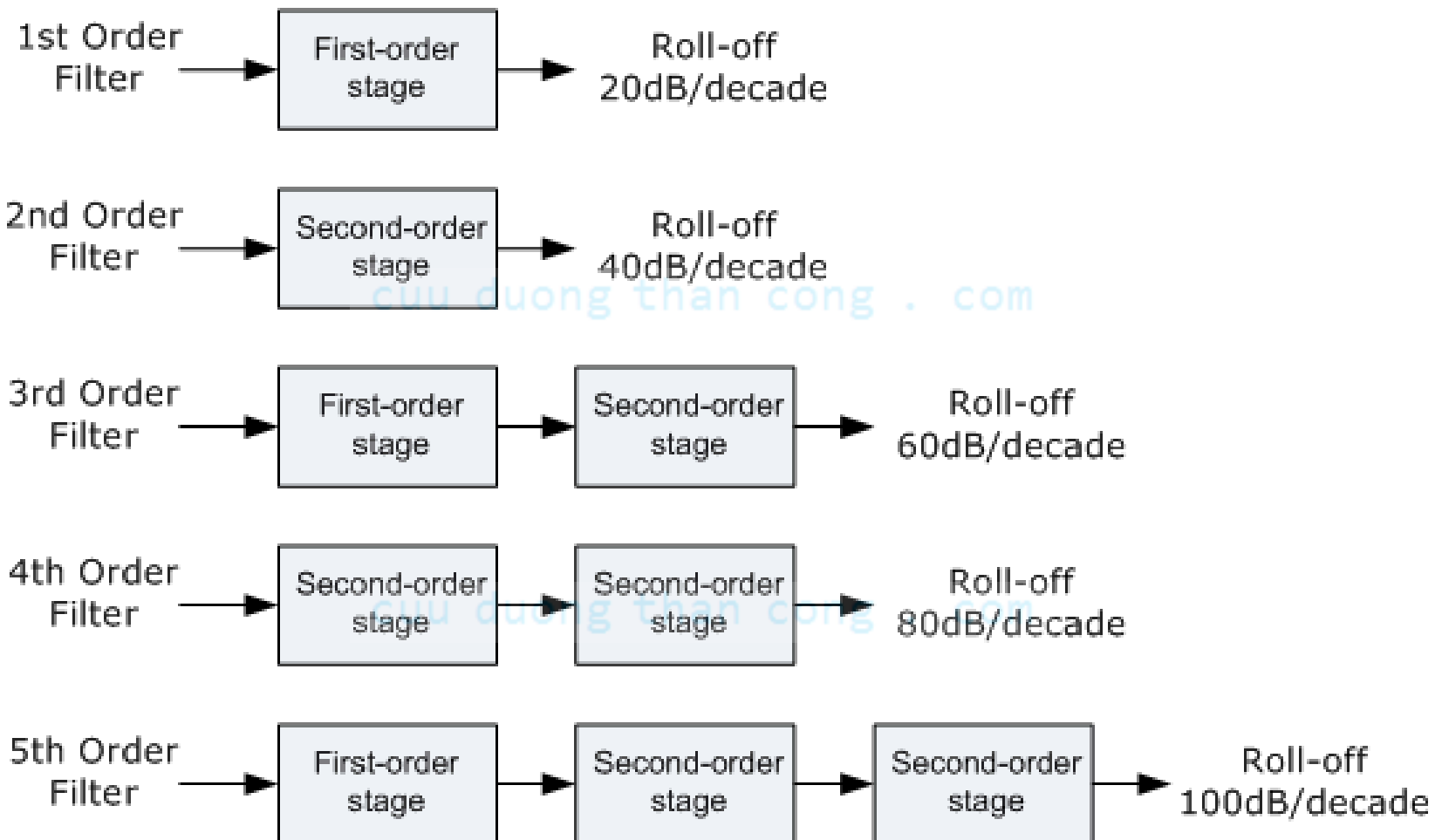

Thiết kế bộ lọc Butterworth (tt)

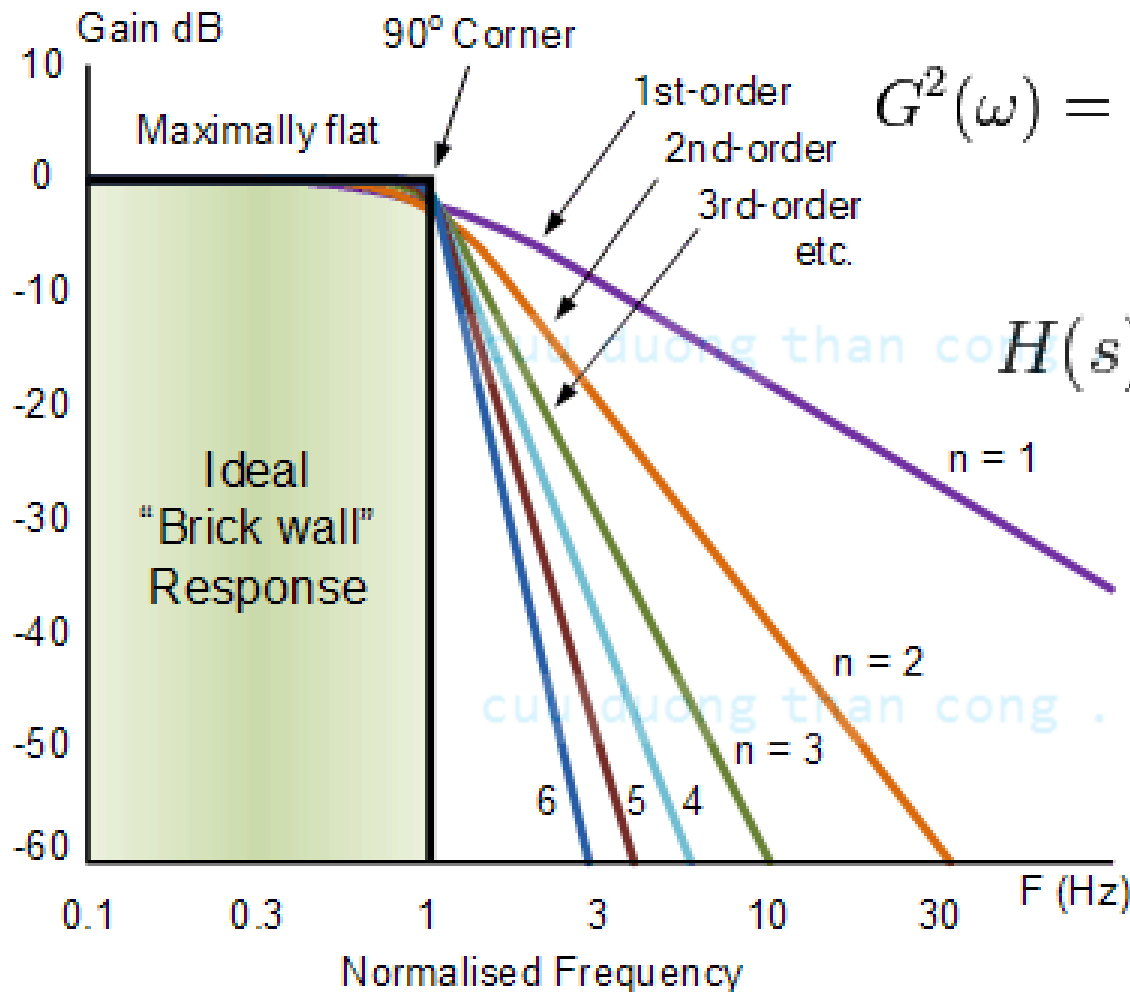


$$G^2(\omega) = |H(j\omega)|^2 = \frac{G_0^2}{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}$$

$$H(s) = \frac{G_0}{\prod_{k=1}^n (s - s_k) / \omega_c}$$

Thiết kế bộ lọc Butterworth (tt)

n	Normalised Denominator Polynomials in Factored Form
1	(1+s)
2	(1+1.414s+s ²)
3	(1+s)(1+s+s ²)
4	(1+0.765s+s ²)(1+1.848s+s ²)
5	(1+s)(1+0.618s+s ²)(1+1.618s+s ²)
6	(1+0.518s+s ²)(1+1.414s+s ²)(1+1.932s+s ²)
7	(1+s)(1+0.445s+s ²)(1+1.247s+s ²)(1+1.802s+s ²)
8	(1+0.390s+s ²)(1+1.111s+s ²)(1+1.663s+s ²)(1+1.962s+s ²)
9	(1+s)(1+0.347s+s ²)(1+s+s ²)(1+1.532s+s ²)(1+1.879s+s ²)
10	(1+0.313s+s ²)(1+0.908s+s ²)(1+1.414s+s ²)(1+1.782s+s ²)(1+1.975s+s ²)
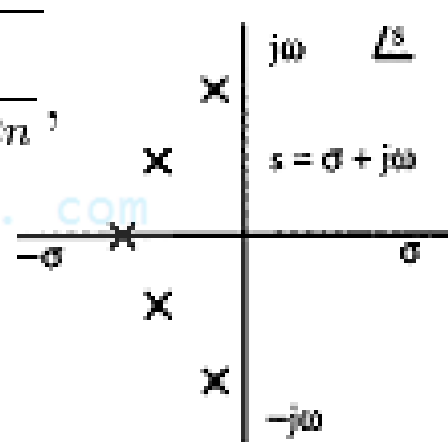
$$G(\omega) = \sqrt{\frac{1}{1 + \omega^{2n}}}$$



$$s_k = \omega_c e^{\frac{j(2k+n-1)\pi}{2n}} \quad k = 1, 2, 3, \dots, n$$

$$H(s) = \frac{G_0}{B_n(a)} \quad a = \frac{s}{\omega_c}$$


cuu duong than cong . com

- n chẵn $B_n(s) = \prod_{k=1}^{\frac{n}{2}} \left[s^2 - 2s \cos \left(\frac{2k + n - 1}{2n} \pi \right) + 1 \right]$


cuu duong than cong . com

- n lẻ $B_n(s) = (s + 1) \prod_{k=1}^{\frac{n-1}{2}} \left[s^2 - 2s \cos \left(\frac{2k + n - 1}{2n} \pi \right) + 1 \right]$

Thông thấp bậc 1

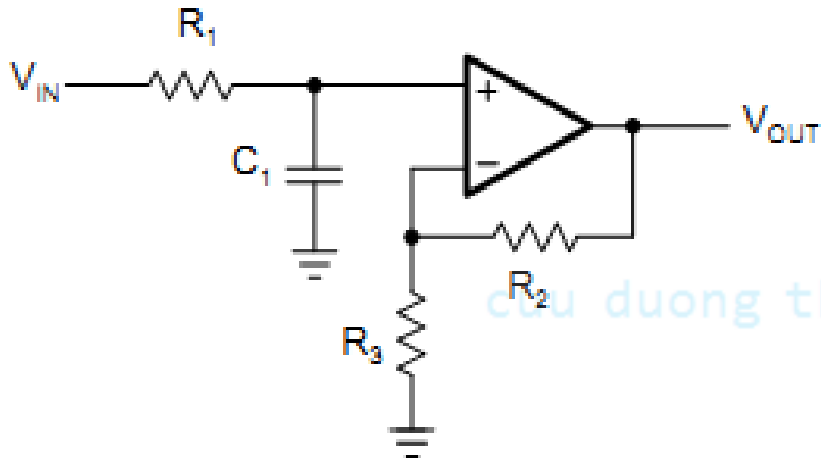

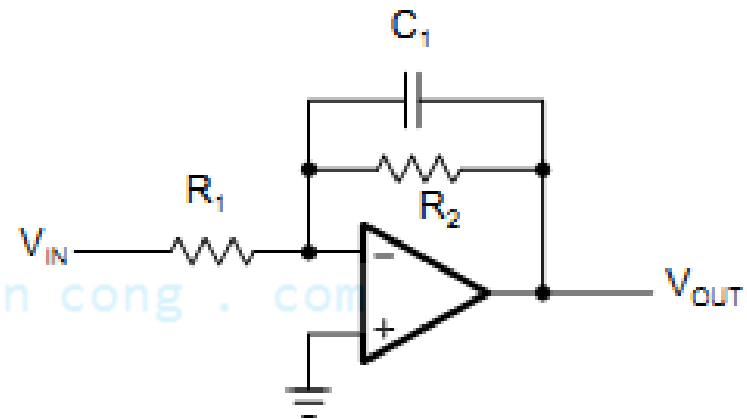
$$\frac{1 + \frac{R_2}{R_3}}{1 + \omega_c R_1 C_1 s}$$



$$\frac{-\frac{R_2}{R_1}}{1 + \omega_c R_2 C_1 s}$$


Thông thấp bậc 2

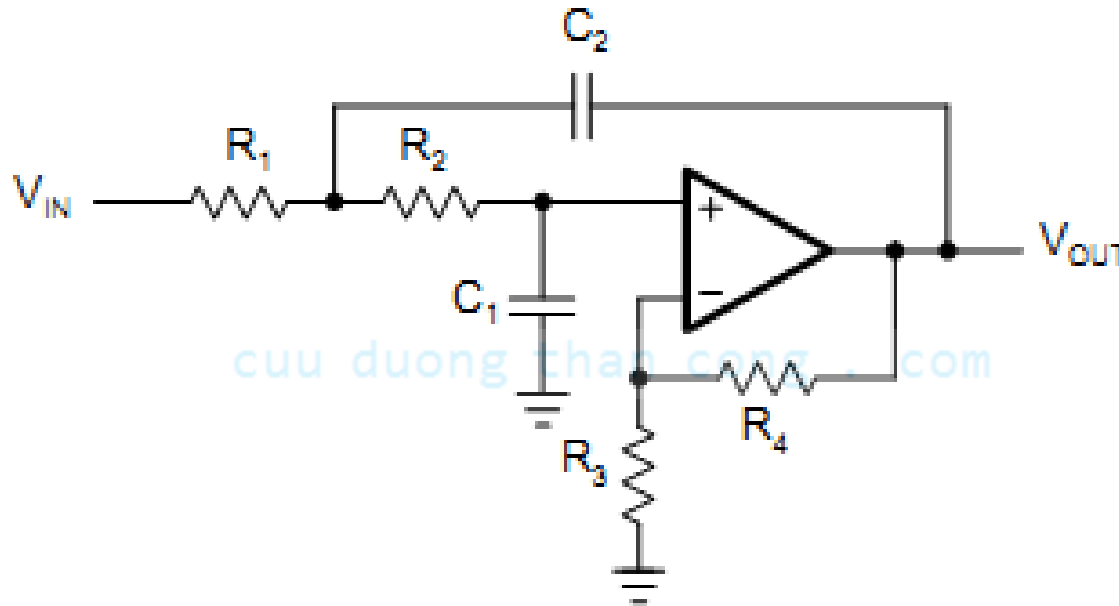

- Hàm truyền đưa về chuẩn hóa từ ω_c

$$\frac{A_0}{1 + \omega_c \left[C_1(R_1 + R_2) + (1 - A_0) R_1 C_2 \right] s + \omega_c^2 R_1 R_2 C_1 C_2 s^2}$$

Thông thấp bậc 2

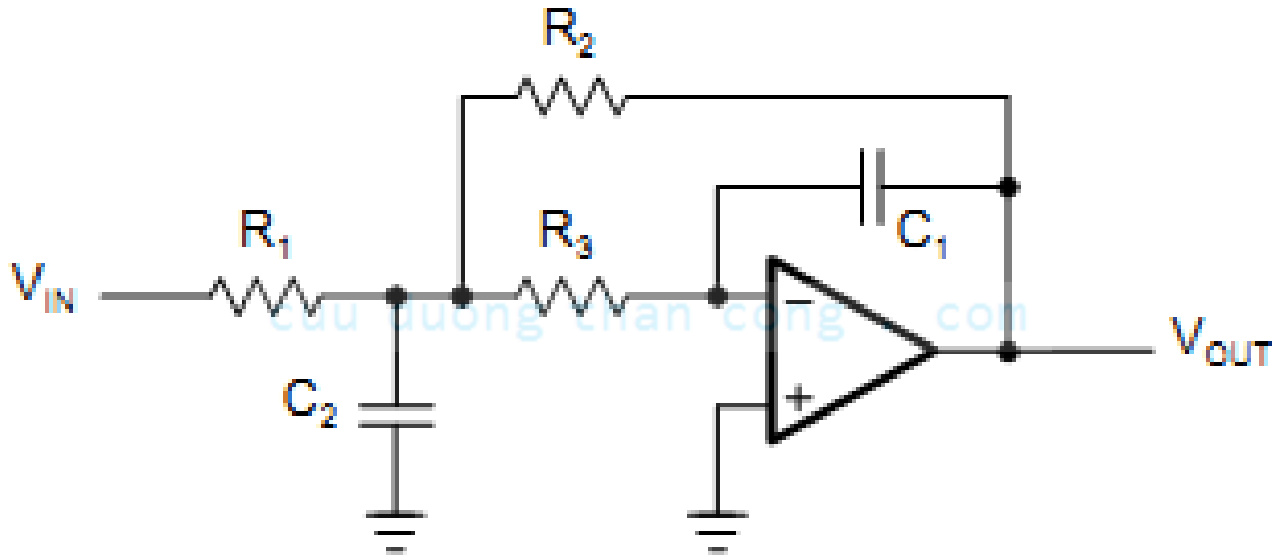

- Hàm truyền đưa về chuẩn hóa từ ω_c

$$-\frac{\frac{R_2}{R_1}}{1 + \omega_c C_1 \left(R_2 + R_3 + \frac{R_2 R_3}{R_1} \right) s + \omega_c^2 C_1 C_2 R_2 R_3 s^2}$$


Lọc thông cao

- Thay s bởi $1/s$
- Thay R bởi C và ngược lại

$$\frac{A_{\infty}}{\prod_i \left(1 + \frac{a_i}{s} + \frac{b_i}{s^2} \right)}$$


Lọc thông dải

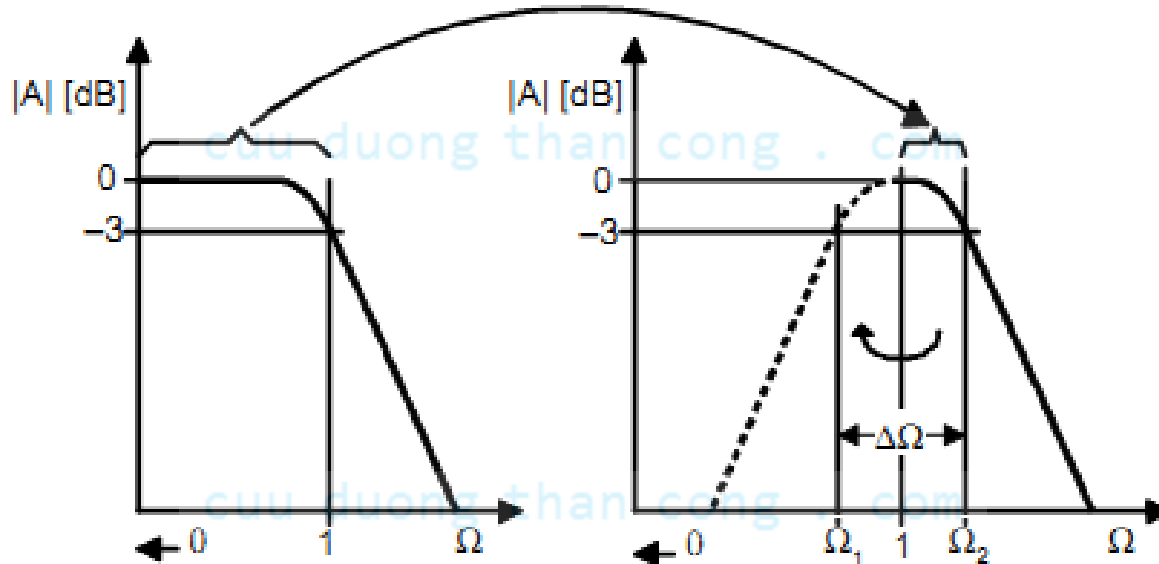- Thay s bởi $\frac{1}{\Delta\Omega} \left(s + \frac{1}{s} \right)$



- Nối tiếp lọc thông thấp với lọc thông cao

Lọc thông dải bậc 2

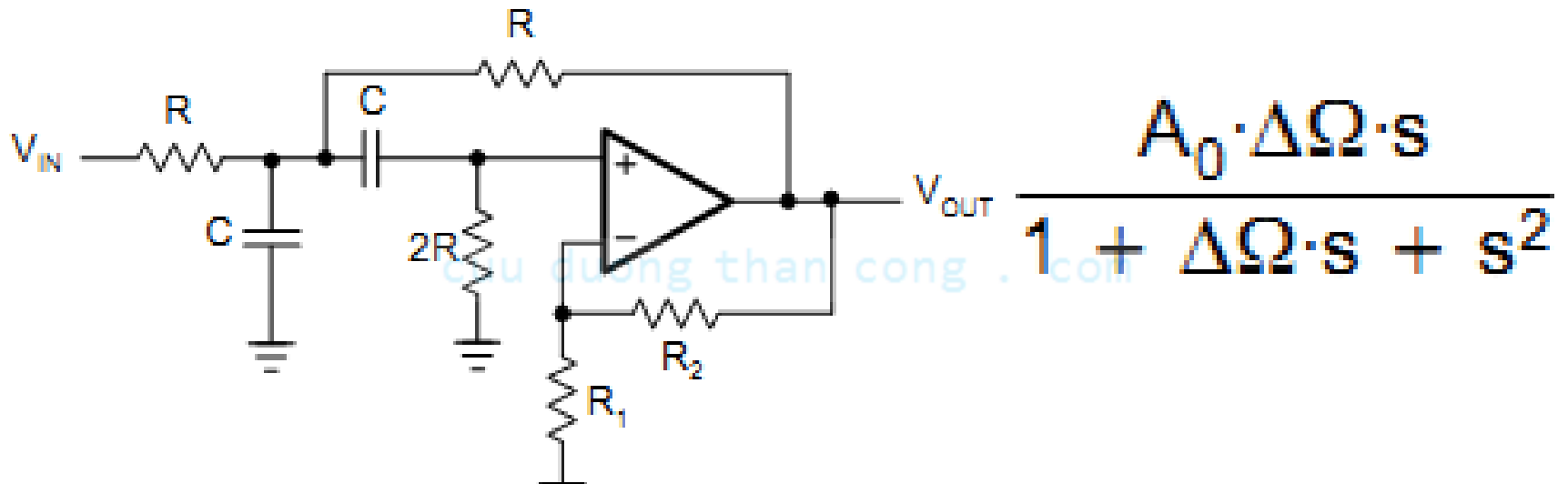


$$\frac{A_0 \cdot \Delta\Omega \cdot s}{1 + \Delta\Omega \cdot s + s^2}$$

$$\frac{G \cdot RC\omega_m \cdot s}{1 + RC\omega_m(3 - G) \cdot s + R^2C^2\omega_m^2 \cdot s^2}$$

$$f_m = \frac{1}{2\pi RC}$$

$$A_m = \frac{G}{3 - G}$$

$$G = 1 + \frac{R_2}{R_1}$$

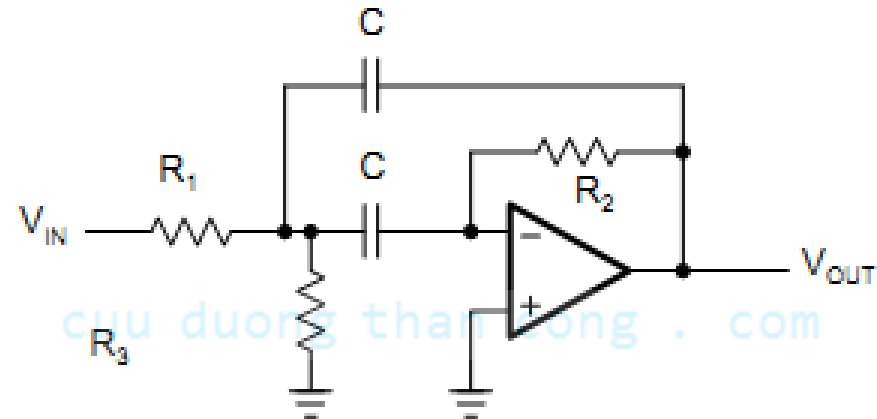


$$\frac{-\frac{R_2 R_3}{R_1 + R_3} C \omega_m \cdot s}{1 + \frac{2R_1 R_3}{R_1 + R_3} C \omega_m \cdot s + \frac{R_1 R_2 R_3}{R_1 + R_3} C^2 \cdot \omega_m^2 \cdot s^2}$$

$$f_m = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}} \quad -A_m = \frac{R_2}{2R_1} \quad B = \frac{1}{\pi R_2 C}$$


Bộ lọc chấn dãi

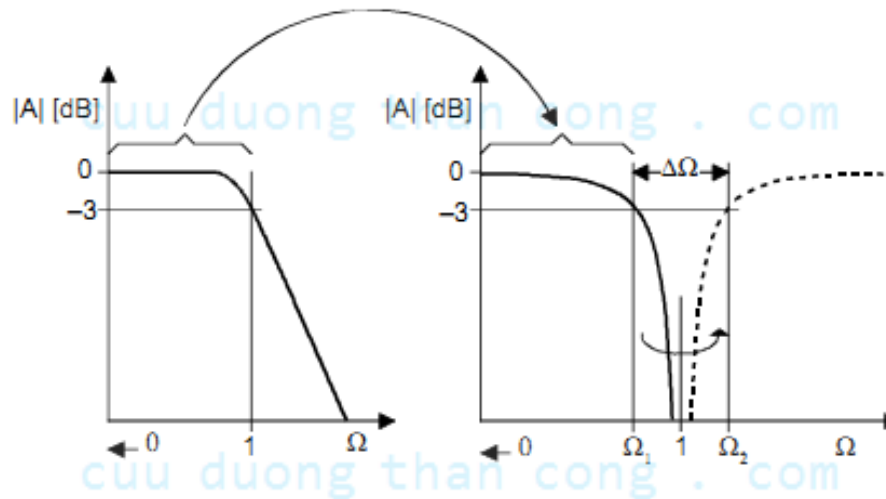- Thay s bởi $\frac{\Delta\Omega}{s + \frac{1}{s}}$



$$\frac{A_0(1 + s^2)}{1 + \Delta\Omega \cdot s + s^2}$$

Mạch lọc chấn dải cầu đôi T

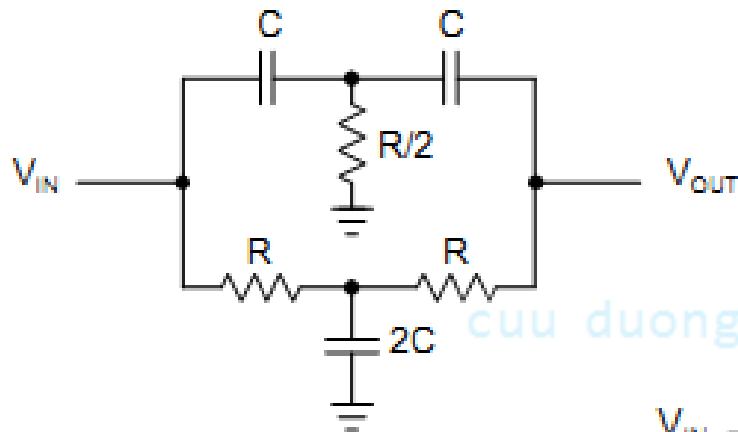


$$\frac{k(1 + s^2)}{1 + 2(2 - k) \cdot s + s^2}$$


$$f_m = \frac{1}{2\pi RC}$$

$$G = 1 + \frac{R_2}{R_1}$$


$$A_0 = G$$

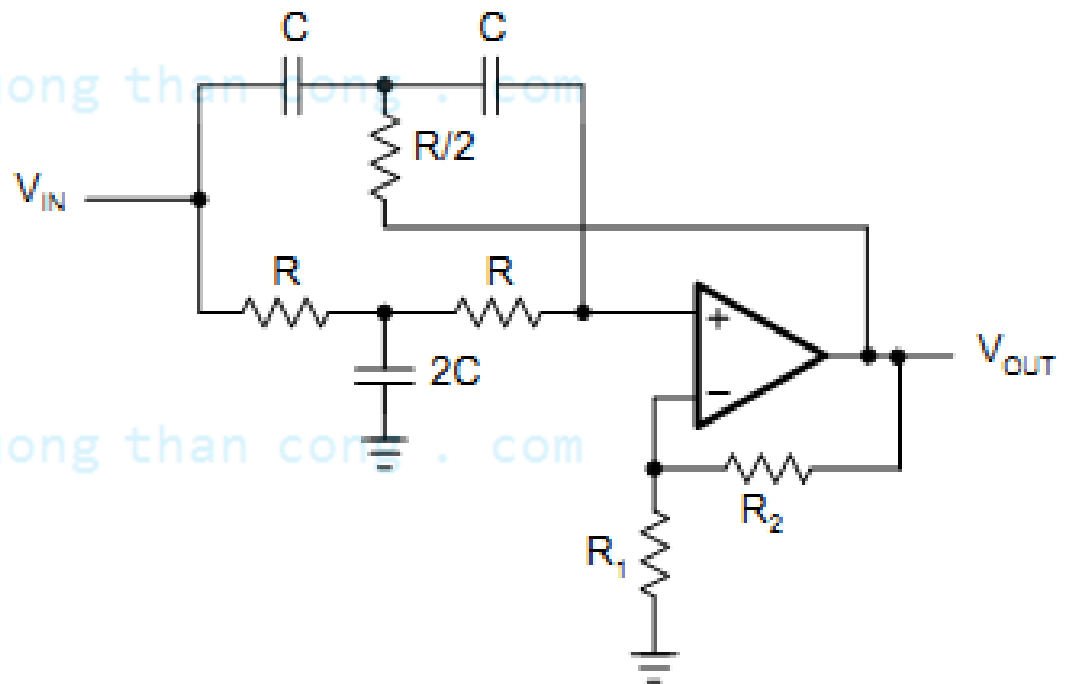

Mạch lọc chấn dải Wien-Robison

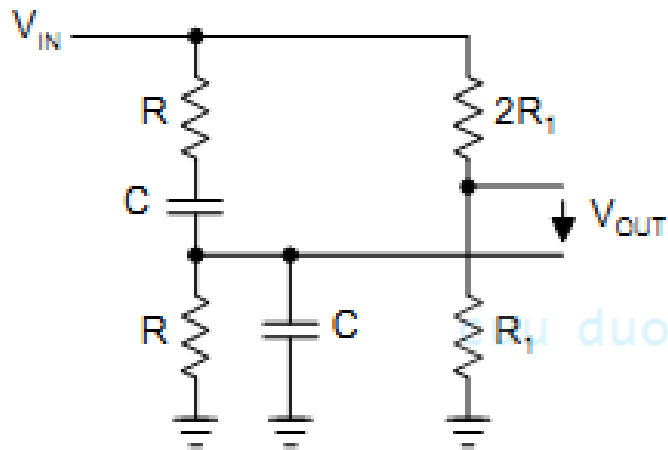
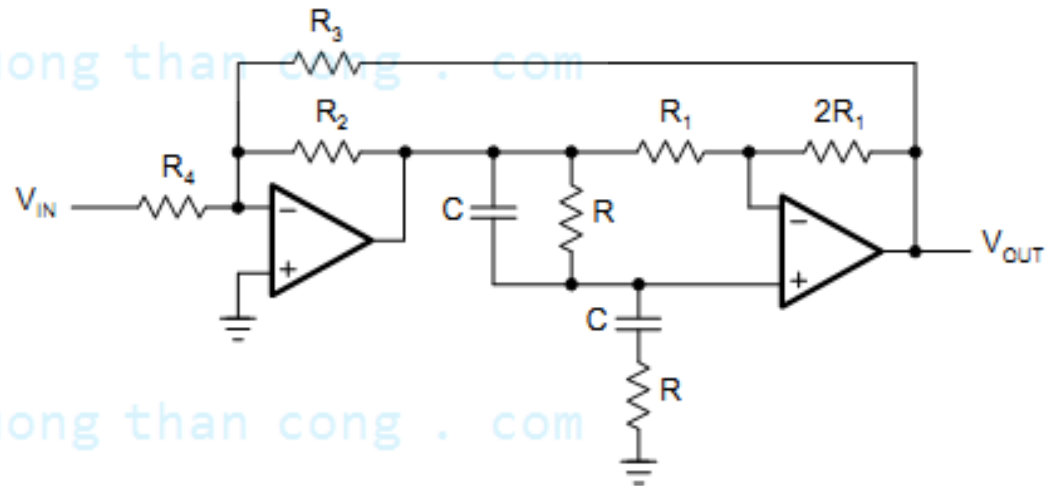
$$- \frac{\frac{\beta}{1+\alpha}(1+s^2)}{1 + \frac{3}{1+\alpha}s + s^2}$$



$$\alpha = \frac{R_2}{R_3}$$

$$\beta = \frac{R_2}{R_4}$$


$$f_m = \frac{1}{2\pi RC}$$

$$A_0 = - \frac{\beta}{1 + \alpha}$$

Mạch lọc toàn dải


$$\frac{\prod_i (1 - a_i s + b_i s^2)}{\prod_i (1 + a_i s + b_i s^2)}$$

cuu duong than cong . com

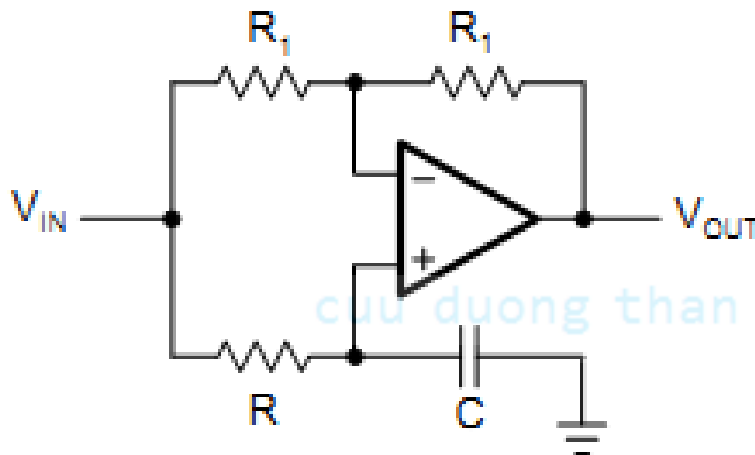


$$\frac{1 - RC\omega_c \cdot s}{1 + RC\omega_c \cdot s}$$

cuu duong than cong . com

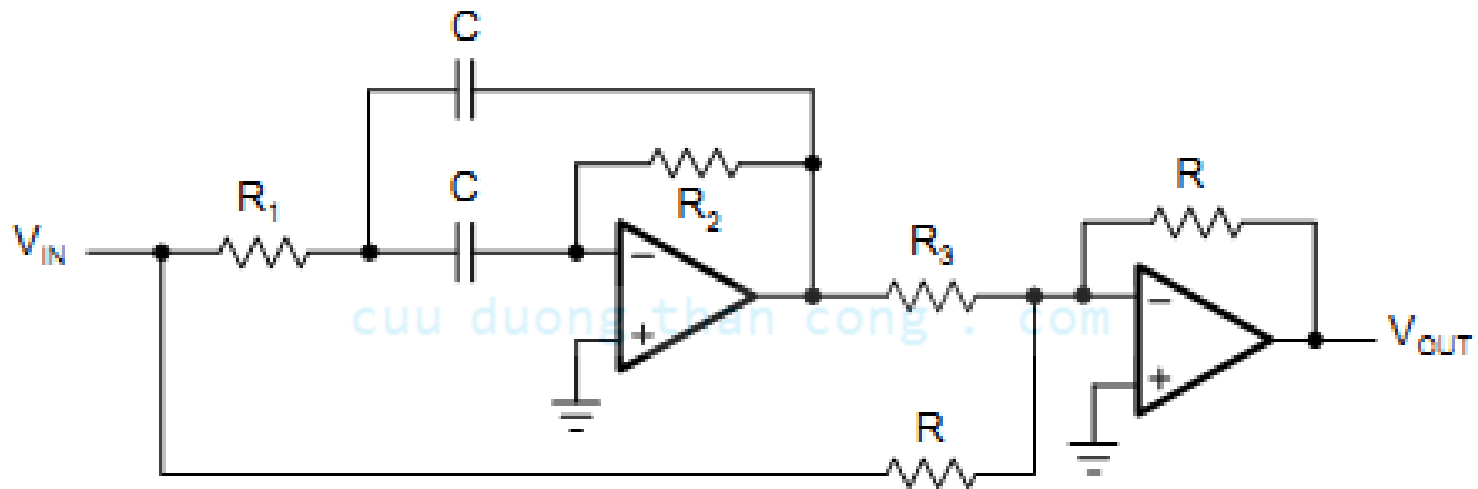

$$\frac{1 + (2R_1 - \alpha R_2)C\omega_c \cdot s + R_1 R_2 C^2 \omega_c^2 \cdot s^2}{1 + 2R_1 C\omega_c \cdot s + R_1 R_2 C^2 \omega_c^2 \cdot s^2}$$

Mạch lọc thông thấp thụ động

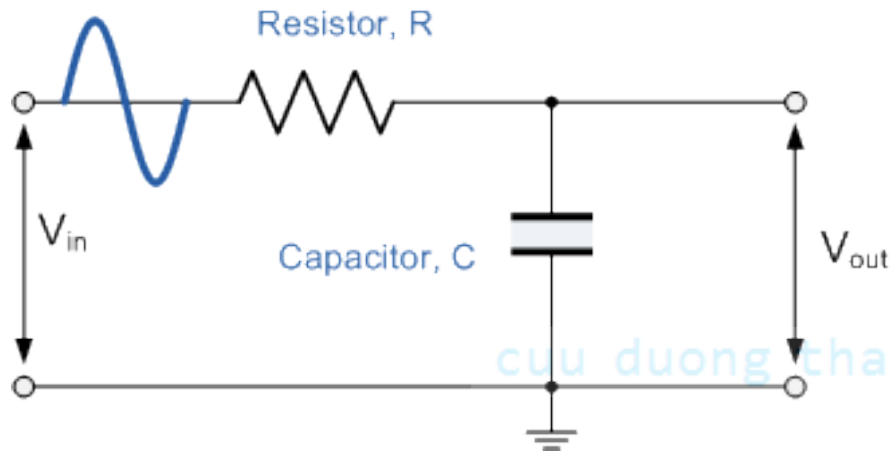


$$\frac{1}{1 + sRC}$$

$$f_c = \frac{1}{2\pi RC}$$





$$|A| = \frac{1}{\sqrt{1 + \Omega^2}}$$


$$\Omega = f/f_c$$

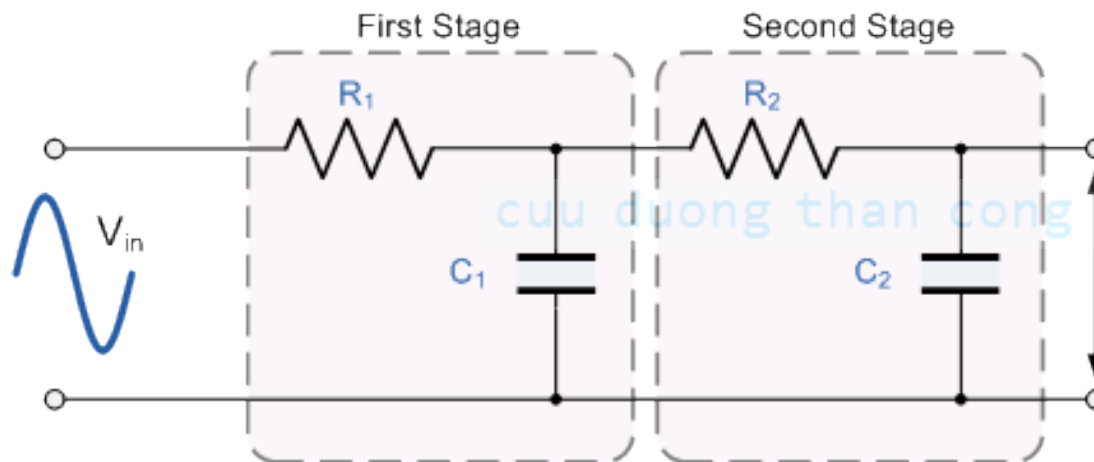


$$f_c = \frac{1}{4\pi\sqrt{R_1 C_1 R_2 C_2}} \text{ Hz}$$

Mạch lọc thông thấp tích cực

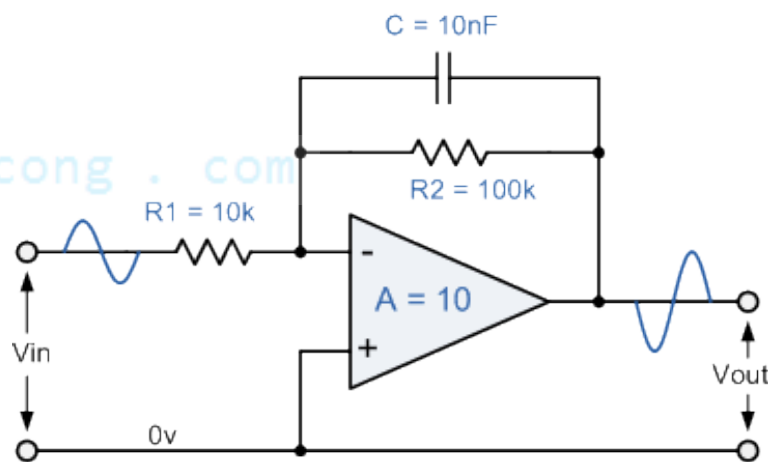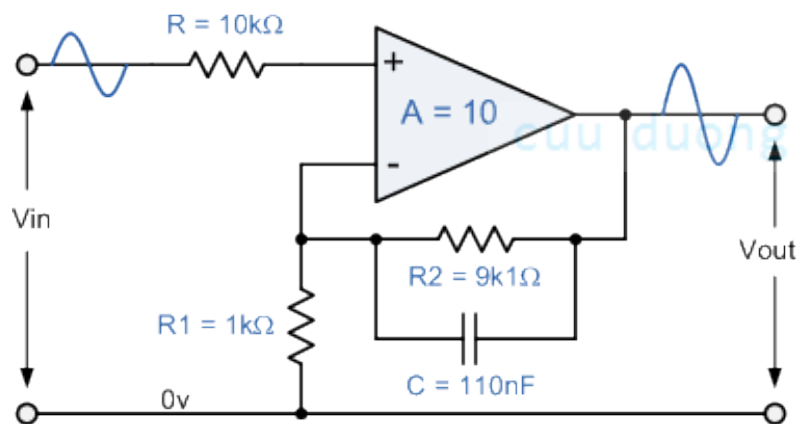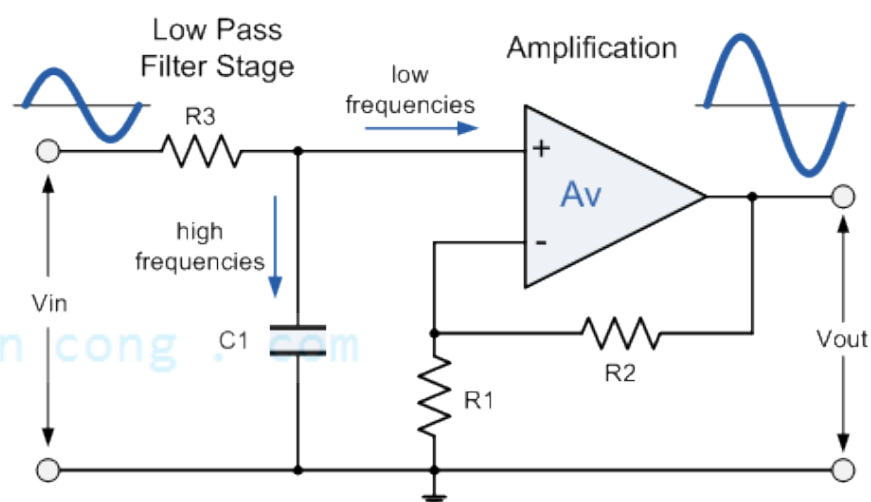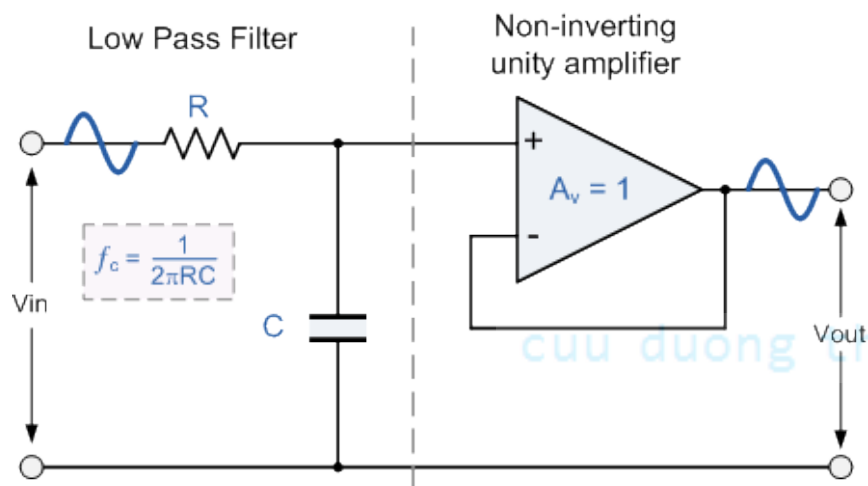

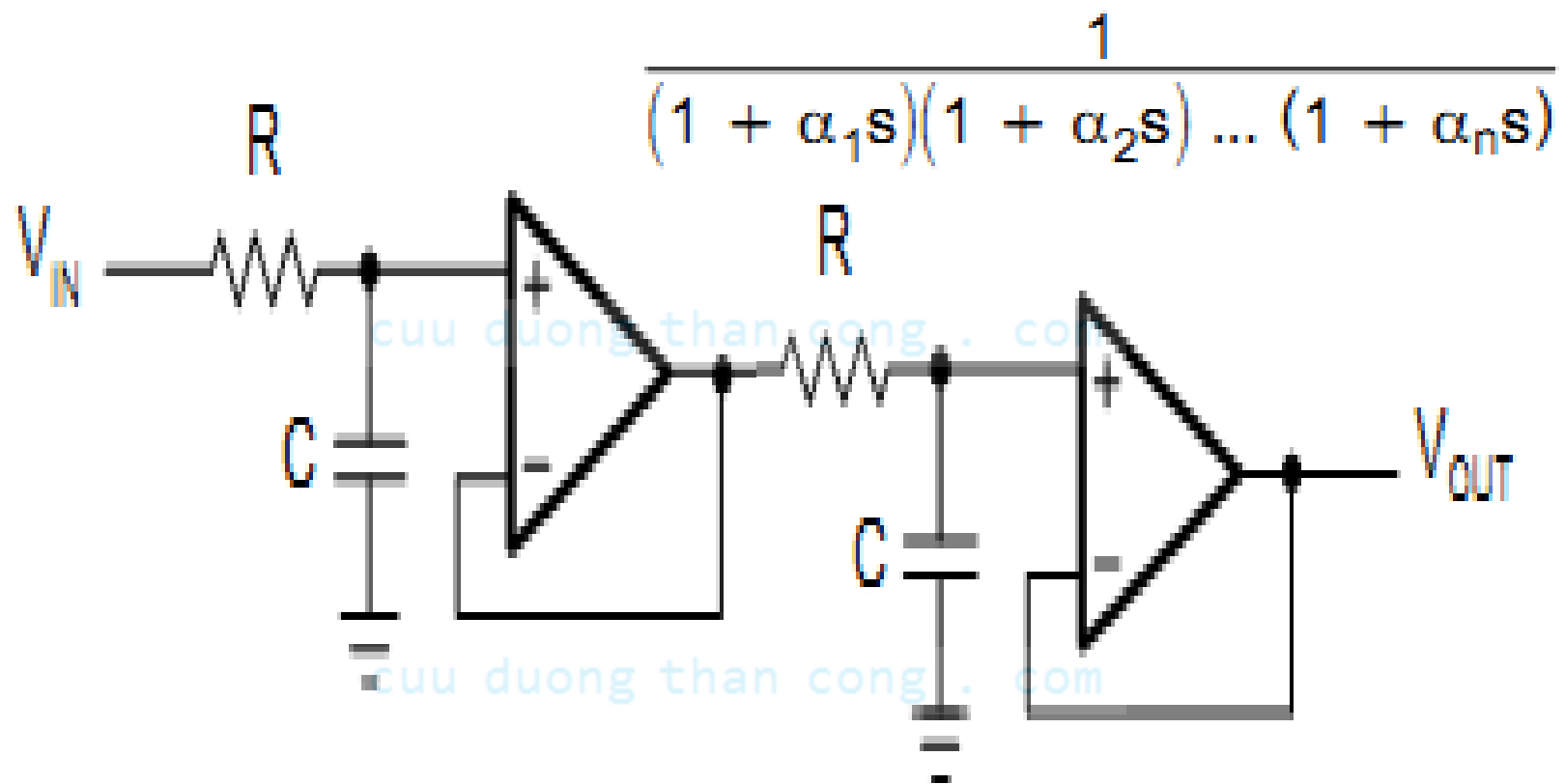

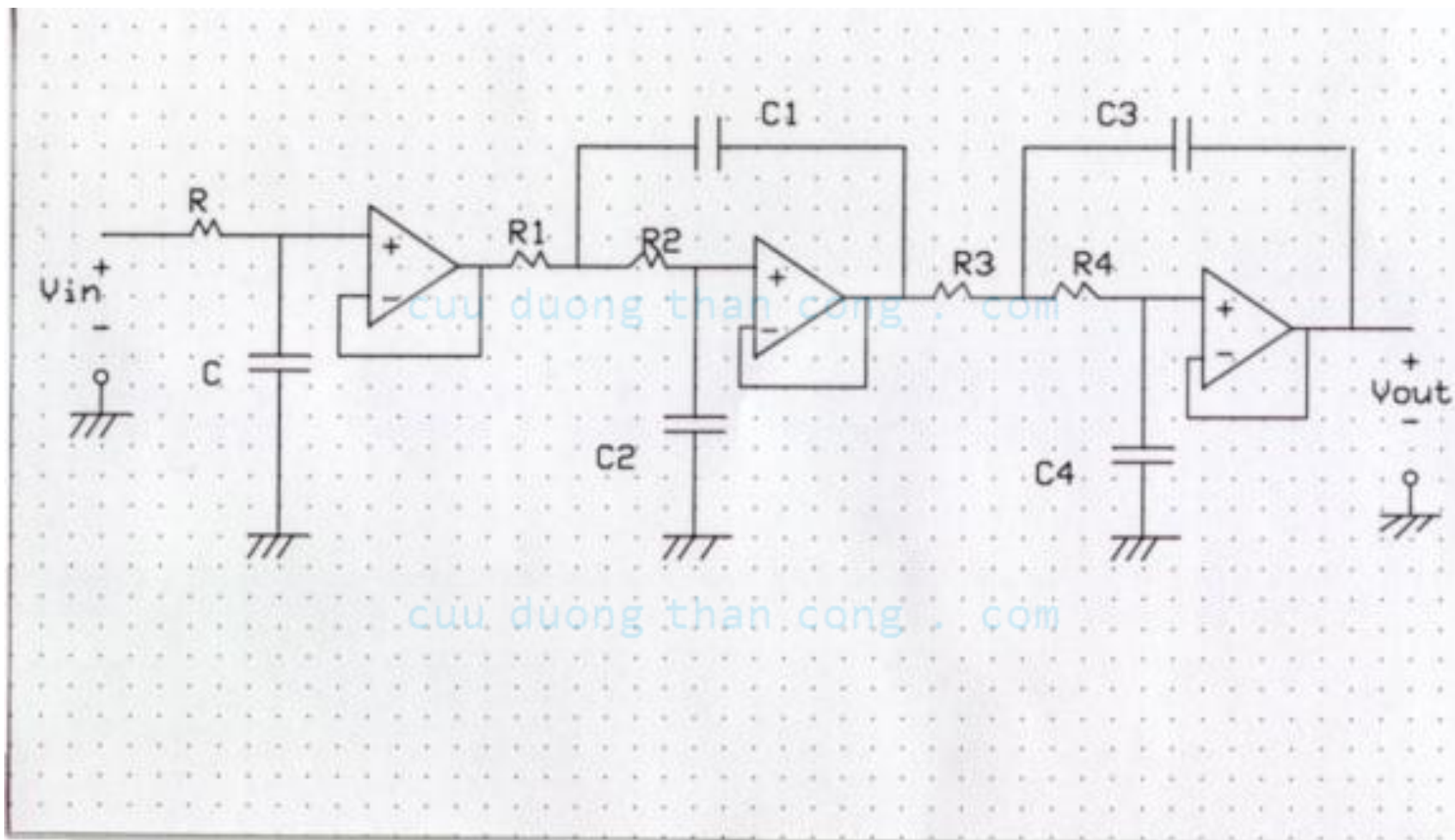
$$\alpha_1 = \alpha_2 = \dots \alpha_n = \alpha = \sqrt[3]{\sqrt{2} - 1}$$



Mạch lọc thông thấp tích cực (tt)


- Sallen & Key 2

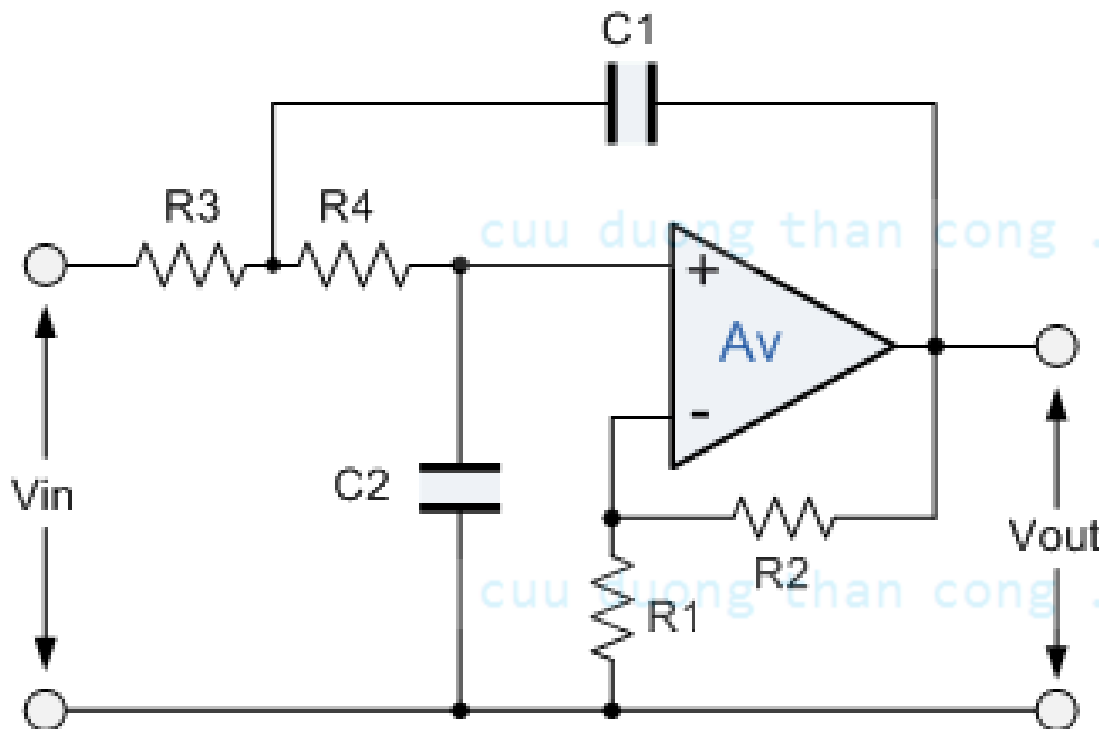

$$A_v = 1 + \frac{R_2}{R_1}$$
$$f_c = \frac{1}{2\pi \sqrt{R_3 R_4 C_1 C_2}}$$

$$H(s) = \frac{k\omega_0^2}{(s^2 + (\omega_0/Q)s + \omega_0^2)}$$


- Sallen & Key 3

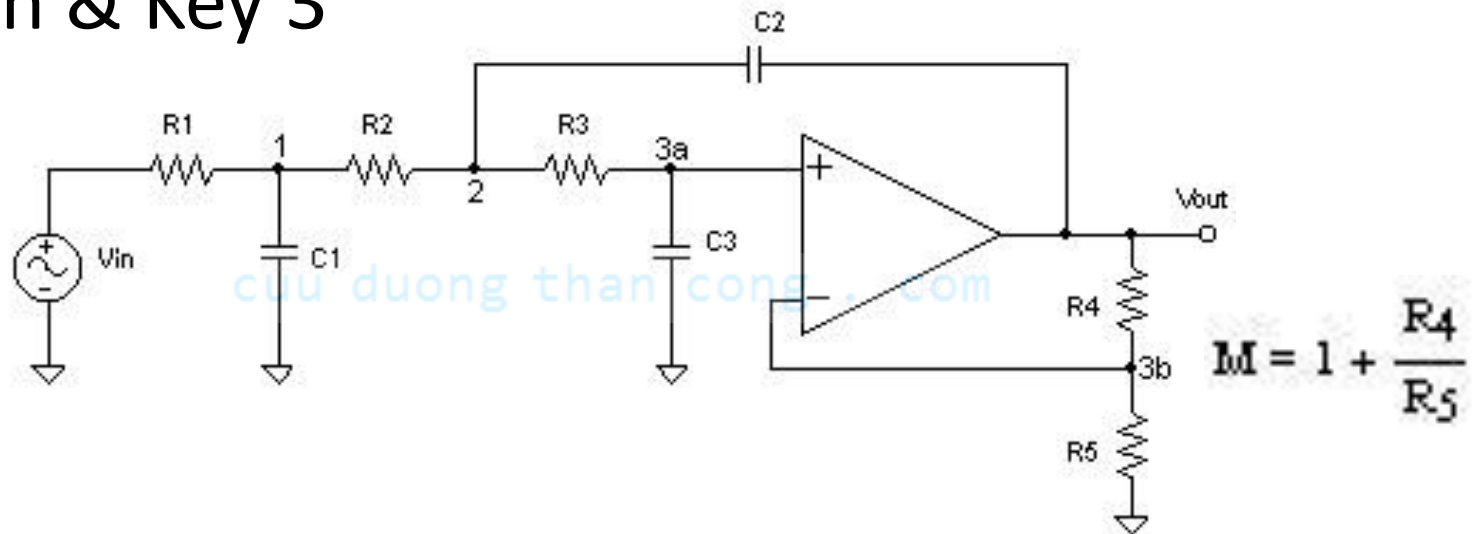

$$\frac{M}{R_1 \cdot R_2 \cdot R_3 \cdot C_1 \cdot C_2 \cdot C_3} \left[s^3 + \left(\frac{1}{R_1 \cdot C_1} + \frac{1}{R_2 \cdot C_1} + \frac{1}{R_2 \cdot C_2} + \frac{1-M}{R_3 \cdot C_3} + \frac{1}{R_3 \cdot C_2} \right) s^2 + \left[\frac{C_3 \cdot R_3 + R_1 \cdot C_3 + R_2 \cdot C_3 + C_1 \cdot R_1 + (1-M) \cdot (R_1 + R_2) \cdot C_2}{R_1 \cdot R_2 \cdot R_3 \cdot C_1 \cdot C_2 \cdot C_3} \right] s + \frac{1}{(R_1 \cdot R_2 \cdot R_3 \cdot C_1 \cdot C_2 \cdot C_3)} \right]$$



Bộ lọc thông thấp bậc 3

- Cauer

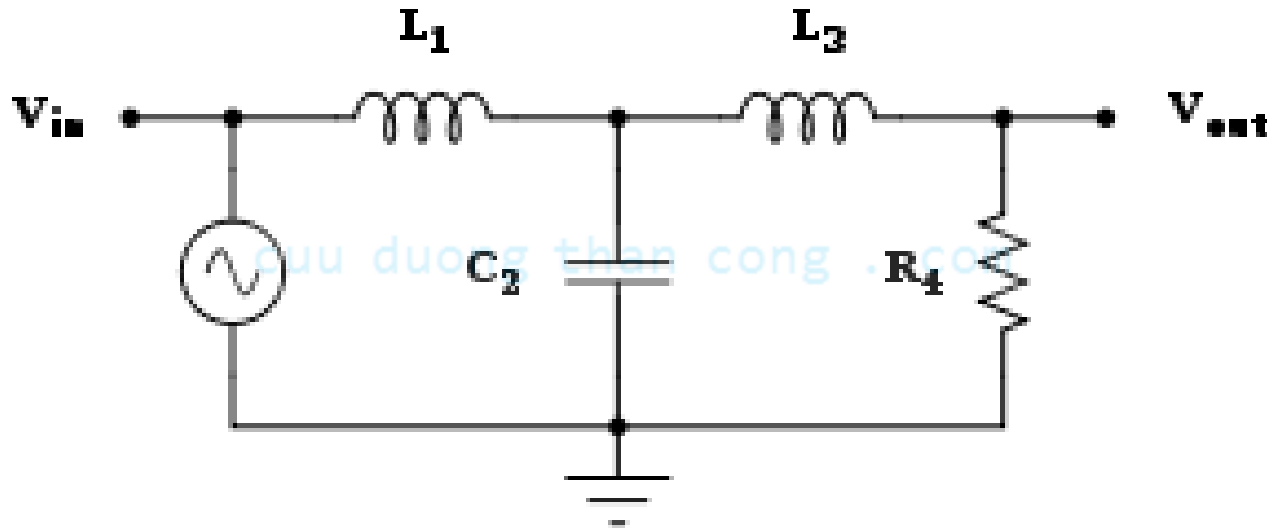


- The filter becomes a Butterworth filter with cutoff frequency $\omega_c=1$ when (for example) $C_2=4/3$ farad, $R_4=1$ ohm, $L_1=3/2$ henry and $L_3=1/2$ henry.


Mạch lọc thông cao thụ động

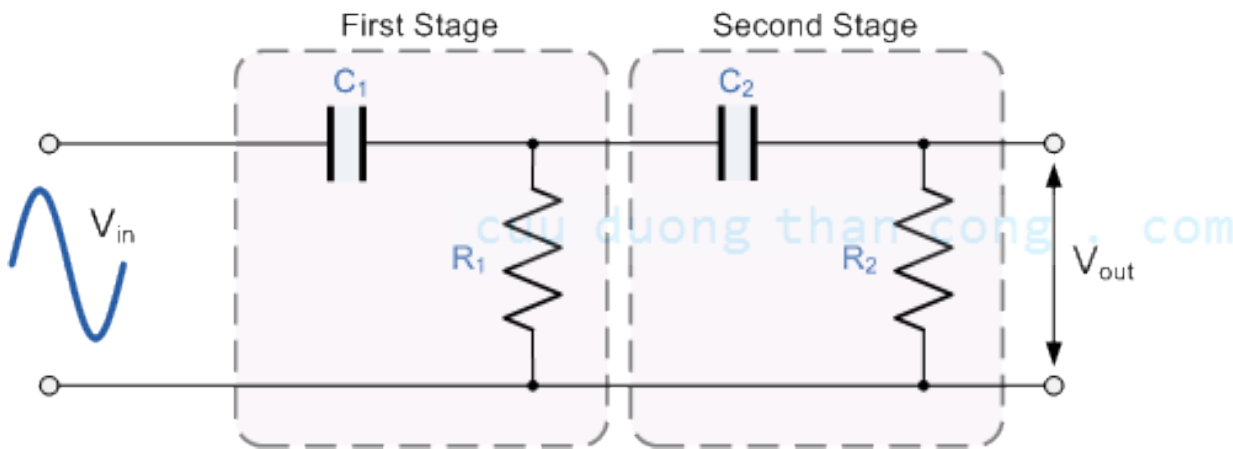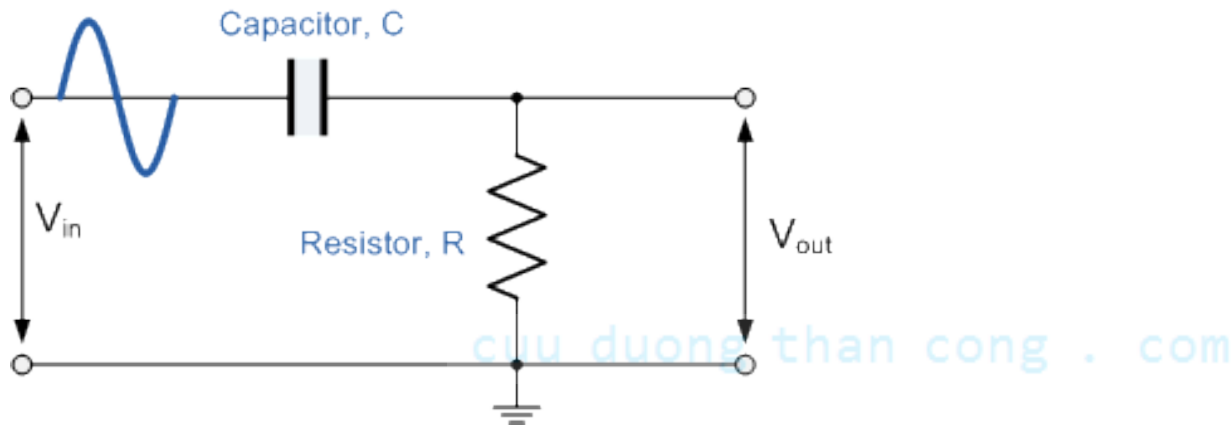

Mạch lọc thông cao tích cực

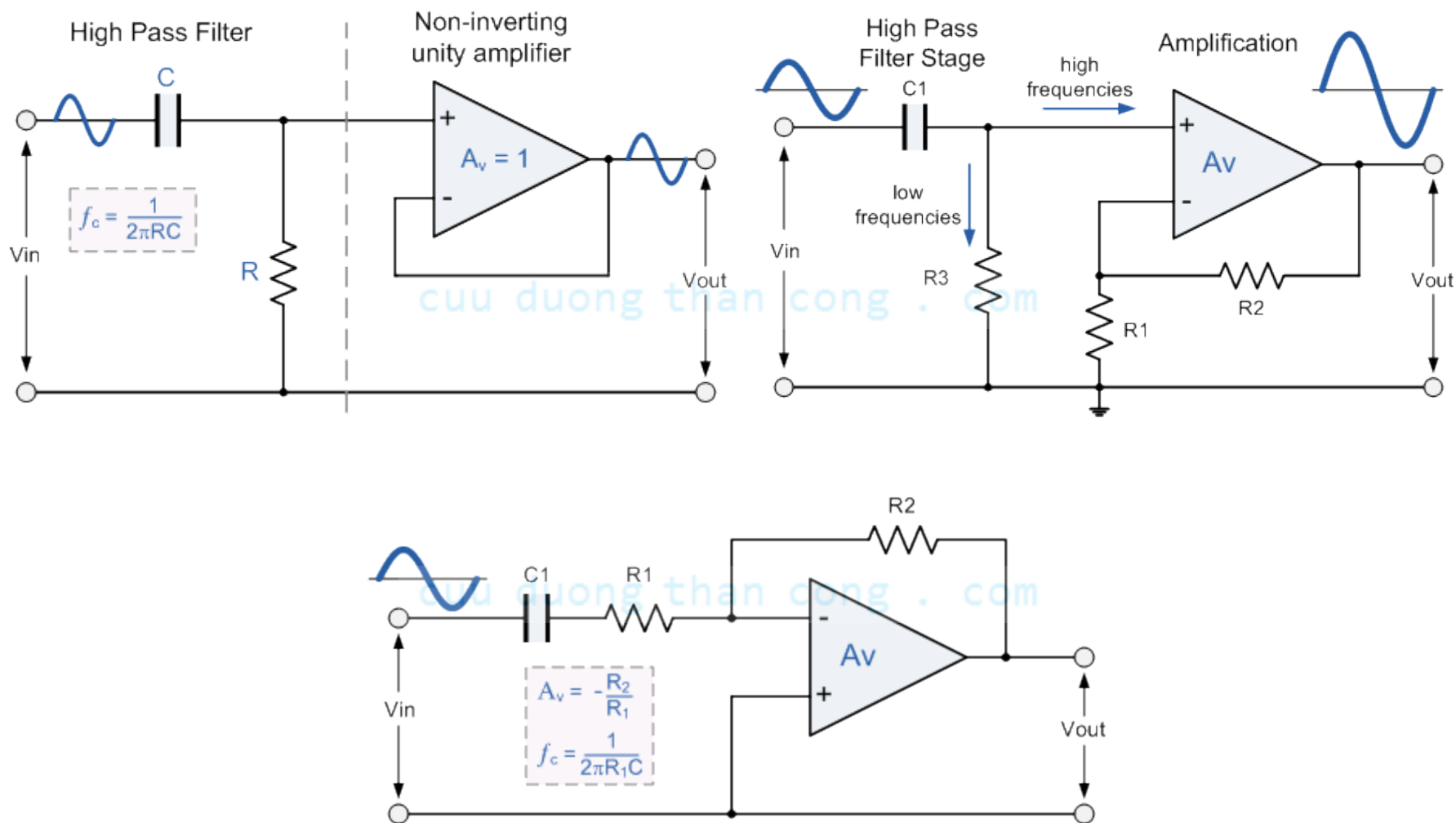


Mạch lọc thông cao tích cực (tt)

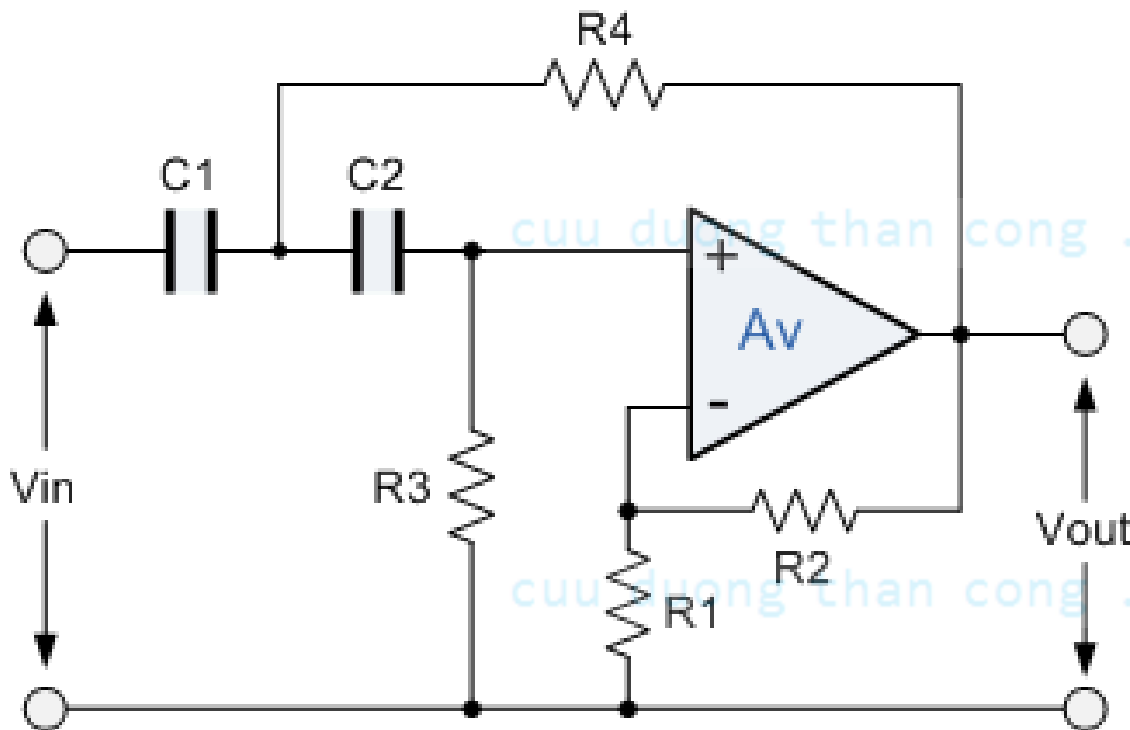


$$A_v = 1 + \frac{R_2}{R_1}$$
$$f_c = \frac{1}{2\pi \sqrt{R_3 R_4 C_1 C_2}}$$


Mạch lọc thông dải thụ động

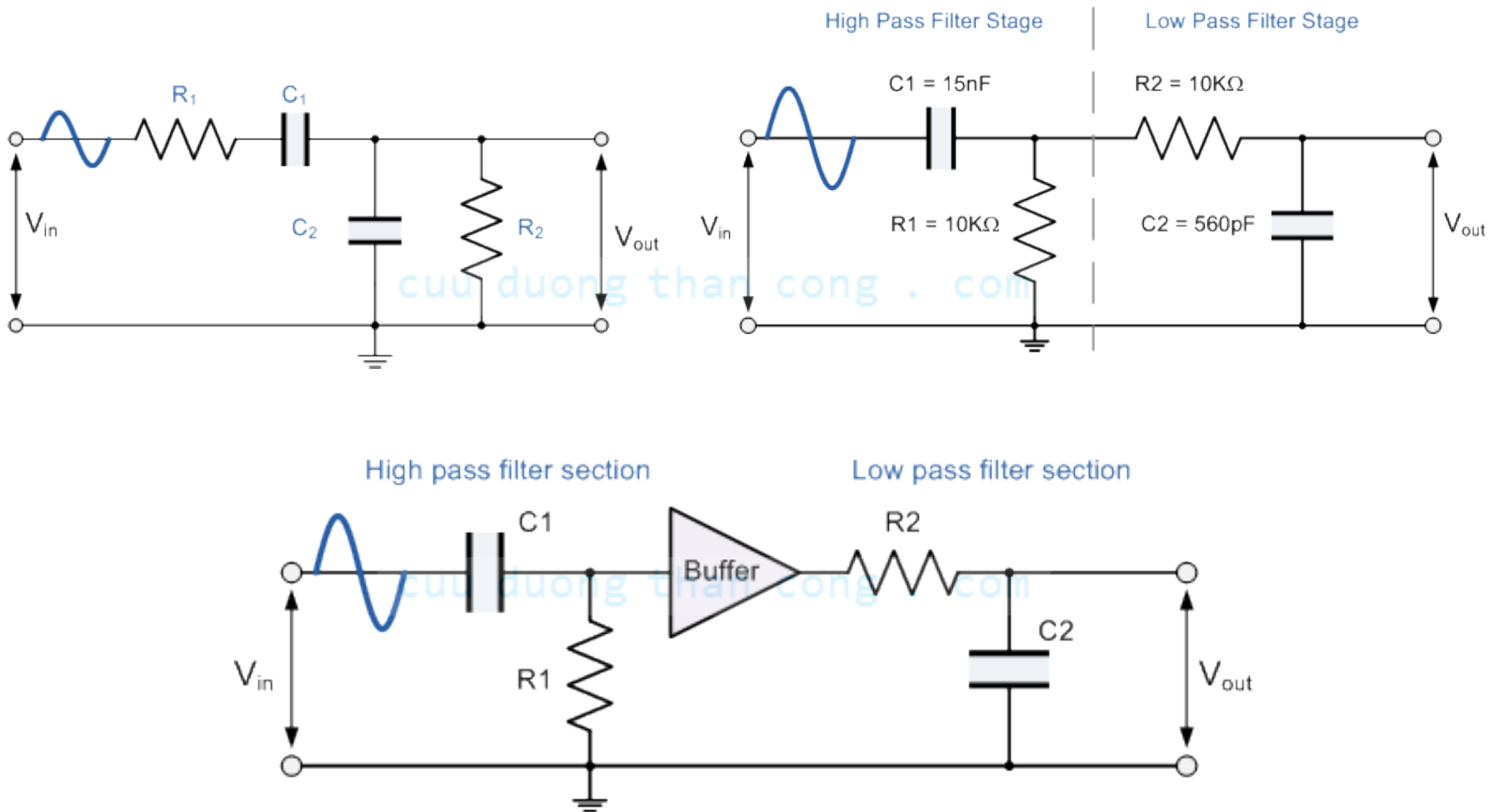

Mạch lọc thông dải tích cực

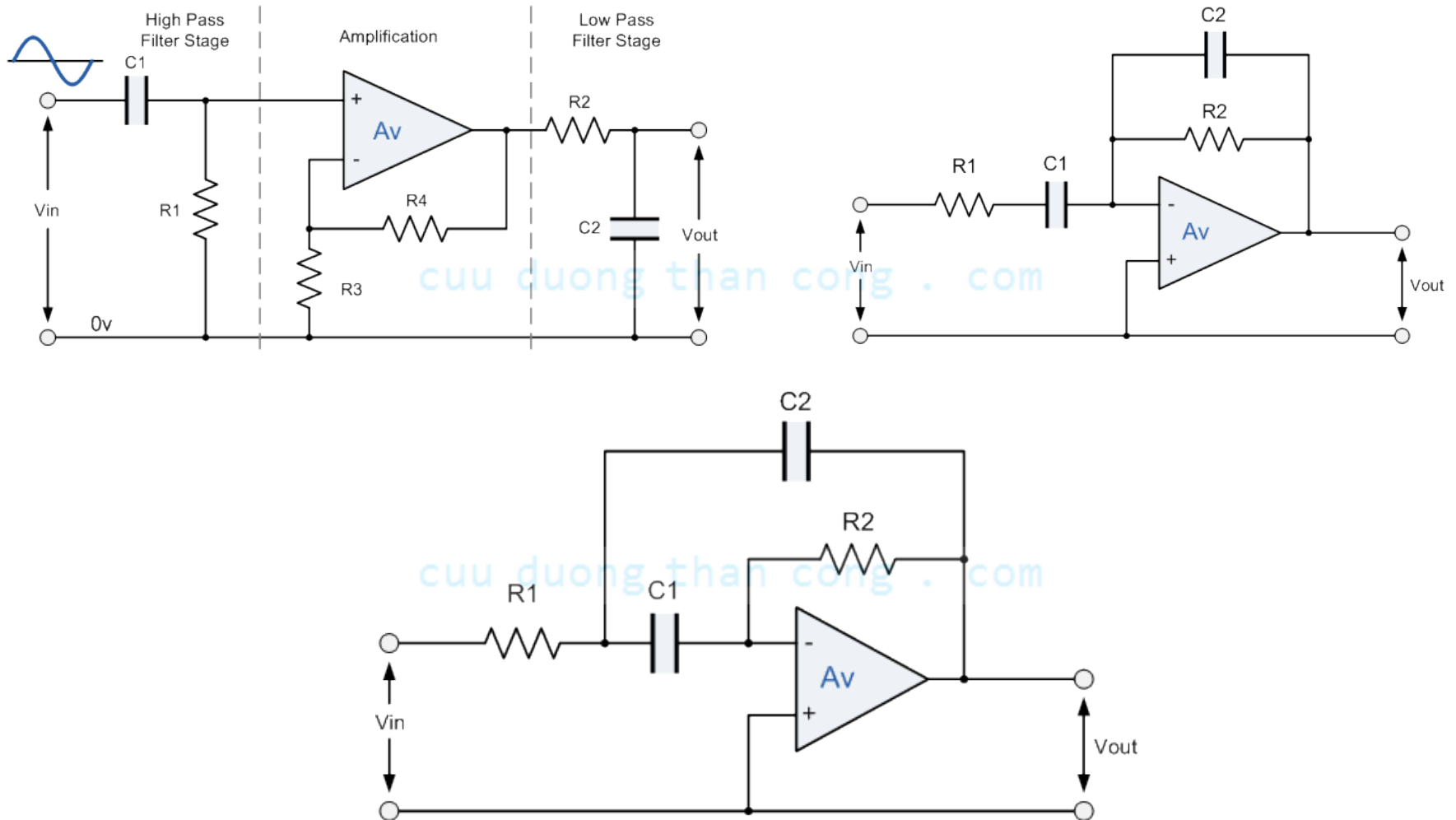




Bộ lọc biến trạng thái bậc 2

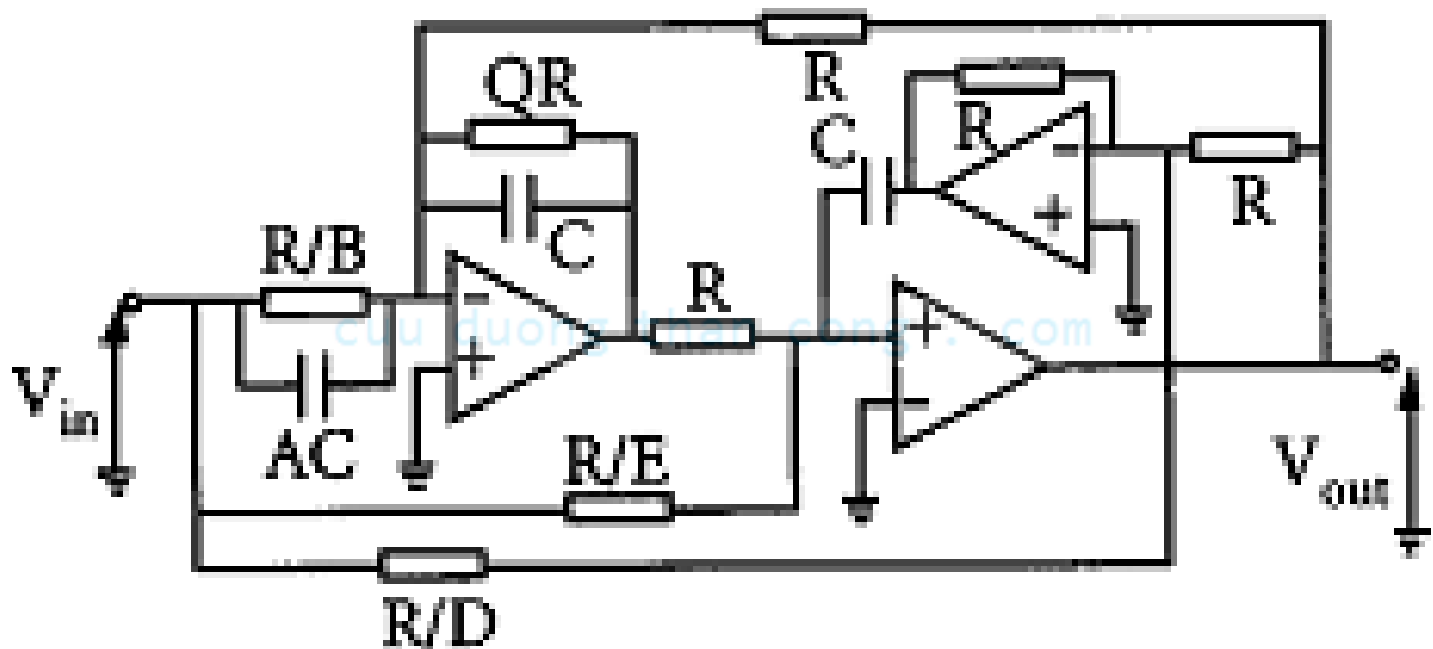

$$-\frac{As^2 + \omega_0(B - D)s + E\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \omega_0 \triangleq 1/RC$$

To transform a low-pass filter to high-pass, we first scale it to a cut-off frequency of 1 rad/s if it is not already at 1 rad/s. This allows a simple frequency rotation about 1 rad/s of $s \rightarrow 1/s$. All L 's become C 's, all C 's become L 's, and all values reciprocate. The cut-off frequency does not change.

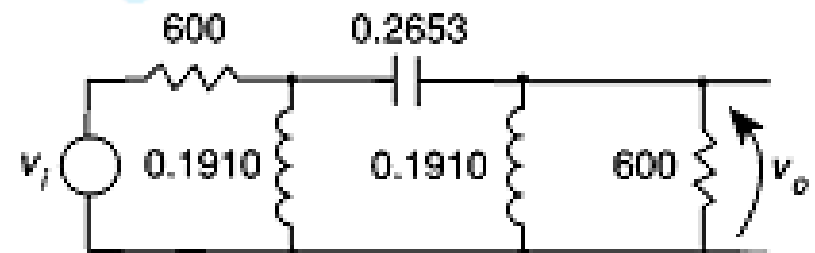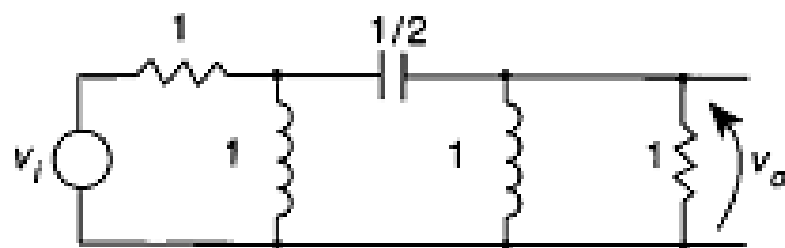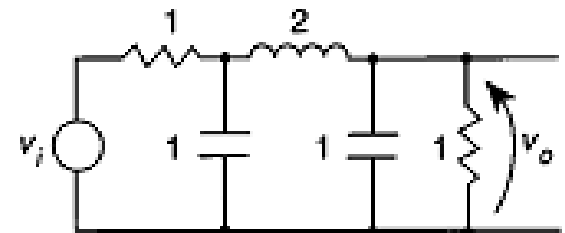Example 4.7. Design a third-order, high-pass Butterworth filter to operate from a $600\text{-}\Omega$ source to a $600\text{-}\Omega$ load with a cut-off frequency of 500 Hz.



To transform a low-pass filter to a bandpass filter we must first scale the low-pass filter so that the cut-off frequency is equal to the bandwidth of the normalized bandpass filter. The normalized center frequency of the bandpass filter is $\omega_0 = 1$ rad/s. Then we apply the transformation $s \rightarrow s + 1/s$. For an inductor

$$Z = Ls \text{ transforms to } Z = L \left(s + \frac{1}{s} \right)$$

For a capacitor

$$Y = Cs \text{ transforms to } Y = C \left(s + \frac{1}{s} \right)$$

The first step is then to determine the Q of the bandpass filter where

$$Q = \frac{f_0}{B} = \frac{\omega_0}{B_r}$$



(f_0 is the center frequency in Hz and B is the 3-dB bandwidth in Hz). Now we scale the low-pass filter to a cut-off frequency of $1/Q$ rad/s, then series tune every inductor, L , with a capacitor of value $1/L$ and parallel tune every capacitor, C , with an inductor of value $1/C$.

Example 4.8. Design a bandpass filter centered at 100 kHz having a 3-dB bandwidth of 10 kHz starting with a third-order Butterworth low-pass filter. The source and load resistors are each to be 600 Ω .

The Q required is

$$Q = \frac{100 \text{ kHz}}{10 \text{ kHz}} = 10, \text{ or } \frac{1}{Q} = 0.1$$

cuu duong than cong . com

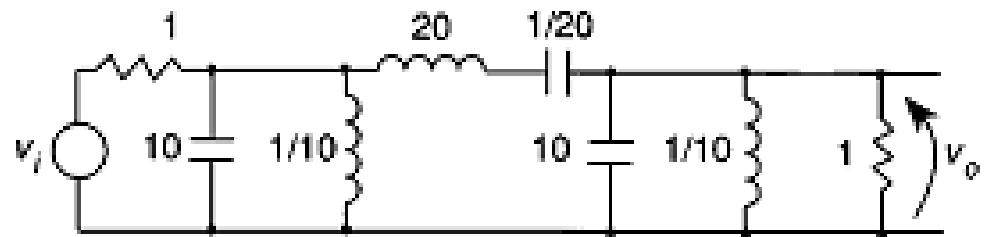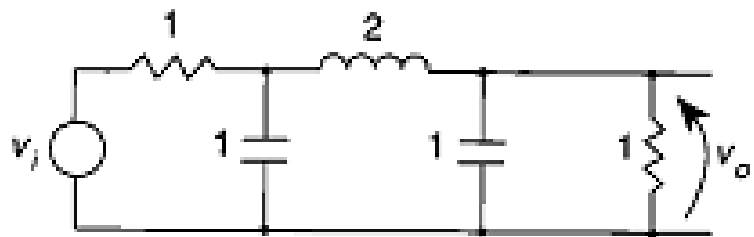

cuu duong than cong . com

