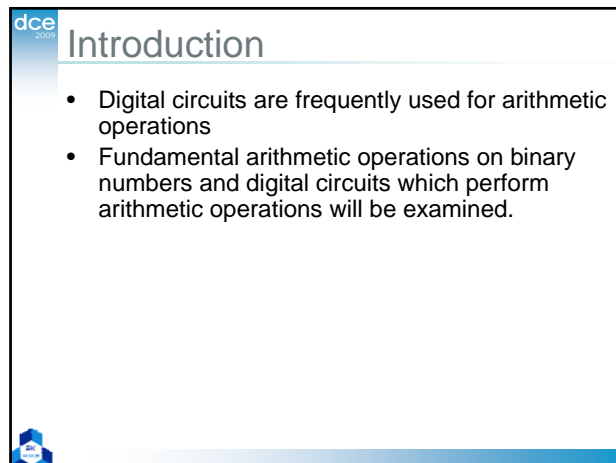


dce 2009

# Digital Logic Design 1

## Arithmetic


BK TP-HCM



dce 2009

# Introduction


- Digital circuits are frequently used for arithmetic operations
- Fundamental arithmetic operations on binary numbers and digital circuits which perform arithmetic operations will be examined.

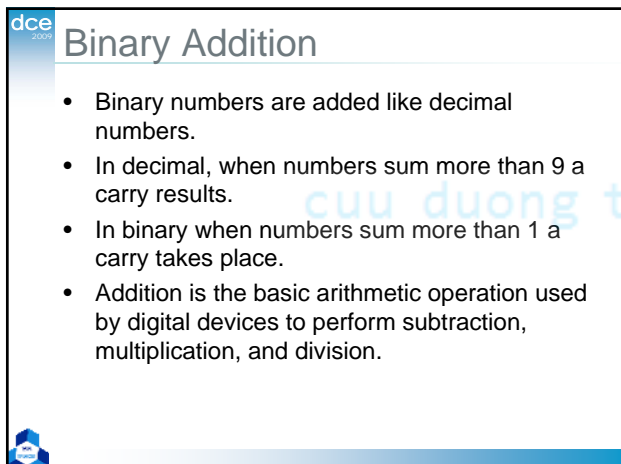

dce 2009

# Binary Addition

- Binary numbers are added like decimal numbers.
- In decimal, when numbers sum more than 9 a carry results.
- In binary when numbers sum more than 1 a carry takes place.
- Addition is the basic arithmetic operation used by digital devices to perform subtraction, multiplication, and division.

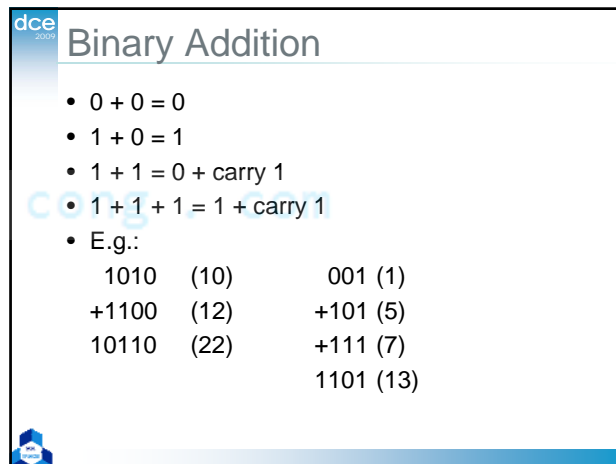


dce 2009

# Binary Addition

- $0 + 0 = 0$
- $1 + 0 = 1$
- $1 + 1 = 0 + \text{carry } 1$
- $1 + 1 + 1 = 1 + \text{carry } 1$
- E.g.:
 


1010	(10)	001	(1)
+1100	(12)	+101	(5)
10110	(22)	+111	(7)
		1101	(13)

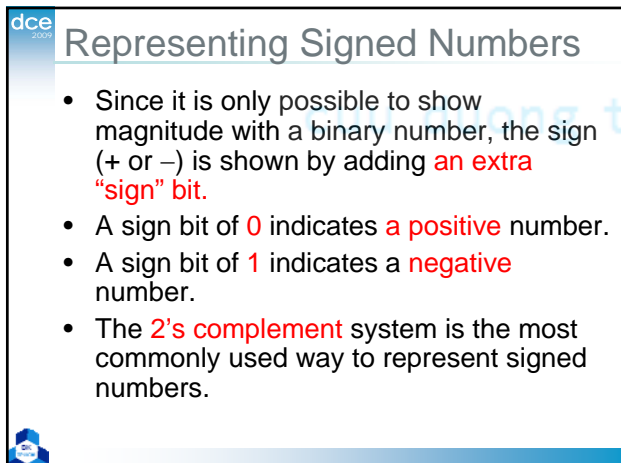

dce 2009

# Representing Signed Numbers

- Since it is only possible to show magnitude with a binary number, the sign (+ or -) is shown by adding an extra "sign" bit.
- A sign bit of 0 indicates a positive number.
- A sign bit of 1 indicates a negative number.
- The 2's complement system is the most commonly used way to represent signed numbers.

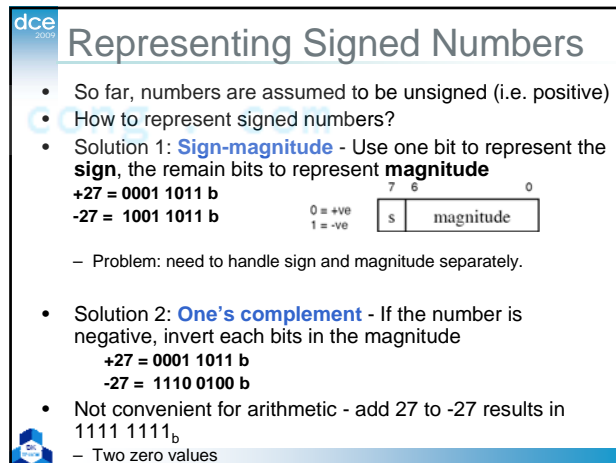

dce 2009

# Representing Signed Numbers

- So far, numbers are assumed to be unsigned (i.e. positive)
- How to represent signed numbers?
- Solution 1: **Sign-magnitude** - Use one bit to represent the **sign**, the remain bits to represent **magnitude**

7	6	0
s	magnitude	

+27 = 0001 1011 b  
-27 = 1001 1011 b

0 = +ve  
1 = -ve

– Problem: need to handle sign and magnitude separately.
- Solution 2: **One's complement** - If the number is negative, invert each bits in the magnitude
 

+27 = 0001 1011 b  
-27 = 1110 0100 b
- Not convenient for arithmetic - add 27 to -27 results in 1111 1111<sub>b</sub>

– Two zero values

dce  
2009

## Representing Signed Numbers

- Solution 3: **Two's complement** - represent negative numbers by taking its magnitude, invert all bits and add one:
  - Positive number      +27 = 0001 1011b
  - Invert all bits        1110 0100b
  - Add 1                -27 = 1110 0101b
- Unsigned number      

2<sup>7</sup> 2<sup>6</sup> 2<sup>0</sup>
- Signed 2's complement      

s

2<sup>7</sup> 2<sup>6</sup> 2<sup>0</sup>

$$x = -b_{N-1}2^{N-1} + b_{N-2}2^{N-2} + \dots + b_12^1 + b_02^0$$

dce  
2009

## Examples of 2's Complement

- A common method to represent -ve numbers:
  - use half the possibilities for positive numbers and half for negative numbers
  - to achieve this, let the MSB have a negative weighting
- Construction of 2's Complement Numbers
  - 4-bit example

Decimal	2's Complement (Signed Binary)			
	-8	+4	+2	+1
5	0	1	0	1
-5	1	0	1	1
7	0	1	1	1
-3	1	1	0	1

dce  
2009

## Why 2's complement representation?

- If we represent signed numbers in 2's complement form, subtraction is the same as addition to negative (2's complemented) number.

27 0001 1011 b

- 17 0001 0001 b

+ 10 0000 1010 b

+ 27 0001 1011 b

+ - 17 1110 1111 b

+ 10 0000 1010 b
- Note that the range for 8-bit unsigned and signed numbers are different.
- 8-bit unsigned: 0 ..... +255
- 8-bit 2's complement signed number: -128 ..... +127

dce  
2009

## Comparison Table

- Note the "wrap-around" effect of the binary representation
  - i.e. The top of the table wraps around to the bottom of the table

	Unsigned	Binary	2' comp
7	0111	7	
6	0110	6	
5	0101	5	
4	0100	4	
3	0011	3	
2	0010	2	
1	0001	1	
0	0000	0	
15	1111	-1	
14	1110	-2	
13	1101	-3	
12	1100	-4	
11	1011	-5	
10	1010	-6	
9	1001	-7	
8	1000	-8	

dce  
2009

## Representing Signed Numbers

- In order to change a binary number to 2's complement it must first be changed to 1's complement.
  - To convert to 1's complement, simply change each bit to its complement (opposite).
  - To convert 1's complement to 2's complement add 1 to the 1's complement.
- A positive number is true binary with 0 in the sign bit.
- A negative number is in 2's complement form with 1 in the sign bit.
- A number is negated when converted to the opposite sign.
- A binary number can be negated by taking the 2's complement of it.

dce  
2009

## Addition in the 2's Complement System

- Perform normal binary addition of magnitudes.
- The sign bits are added with the magnitude bits.
- If addition results in a carry of the sign bit, the carry bit is ignored.
- If the result is positive it is in pure binary form.
- If the result is negative it is in 2's complement form.

CuuDuongThanCong.com

Digital Logic Design 1

https://fb.com/tailieudientucntt

dce  
2009

### Addition in the 2's Complement System

- Perform normal binary addition of magnitudes.

+9 →  
+4 →

0 1 0 0 1  
0 0 1 0 0  
-----  
0 1 1 0 1 (+1)

↑  
Sign bit

+9 →  
-4 →

0 1 0 0 1  
1 1 1 0 0  
-----  
0 0 1 0 1 (+5)

↑  
Sign bit

-9 →  
+4 →

1 1 0 0 1  
0 0 1 0 0  
-----  
1 1 0 1 1 (-5)

↑  
Sign bit

-9 →  
-4 →

1 1 0 0 1  
1 1 1 0 0  
-----  
1 0 0 1 1 (-13)

↑  
Sign bit

+9 →  
-9 →

0 1 0 0 1  
1 0 1 1 1  
-----  
0 0 0 0 0 (0)

↑  
Sign bit

Don't care carry

dce  
2009

### Subtraction in the 2's Complement System

- The number subtracted (subtrahend) is negated.
- The result is added to the minuend.
- The answer represents the difference.
- If the answer exceeds the number of magnitude bits an overflow results.

+9 →  
+8 →

0 1 0 0 1  
0 1 0 0 0  
-----  
1 0 0 0 1

↑  
Sign bit

dce  
2009

### Multiplication

- In decimal, multiplying by 10 can be achieved by
  - shifting the number left by one digit adding a zero at the LS digit
- In binary, this operation multiplies by 2
- In general, left shifting by N bits multiplies by 2<sup>N</sup>
  - zeros are always brought in from the right-hand end
  - E.g.

Binary	Decimal
1101	13
11010	26
110100	52

dce  
2009

### Binary Division

- This is similar to decimal long division.
- It is simpler because only 1 or 0 are possible.
- The subtraction part of the operation is done using 2's complement subtraction.
- If the signs of the dividend and divisor are the same the answer will be positive.
- If the signs of the dividend and divisor are different the answer will be negative.

dce  
2009

### Summary of Signed and Unsigned Numbers

Unsigned	Signed
MSB has a positive value (e.g. +8 for a 4-bit system)	MSB has a negative value (e.g. -8 for a 4-bit system)
The carry-out from the MSB of an adder can be used as an extra bit of the answer to avoid overflow	To avoid overflow in an adder, need to sign extend and use an adder with one more bit than the numbers to be added
To increase the number of bits, add zeros to the left-hand side	To increase the number of bits, sign extend by duplicating the MSB
Complementing and adding 1 converts X to (2 <sup>N</sup> - X)	Complementing and adding 1 converts X to -X

dce  
2009

### BCD Addition

- When the sum of each decimal digit is less than 9, the operation is the same as normal binary addition.
- When the sum of each decimal digit is greater than 9, a binary 6 is added. This will always cause a carry.

47  
+35  
-----  
82

0100  
+ 0011  
-----  
0111

0111  
+ 1100  
-----  
10010

1

0111  
+ 0101  
-----  
1100

0110  
+ 0010  
-----  
10010

1

→ 47 BCD  
→ 35 BCD  
→ invalid  
→ + 6  
→ valid

CuuDuongThanCong.com

Digital Logic Design 1

https://fb.com/tailieudientucntt

## Hexadecimal Arithmetic

- Hex addition:
  - Add the hex digits in decimal.
  - If the sum is 15 or less express it directly in hex digits.
  - If the sum is greater than 15, subtract 16 and carry 1 to the next position.
- Hex subtraction – use the same method as for binary numbers.
- When the MSD in a hex number is 8 or greater, the number is negative. When the MSD is 7 or less, the number is positive.

## Arithmetic Circuits

- An arithmetic/logic unit (ALU) accepts data stored in memory and executes arithmetic and logic operations as instructed by the control unit.

## Arithmetic Circuits

- Typical sequence of operations:
  - Control unit is instructed to add a specific number from a memory location to a number stored in the accumulator register.
  - The number is transferred from memory to the B register.
  - Number in B register and accumulator register are added in the logic circuit, with sum sent to accumulator for storage.
  - The new number remains in the accumulator for further operations or can be transferred to memory for storage.

## Binary Addition

- Recall the binary addition process
 
$$\begin{array}{r} A \ 1001 \\ + B \ 0011 \\ \hline S \ 1100 \end{array}$$
- LS Column has 2 inputs 2 outputs
  - Inputs:  $A_0 \ B_0$
  - Outputs:  $S_0 \ C_1$
- Other Columns have 3 inputs, 2 outputs
  - Inputs:  $A_n \ B_n \ C_n$
  - Outputs:  $S_n \ C_{n+1}$
  - We use a "half adder" to implement the LS column
  - We use a "full adder" to implement the other columns
  - Each column feeds the next-most-significant column.

## Parallel Binary Adder

- The A and B variables represent 2 binary numbers to be added. The C variables are the carries. The S variables are the sum bits.

## Half Adder

- Truth Table
 

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
- Boolean Equations
 
$$S = \overline{A}B + A\overline{B} = A \oplus B$$

$$C = AB$$
- Implementation
- Note also XOR implementation possible for S

dce  
2009


### Full Adder

- Truth Table

Augend bit input	Addend bit input	Carry bit input	Sum bit output	Carry bit output
A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Boolean Equations
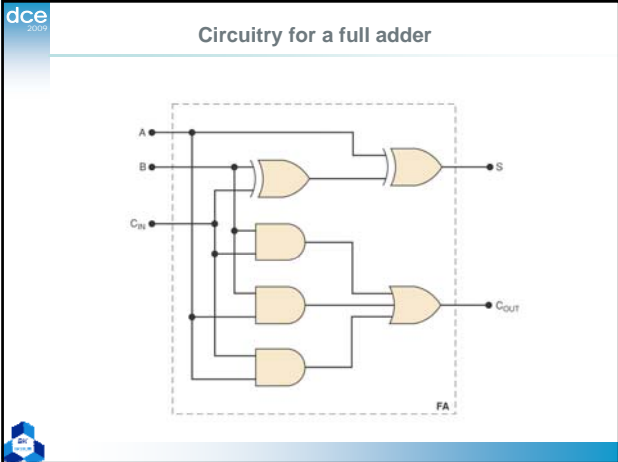
$$S = \overline{A}.\overline{B}.C_i + \overline{A}.B.\overline{C}_i + A.\overline{B}.\overline{C}_i + A.B.C_i$$
$$= A \oplus B \oplus C_i$$
$$C_o = \overline{A}BC_i + \overline{A}\overline{B}C_i + A\overline{B}\overline{C}_i + ABC_i$$
$$= AB + AC_i + BC_i$$
$$= AB + C_i(A + B)$$




dce  
2009

### Full Adder from Half Adders

- Truth Table

A	B	HA <sub>s</sub>	HA <sub>c</sub>	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0	0	0
0	0	0	0	1	1	0
0	1	1	0	0	1	0
0	1	1	0	1	0	1
1	0	1	0	0	1	0
1	0	1	0	1	0	1
1	1	0	1	0	0	1
1	1	0	1	1	1	1


- Boolean Equations

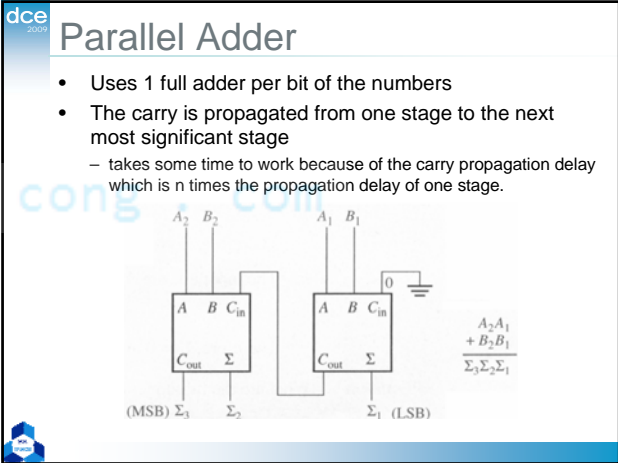

dce  
2009

### Complete Parallel Adder With Registers

- Register notation – to indicate the contents of a register we use brackets:
  - [A]=1011 is the same as A<sub>3</sub>=1, A<sub>2</sub>=0, A<sub>1</sub>=1, A<sub>0</sub>=1
- A transfer of data to or from a register is indicated with an arrow
  - [B]→[A] means the contents of register B have been transferred to register A.
- Eg.: 1001 + 0101 using the parallel adder:
  - t1 : A CLR pulse is applied
  - t2 : 1001 from mem→ B
  - t3 : 1001 + 0000 → A
  - t4 : 0101 from mem→ B
  - t5 : The sum outputs → A
  - The sum of the two numbers is now present in the accumulator.

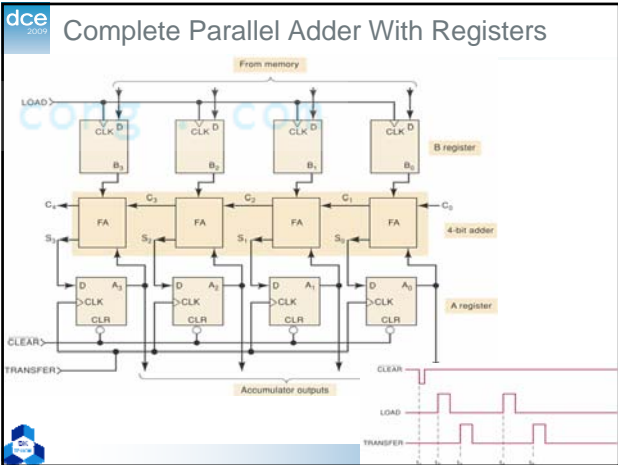

dce2009

### Carry Propagation

- Parallel adder speed is limited by carry propagation (also called **carry ripple**).
- Carry propagation results from having to wait for the carry bits to “ripple” through the device.
- Additional bits will introduce more delay.
- Various techniques have been developed to reduce the delay. The **look-ahead carry** scheme is commonly used in high speed devices.

dce2009

### Integrated Circuit Parallel Adder

- The most common parallel adder is a 4 bit device with 4 interconnected FAs and look-ahead Carry circuits.
- Parallel adders may be cascaded together as shown to add larger numbers

dce2009

### Parallel adder used to add and subtract numbers in 2's-complement system

dce2009

### 2's Complement Addition using 1's Complement Operands

Parallel adder used to perform subtraction ( $A - B$ ) using the 2's-complement system. The bits of the subtrahend ( $B$ ) are inverted (1's complement), and  $C_0 = 1$  to produce the 2's complement

dce2009

### Parallel adder/subtractor using the 2's-complement system

ADD = 1, SUB = 0:  
B register passes to adder and Carry in = 0

ADD = 0, SUB = 1:  
Complement of B register passes to adder and Carry in = 1

dce2009

### ALU Integrated Circuits

S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Operation	Comments
0	0	0	CLEAR	F <sub>3</sub> F <sub>2</sub> F <sub>1</sub> F <sub>0</sub> = 0000
0	0	1	B minus A	Needs C <sub>n</sub> = 1
0	1	0	A minus B	Needs C <sub>n</sub> = 0
0	1	1	A plus B	
1	0	0	A ⊕ B	Exclusive-OR
1	0	1	A + B	OR
1	1	0	AB	AND
1	1	1	PRESET	F <sub>3</sub> F <sub>2</sub> F <sub>1</sub> F <sub>0</sub> = 1111

Notes: S inputs select operation.  
OVR = 1 for signed-number overflow.

- ALUs can perform different arithmetic and logic functions as determined by a binary code on the function select inputs.

