 


## Multiplexing and Multiplexer

- Multiplexers are circuits which select one of many inputs
- In here, we assume that we have one-bit inputs (in general, each input may have more than one bit)
- Suppose we have eight inputs: I0, I1, I2, I3, I4, I5, I6, I7
- We want one of them to be output based on selection signals
- 3 bits of selection signals to decide which input goes to output
- Note the order of selection signals
  - X is MSB and Z is LSB



X	Y	Z	F
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7


CprE 210

Lec 15

1
 
## Multiplexer Implementation

- We can write a logic expression for output F as follows
 
$$F = X'Y'Z'I_0 + X'Y'Z'I_1 + X'Y'Z'I_2 + X'Y'Z'I_3 + X'Y'Z'I_4 + X'Y'Z'I_5 + X'Y'Z'I_6 + X'Y'Z'I_7$$
- This circuit can be implemented using
  - eight 4-input AND gates and one 8-input OR gates




X	Y	Z	F
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7

CprE 210

Lec 15

2

## Implementing 4-to-1 MUX using 2-to-1 MUXs

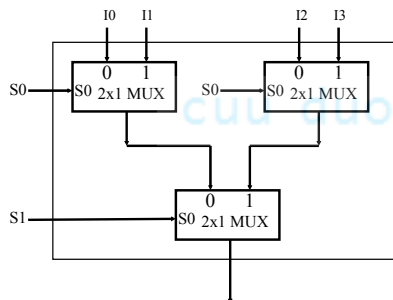

CprE 210


Lec 15

3

## Making a 2-bit 4-to-1 Multiplexer

- Four 2-bit inputs A, B, C, D
- One 2-bit output F
- Two bits of selection signal X Y

X	Y	F
0	0	A
0	1	B
1	0	C
1	1	D

 


CprE 210

Lec 15

4
 
## Synthesis of Logic Functions using Multiplexers

- Multiplexers can be directly used to implement a function
- Easiest way is to use function inputs as selection signals
- Input to multiplexer is a set of 1s and 0s depending on the function to be implemented
- We use a 8-to-1 multiplexer to implement function F
- Three select signals are X, Y, and Z, and output is F
- Eight inputs to multiplexer are 1 0 1 0 1 1 0 0
- Depending on the input signals
  - multiplexer will select proper output



X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

CprE 210


Lec 15

5

## Implementing 3-variable functions with 4x1 MUX

- Divide the outputs into 4 groups based on X and Y.
- Write the outputs as a function of Z
- There are only 4 possibilities:  $F=Z$ ,  $F=Z'$ ,  $F=0$ ,  $F=1$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

CprE 210

Lec 15

6

### Implementing 4-variable functions with 8x1 MUX

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$F=D$

$F=D$

$F=D'$


$F=0$

$F=0$

$F=D$

$F=1$

$F=1$

 

CprE 210

Lec 15

7

### Implementing 4-variable functions with 4x1 MUX


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$F=D$

$F=C'D'$

$F=CD$

$F=1$

 

CprE 210

Lec 15

8

### Implementing 4-variable functions with 4x1 MUX

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$F=$

$F=$


$F=$

$F=$

$F=$

$F=$

$F=$

 

CprE 210

Lec 15

9

### Definition of Decoder

- Suppose we have  $n$  input bits (which can represent up to  $2^n$  distinct elements of coded information).
- We need a device that allows us to select which of the  $2^n$  elements, devices, memory locations, etc. is being selected.
- In general:
  - A decoder has  $n$  input bits
  - A decoder has  $2^n$  (or less) output bits
  - As a rule, all but one of the outputs is zero (deselected) at any time (called *one-hot encoded*)

CprE 210


Lec 15

10

### 2-to-4 Decoder

- The 2-to-4 decoder is a block which decodes the 2-bit binary inputs and produces four outputs
- One output corresponding to the input combination is a one
- Two inputs and four outputs are shown in the figure
- The equations are
  - $y_0 = x_1' \cdot x_0'$
  - $y_1 = x_1' \cdot x_0$
  - $y_2 = x_1 \cdot x_0'$
  - $y_3 = x_1 \cdot x_0$
- The truth table:

x1	x0	y3	y2	y1	y0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

CprE 210

Lec 15

11

### Definition of Encoder

- Encoders perform the inverse function of Decoders.
- An encoder has  $2^n$  (or less) input bits and  $n$  output bits
- The output bits generate the binary code corresponding to the input value
- Assuming only one input has a value of 1 at any given time
- Example: An 8-to-3 Encoder

Inputs								Outputs		
D7	D6	D5	D4	D3	D2	D1	D0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_2 = D_4 + D_5 + D_6 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$


$$A_0 = D_1 + D_3 + D_5 + D_7$$

CprE 210

Lec 15

12

### What are the outputs of the following circuits?

 

CprE 210

Lec 15

13

### Priority Encoders

- Each input signal has a priority level associated with it
- May have more than one 1's in the input signals
- Outputs indicate the active input that has the highest priority
- Example: 4-to-2 priority encoder
  - Assume  $w_3$  has the highest priority and  $w_0$  the lowest
  - $y_1 y_0$  indicate the active input with highest priority
  - $z$  indicates none of the inputs is equal to 1

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

x: both 0 and 1 (irrelevant)

Let  $i_0 = w_0 w_1' w_2' w_3'$   
 $i_1 = w_1 w_2' w_3'$   
 $i_2 = w_2 w_3'$   
 $i_3 = w_3$   
 Then  $y_0 = i_1 + i_3$   
 $y_1 = i_2 + i_3$


CprE 210

Lec 15

14

### Decoder with Enable

- A 2-to-4 decoder can be designed with an enable signal
- If enable is zero, all outputs are zero
- If enable is 1, then an output corresponding to two inputs is a one, all others are still zero
- The equations are
  - $y_0 = x_1' \cdot x_0' \cdot E$
  - $y_1 = x_1' \cdot x_0 \cdot E$
  - $y_2 = x_1 \cdot x_0' \cdot E$
  - $y_3 = x_1 \cdot x_0 \cdot E$

 

CprE 210

Lec 15

15

### Truth Table for 2-to-4 Decoder with Enable

$x_1$	$x_0$	$E$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	0
1	1	1	1	0	0	0


CprE 210

Lec 15

16

### Demultiplexers

- Perform the opposite function of multiplexers
- Placing the value of a single data input onto one of the multiple data outputs
- Same implementation as decoder with enable
- Enable input of decoder serves as the data input for the demultiplexer

 


CprE 210

Lec 15

17

### 3-to-8 decoder using a 2-to-4 decoder with Enable

- The 3-to-8 decoder can be implemented using two 2-to-4 decoders with enable and one NOT gate
- The implementation is as shown

 

CprE 210

Lec 15

18