


Supplementation

- Field Effect Transistors
- DC Biasing
- FET Amplifiers

Field Effect Transistors

What is FET?

 In FET, a weak electrical signal coming through one electrode creates an electric field which controls the current flowing.



FET	BJT
<ol style="list-style-type: none"> 1. FET is an unipolar semiconductor device because its operation depends upon the flow of majority carriers i.e., either holes or electrons as the case may be. 2. The input impedance of FET is much more larger (ranging in Megaohms) than BJT. The reason behind this is that the input terminal i.e., gate to source of FET is reverse biased and reverse bias offers ideally infinite resistance. 3. FET is a voltage controlled device. 4. FET is less noisy. Because there are no junctions. 5. Higher frequency response. 6. Good thermal stability because of absence of minority carriers. 7. Costlier than BJT. 8. Small sized. 9. In FET, relationship between input and output quantities is nonlinear due to square term in shockley's equations $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$ <ol style="list-style-type: none"> 10. No offset voltage; so it works better as a switch or chopper. 11. Small gain bandwidth product. 	<ol style="list-style-type: none"> 1. BJT is a bipolar semiconductor device because the current constituting elements are both majority carriers as well as minority carriers in this case. 2. The input impedance of BJT is very less in comparison to FET. 3. BJT is a current controlled device. 4. Much noisy than FET. 5. Frequency variation affects the performance. 6. Temperature dependent, thermal runaway may cause. 7. Relatively cheaper. 8. Comparatively bigger. 9. The BJT is an almost linear device or we can say that BJT works linearly in active region as an amplifier. 10. There is always an offset voltage before switching. 11. Greater than FET.

FET are smaller and more temperature stable than BJT and suited for IC applications.

FETs vs. BJTs

Similarities:

- Amplifiers
- Switching devices
- Impedance matching circuits

Differences:


FETs are voltage controlled devices. BJTs are current controlled devices.

FETs have higher input impedance. BJTs have higher gain.

FETs are less sensitive to temperature variations and are better suited for integrated circuits

FETs are generally more static sensitive than BJTs.

FET Family

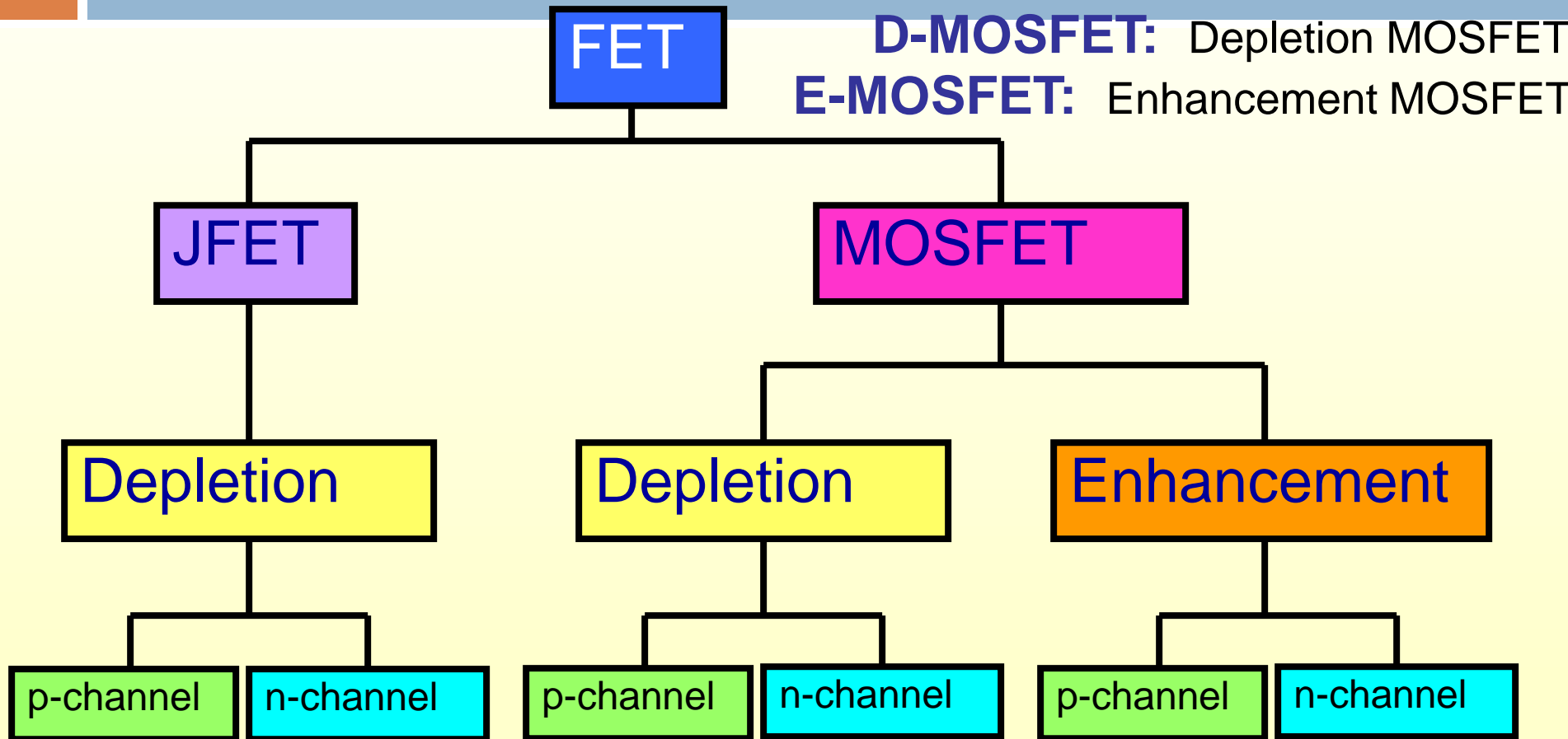


JFET: Junction FET


MOSFET: Metal–Oxide–Semiconductor FET

CMOS


JFET construction.

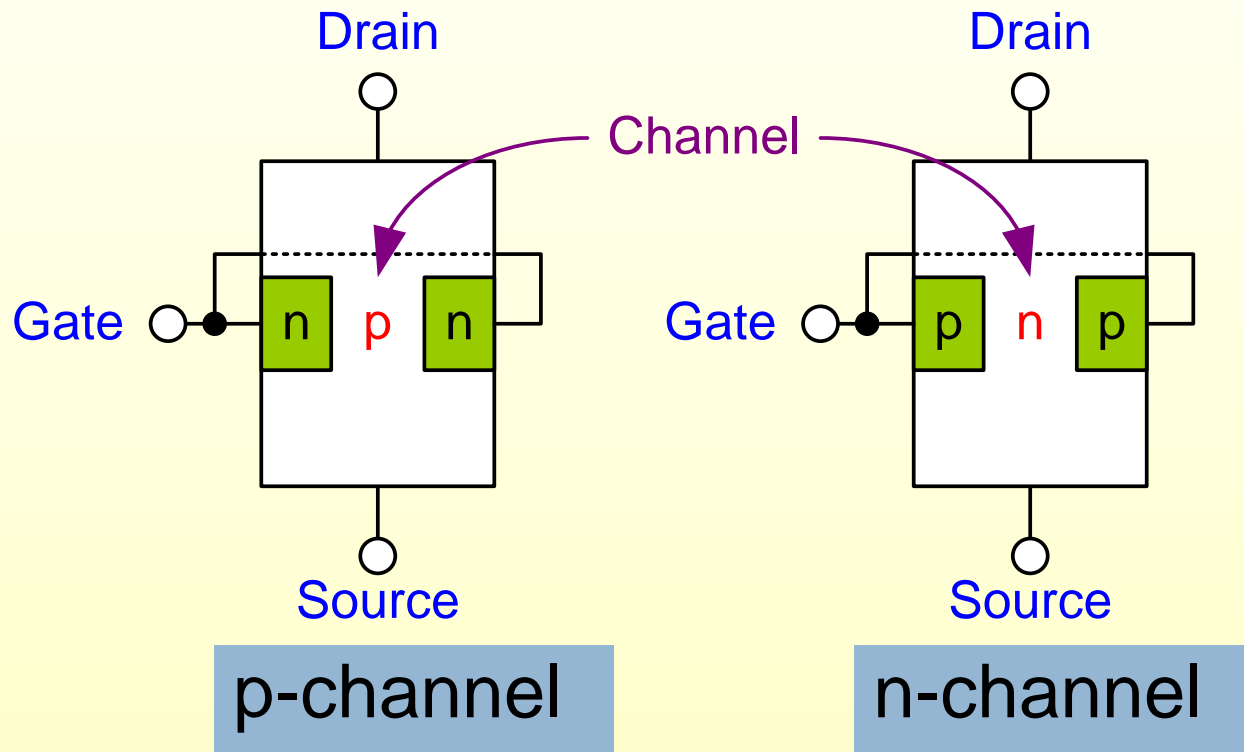

JFET schematic symbols.



 


n-channel



 


p-channel

  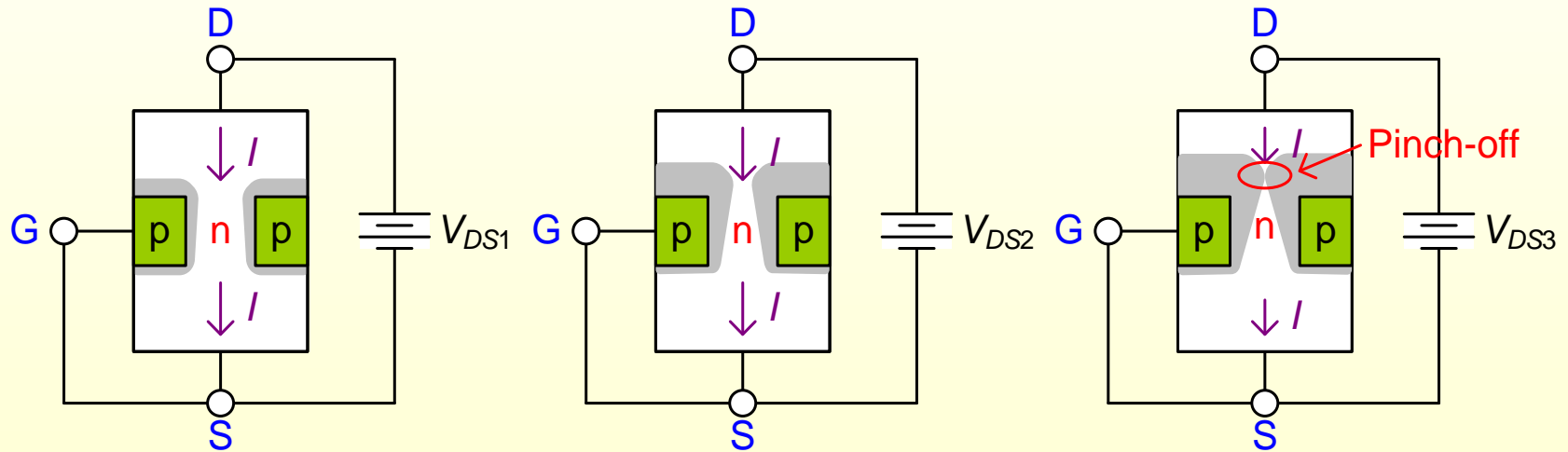Summary: Varying V_{DS} with $V_{GS} = 0V$



Summary: Varying V_{GS}

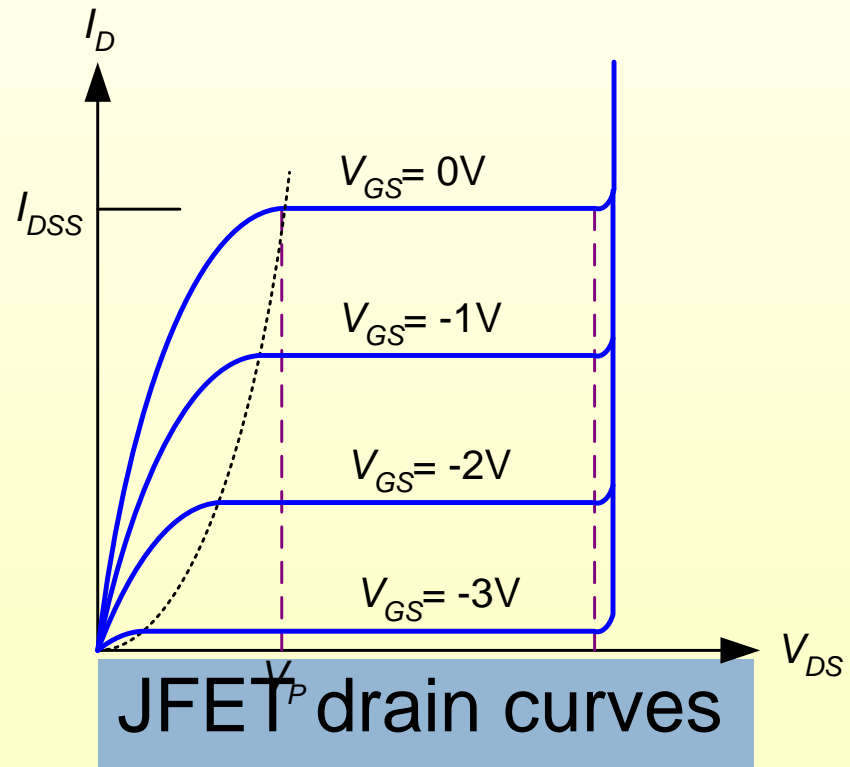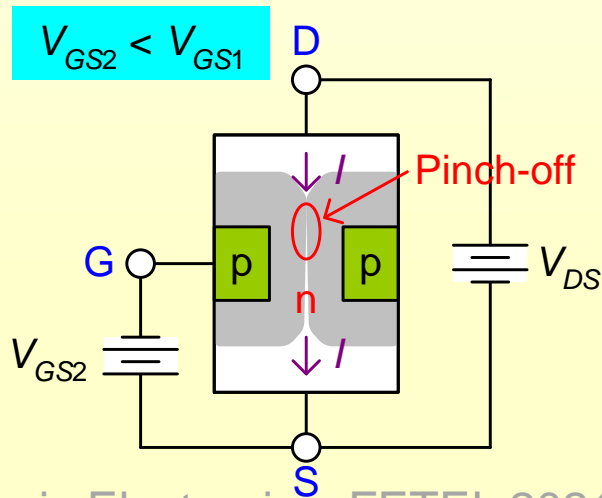
 


JFET Transfer Curve

This graph shows the value of I_D for a given value of V_{GS} .

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

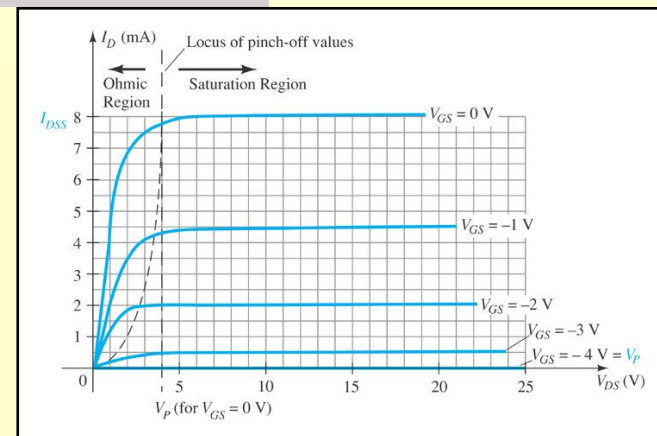 where I_{DSS} = saturation drain current
 V_P = pinch-off voltage (or $V_{GS(off)}$)



BJT vs. JFET

control variable




$$I_C = f(I_B) = \beta I_B$$

constant

control variable

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

constants

   


JFET


Specification Sheet

FAIRCHILD
SEMICONDUCTOR™

2N5457
2N5458
2N5459

 

MMBF5457
MMBF5458
MMBF5459

 

N-Channel General Purpose Amplifier

This device is a low level audio amplifier and switching transistors, and can be used for analog switching applications. Sourced from Process 55.

Absolute Maximum Ratings*

TA = 25°C unless otherwise noted

Symbol	Parameter	Value	Units
V _{DG}	Drain-Gate Voltage	25	V
V _{GS}	Gate-Source Voltage	- 25	V
I _{GF}	Forward Gate Current	10	mA
T _J , T _{stg}	Operating and Storage Junction Temperature Range	-55 to +150	°C

N-Channel General Purpose Amplifier (continued)

Electrical Characteristics

TA = 25°C unless otherwise noted

Symbol	Parameter	Test Conditions	Min	Typ	Max	Units
--------	-----------	-----------------	-----	-----	-----	-------

OFF CHARACTERISTICS

V _{BR/GSS}	Gate-Source Breakdown Voltage	I _G = 10 μA, V _{DS} = 0	- 25			V
I _{GSS}	Gate Reverse Current	V _{GS} = -15 V, V _{DS} = 0 V _{GS} = -15 V, V _{DS} = 0, T _A = 100°C			- 1.0 - 200	nA nA
V _{GS(off)}	Gate-Source Cutoff Voltage	V _{DS} = 15 V, I _D = 10 nA	- 0.5 - 1.0 - 2.0		- 6.0 - 7.0 - 8.0	V V V
V _{GS}	Gate-Source Voltage	V _{DS} = 15 V, I _D = 100 μA V _{DS} = 15 V, I _D = 200 μA V _{DS} = 15 V, I _D = 400 μA		- 2.5 - 3.5 - 4.5		V V V

ON CHARACTERISTICS

I _{DSS}	Zero-Gate Voltage Drain Current*	V _{DS} = 15 V, V _{GS} = 0	1.0 2.0 4.0	3.0 6.0 9.0	5.0 9.0 16	mA mA mA
------------------	----------------------------------	---	-------------------	-------------------	------------------	----------------

SMALL SIGNAL CHARACTERISTICS

g _{fs}	Forward Transfer Conductance*	V _{DS} = 15 V, V _{GS} = 0, f = 1.0 kHz	1000 1500 2000		5000 5500 6000	μmhos μmhos μmhos
g _{os}	Output Conductance*	V _{DS} = 15 V, V _{GS} = 0, f = 1.0 kHz		10	50	μmhos
C _{iss}	Input Capacitance	V _{DS} = 15 V, V _{GS} = 0, f = 1.0 MHz		4.5	7.0	pF
C _{rss}	Reverse Transfer Capacitance	V _{DS} = 15 V, V _{GS} = 0, f = 1.0 MHz		1.5	3.0	pF
NF	Noise Figure	V _{DS} = 15 V, V _{GS} = 0, f = 1.0 kHz, R _G = 1.0 megohm, BW = 1.0 Hz			3.0	dB

2N5457 / 5458 / 5459 / MMBF5457 / 5458 / 5459

2N5457 / 5458 / 5459 / MMBF5457 / 5458 / 5459

Example

The partial datasheet for a 2N5459 JFET indicates that typically $I_{DSS} = 9 \text{ mA}$ and $V_{GS(off)} = -8 \text{ V}$ (maximum). Using these values, determine the drain current for $V_{GS} = 0 \text{ V}$, -1 V , and -4 V .

For $V_{GS} = 0 \text{ V}$,

$$I_D = I_{DSS} = \mathbf{9 \text{ mA}}$$

For $V_{GS} = -1 \text{ V}$,

$$\begin{aligned} I_D &\cong I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (9 \text{ mA}) \left(1 - \frac{-1 \text{ V}}{-8 \text{ V}} \right)^2 \\ &= (9 \text{ mA})(1 - 0.125)^2 = (9 \text{ mA})(0.766) = \mathbf{6.89 \text{ mA}} \end{aligned}$$

For $V_{GS} = -4 \text{ V}$,

$$I_D \cong (9 \text{ mA}) \left(1 - \frac{-4 \text{ V}}{-8 \text{ V}} \right)^2 = (9 \text{ mA})(1 - 0.5)^2 = (9 \text{ mA})(0.25) = \mathbf{2.25 \text{ mA}}$$


JFET Biasing Circuits

- Gate bias (Fixed bias) circuit
- Self bias circuit
- Voltage-divider bias circuit


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$V_{GS} = \text{????} \rightarrow \text{BIAS}$

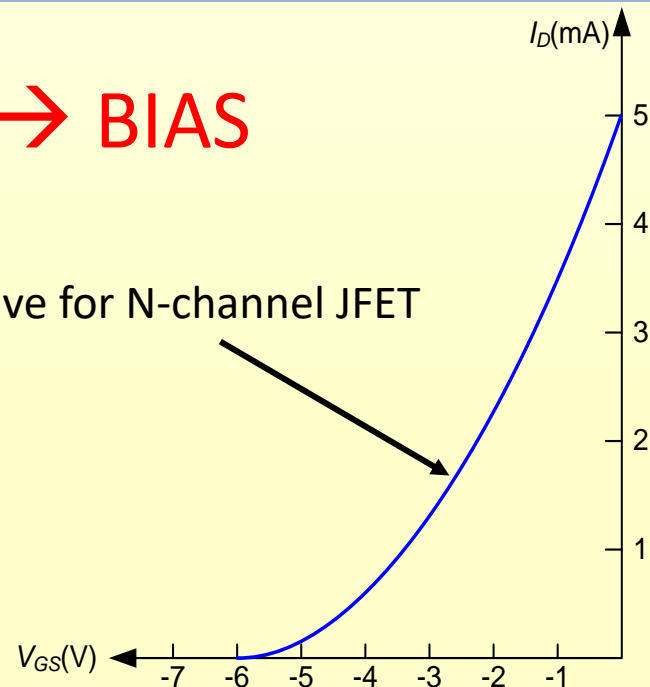
V_{GS} must be negative for N-channel JFET




Gate Bias (Fixed bias)

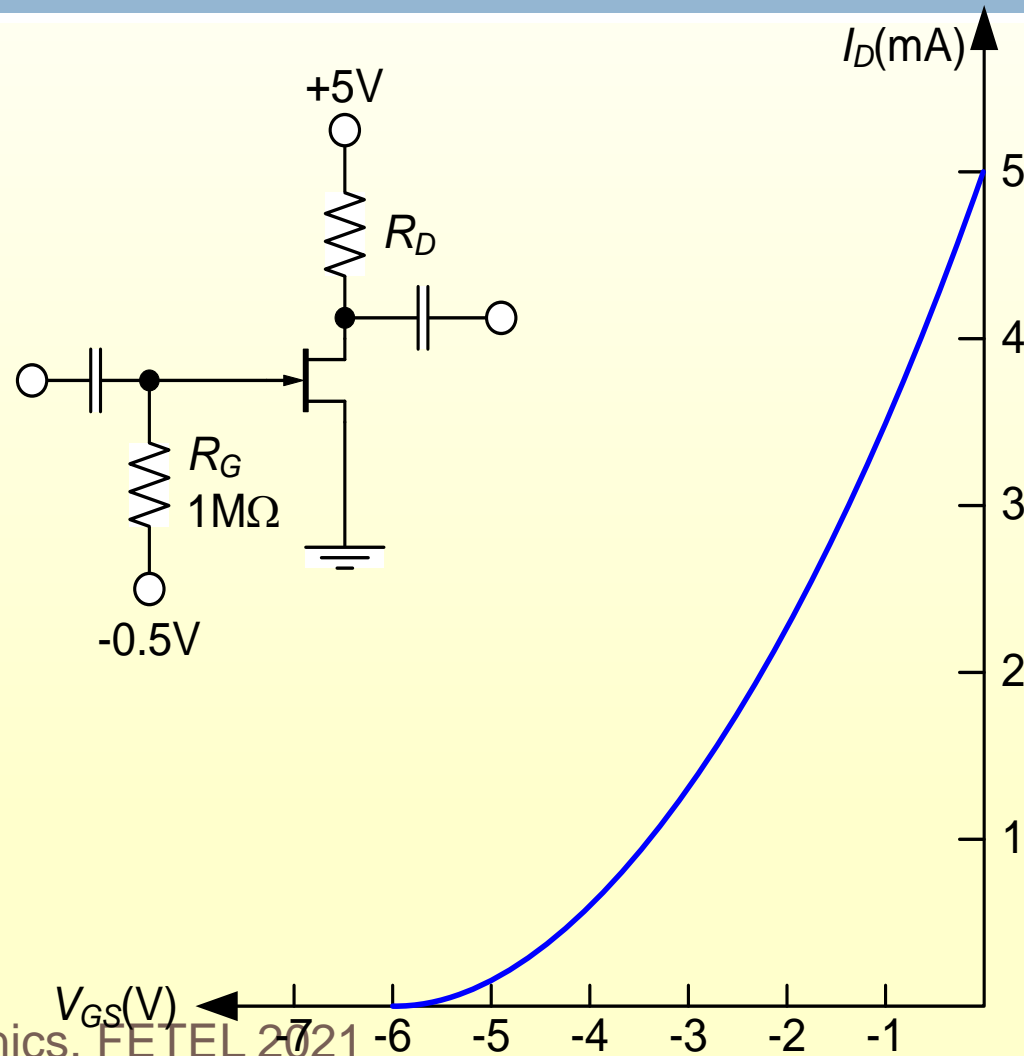

Self bias circuit.

 

Voltage-divider bias.

 

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$$

$$\therefore I_D|_{V_{GS}=0} = \frac{V_G}{R_S}$$

$$\therefore V_{GS}|_{I_D=0} = V_G$$

JFET Biasing:

Gate bias/Fixed Bias Configuration

$$V_{DS} = V_{DD} - I_D R_D$$


$$V_S = 0 \text{ V}$$

$$V_C = V_{DS}$$


$$V = V_{GS}$$

$$V_{GS} = -V_{GG}$$
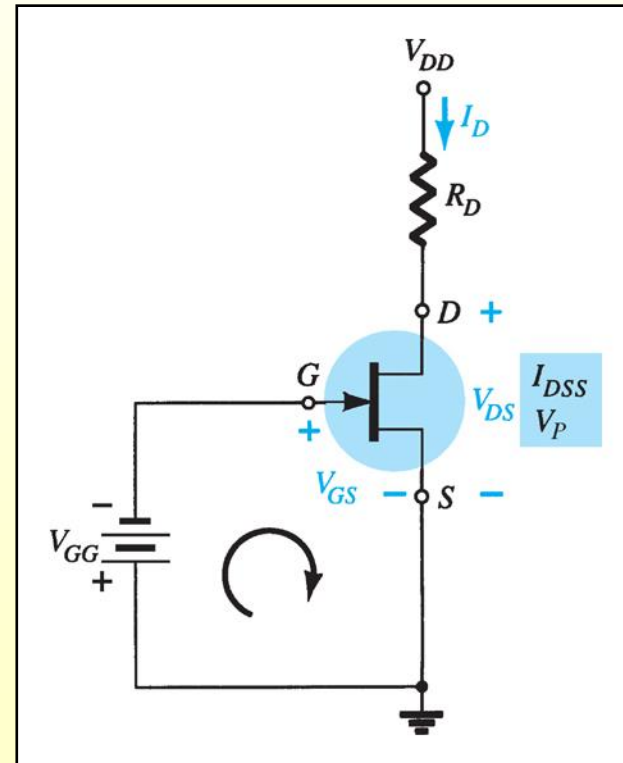
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



Example

 


Mathematical Approach

- $V_{GS_Q} = -V_{GG} = -2 \text{ V}$
- $I_{D_Q} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 - \frac{-2 \text{ V}}{-8 \text{ V}} \right)^2$
 $= 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625)$
 $= 5.625 \text{ mA}$
- $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.25 \text{ V} = 4.75 \text{ V}$
- $V_D = V_{DS} = 4.75 \text{ V}$
- $V_G = V_{GS} = -2 \text{ V}$
- $V_S = 0 \text{ V}$

Graphical Approach

 
- $V_{GS_Q} = -V_{GG} = -2 \text{ V}$
- $I_{D_Q} = 5.6 \text{ mA}$
- $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$
- $V_D = V_{DS} = 4.8 \text{ V}$
- $V_G = V_{GS} = -2 \text{ V}$
- $V_S = 0 \text{ V}$



- V_{GS_Q}
- I_{D_Q}
- V_{DS}
- V_D
- V_G
- V_S

JFET Biasing:

Self-Bias Configuration

 

JFET Biasing:

Self-Bias Calculations


Graphical calculations

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

1. Select a value of $I_D < I_{DSS}$ and use the component value of R_S to calculate V_{GS} . Plot the point identified by I_D and V_{GS} and draw a line from the origin of the axis to this point.
2. Plot the transfer curve using I_{DSS} and V_P ($V_P = |V_{GSoff}|$ on spec sheets) and a few points such as $V_{GS} = V_P/4$ and $V_{GS} = V_P/2$ etc.

 The Q-point is located where the first line intersects the transfer curve. Using the value of I_D at the Q-point (I_{DQ}):





$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_D = V_{DS} + V_S = V_{DD} - V_{RD}$$

  Example

- V_{GS_Q}
- I_{D_Q}
- V_{DS}
- V_S
- V_G
- V_D




$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= I_{DSS} \left(1 - \frac{-I_D R_S}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$

$$V_{GS_Q} = -2.6 \text{ V}$$

 

b. At the quiescent point

$$I_{D_Q} = 2.6 \text{ mA}$$

c.

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$= 20 \text{ V} - (2.6 \text{ mA})(1 \text{ k}\Omega + 3.3 \text{ k}\Omega)$$

$$= 20 \text{ V} - 11.18 \text{ V}$$

$$= 8.82 \text{ V}$$

d.

$$V_S = I_D R_S$$

$$= (2.6 \text{ mA})(1 \text{ k}\Omega)$$

$$= 2.6 \text{ V}$$

e. $V_G = 0 \text{ V}$

f. $V_D = V_{DS} + V_S = 8.82 \text{ V} + 2.6 \text{ V} = 11.42 \text{ V}$


$$V_D = V_{DD} - I_D R_D = 20 \text{ V} - (2.6 \text{ mA})(3.3 \text{ k}\Omega) = 11.42 \text{ V}$$

JFET Biasing:

Voltage-Divider Bias

$$I_G = 0 \text{ A}$$

I_D responds to changes in V_{GS} .

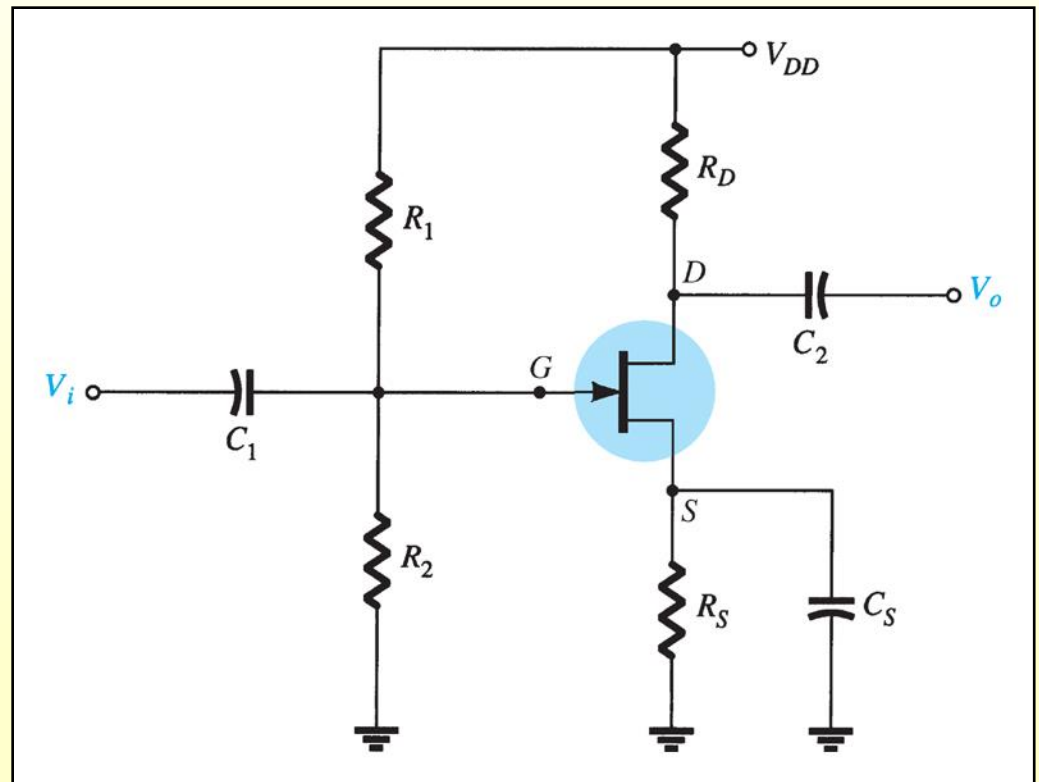

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

JFET Biasing:


Voltage-Divider Bias Calculations

V_G is equal to the voltage across divider resistor R_2 :

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Using Kirchhoff's Law:

$$V_{GS} = V_G - I_D R_S$$

 

The Q-point is established by plotting a line that intersects the transfer curve.

JFET Biasing:


Voltage-Divider Q-Point

Plot the line that is defined by these two points:

$$V_{GS} = V_G, I_D = 0 \text{ A}$$

$$V_{GS} = 0 \text{ V}, I_D = V_G / R_S$$

 Plot the transfer curve by plotting I_{DSS} , V_P and the calculated values of I_D



The Q-point is located where the line intersects the transfer curve

JFET Biasing:

Voltage-Divider Bias Calculations

Using the value of I_D at the Q-point, solve for the other values in the voltage-divider bias circuit:


$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

 Example

- I_{DQ} and V_{GSQ} .
- V_D .
- V_S .
- V_{DS} .
- V_{DG} .



$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$= \frac{(270 \text{ k}\Omega)(16 \text{ V})}{2.1 \text{ M}\Omega + 0.27 \text{ M}\Omega}$$


$$= 1.82 \text{ V}$$

$$V_{GS} = V_G - I_D R_S$$

$$= 1.82 \text{ V} - I_D (1.5 \text{ k}\Omega)$$

$$I_{DQ} = 2.4 \text{ mA}$$

$$V_{GSQ} = -1.8 \text{ V}$$

 

Determining the Q-point

$$b. V_D = V_{DD} - I_D R_D$$

$$= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega)$$

$$= 10.24 \text{ V}$$

$$c. V_S = I_D R_S = (2.4 \text{ mA})(1.5 \text{ k}\Omega)$$

$$= 3.6 \text{ V}$$

$$d. V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega + 1.5 \text{ k}\Omega)$$

$$= 6.64 \text{ V}$$

$$\text{or } V_{DS} = V_D - V_S = 10.24 \text{ V} - 3.6 \text{ V}$$

$$= 6.64 \text{ V}$$

$$V_{DG} = V_D - V_G$$

$$= 10.24 \text{ V} - 1.82 \text{ V}$$

$$= 8.42 \text{ V}$$



JFET Amplifiers


JFET amplifier:

FET Small-Signal Model

Transconductance: The ratio of a change in I_D to the corresponding change in V_{GS}

- Transconductance is denoted g_m and given by:
 
$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$



JFET amplifier:

Mathematical Definitions of g_m

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$


$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

For $V_{GS} = 0 \text{ V}$

$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right] = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

FET AC Equivalent Circuit

 

JFET amplifier:

FET Impedance

Input impedance:

$$Z_i = \infty \Omega$$

Output Impedance:



$$Z_o = r_d = \frac{1}{y_{os}} \quad \text{where} \quad r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} = \text{constant}}$$

y_{os} = admittance parameter listed on FET spec sheets

JFET amplifier:

Common-Source (CS) Self-Bias

  This is a common-source amplifier configuration, so the input is applied to the gate and the output is taken from the drain.



There is a 180° phase shift between input and output.

JFET amplifier:

Common-Source (CS) Self-Bias Calculation

32

Input impedance:

$$Z_i = R_G$$

Output impedance:


$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \Big|_{r_d \geq 10 R_D}$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$



$$A_v = -g_m R_D \Big|_{r_d \geq 10 R_D}$$

 

JFET amplifier:

Common-Source (CS) Self-Bias Calculation, without C_S

  Removing C_S affects the gain of the circuit.



JFET amplifier:

Common-Source (CS) Self-Bias Calculation, without C_S

Input impedance:

$$Z_i = R_G$$


Output impedance:

$$Z_o \cong R_D \Big|_{r_d \geq 10 R_D}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$



$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S} \Big|_{r_d \geq 10(R_D + R_S)}$$

 

JFET amplifier:

Common-Source (CS) Voltage-Divider Bias

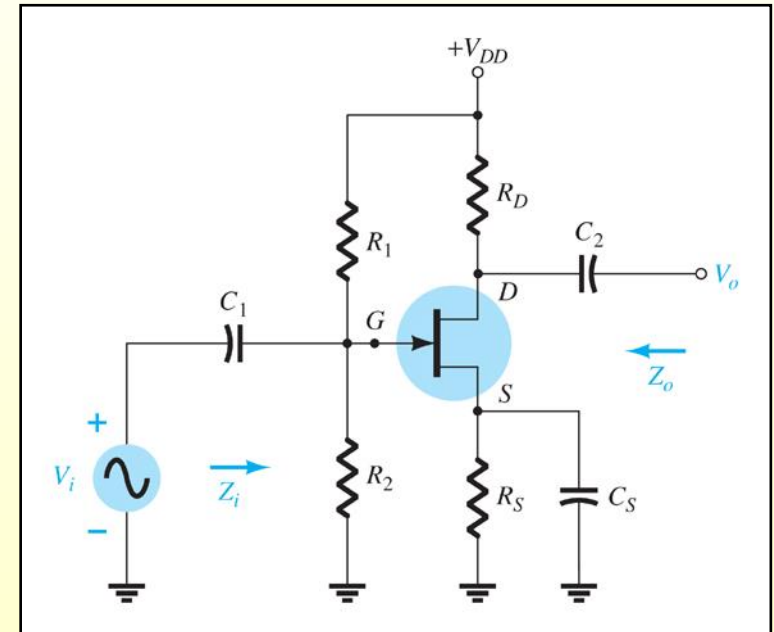 This is a common-source amplifier configuration, so the input is applied to the gate and the output is taken from the drain.



JFET amplifier:

Common-Source (CS) Voltage-Divider Bias

Impedances

Input impedance:


$$Z_i = R_1 \parallel R_2$$

Output impedance:




$$Z_o = r_d \parallel R_D$$
$$Z_o \cong R_D \Big|_{r_d \geq 10 R_D}$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$
$$A_v = -g_m R_D \Big|_{r_d \geq 10 R_D}$$

 

JFET amplifier

  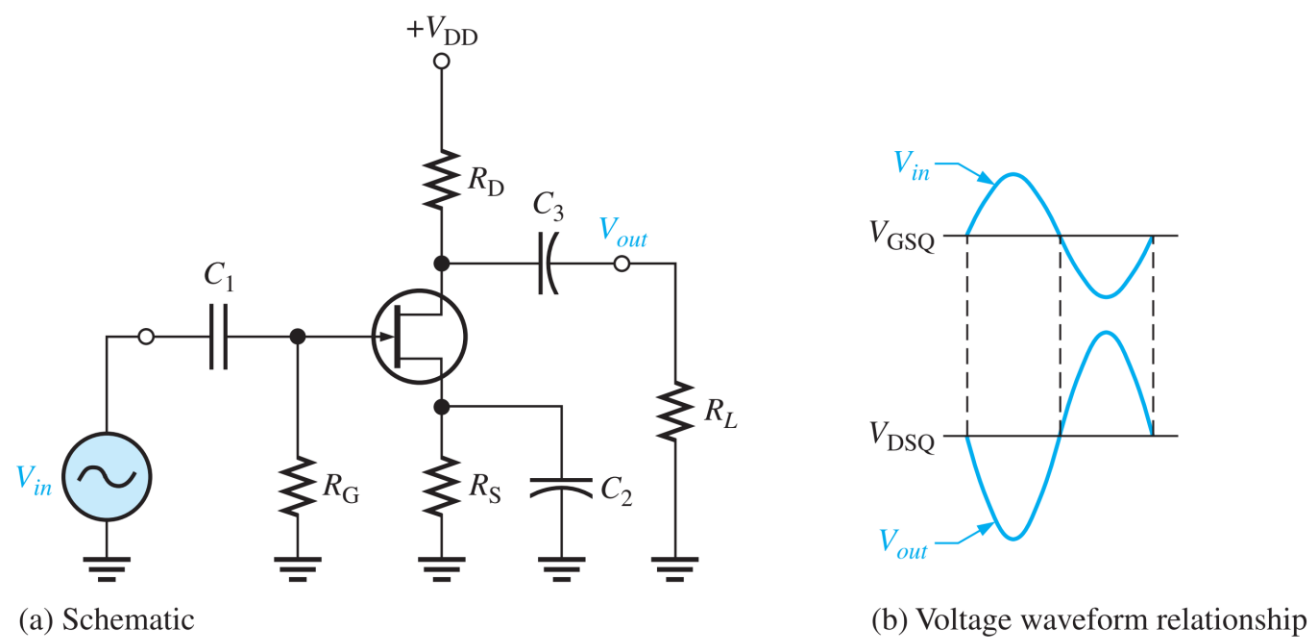

EXAMPLE 8.8 The self-bias configuration of Example 7.2 has an operating point defined by $V_{GS_Q} = -2.6$ V and $I_{D_Q} = 2.6$ mA, with $I_{DSS} = 8$ mA and $V_P = -6$ V. The network is redrawn as Fig. 8.20 with an applied signal V_i . The value of g_{os} is given as $20 \mu\text{S}$.

- Determine g_m .
- Find r_d .
- Find Z_i .
- Calculate Z_o with and without the effects of r_d . Compare the results.
- Calculate A_v with and without the effects of r_d . Compare the results.

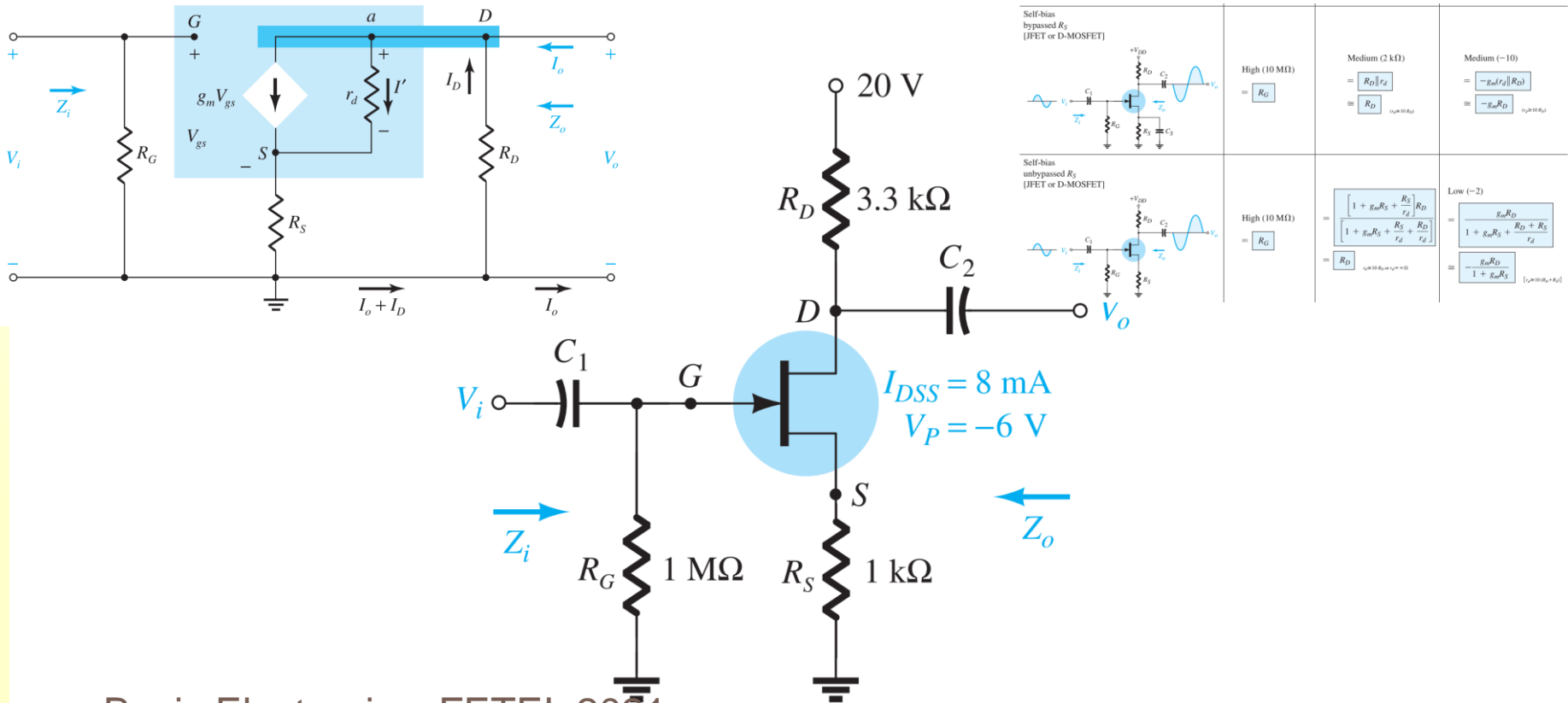


FIG. 8.20

Solution:

$$\text{a. } g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(8 \text{ mA})}{6 \text{ V}} = 2.67 \text{ mS}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS_Q}}{V_P} \right) = 2.67 \text{ mS} \left(1 - \frac{(-2.6 \text{ V})}{(-6 \text{ V})} \right) = \mathbf{1.51 \text{ mS}}$$

$$\text{b. } r_d = \frac{1}{y_{os}} = \frac{1}{20 \mu\text{S}} = \mathbf{50 \text{ k}\Omega}$$

$$\text{c. } Z_i = R_G = \mathbf{1 \text{ M}\Omega}$$

d. With r_d ,

$$r_d = 50 \text{ k}\Omega > 10R_D = 33 \text{ k}\Omega$$

Therefore,

$$Z_o = R_D = \mathbf{3.3 \text{ k}\Omega}$$

If $r_d = \infty \Omega$,







$$Z_o = R_D = \mathbf{3.3 \text{ k}\Omega}$$











e. With r_d ,









$$\begin{aligned} A_v &= \frac{-g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}} = \frac{-(1.51 \text{ mS})(3.3 \text{ k}\Omega)}{1 + (1.51 \text{ mS})(1 \text{ k}\Omega) + \frac{3.3 \text{ k}\Omega + 1 \text{ k}\Omega}{50 \text{ k}\Omega}} \\ &= \mathbf{-1.92} \end{aligned}$$





With $r_d = \infty \Omega$ (open-circuit equivalence),





$$\text{39 Basic Electronics, FETEL 2021 } A_v = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-(1.51 \text{ mS})(3.3 \text{ k}\Omega)}{1 + (1.51 \text{ mS})(1 \text{ k}\Omega)} = \mathbf{-1.98}$$

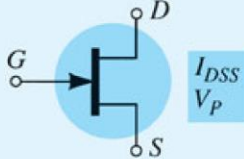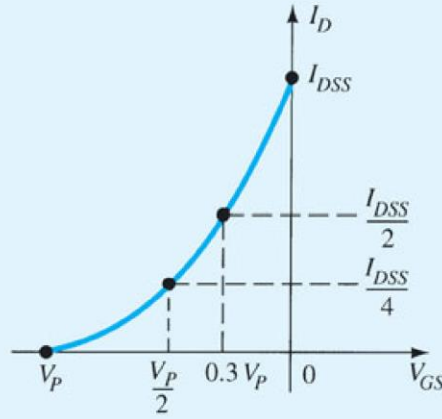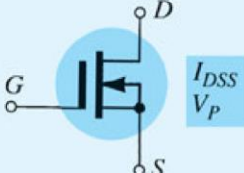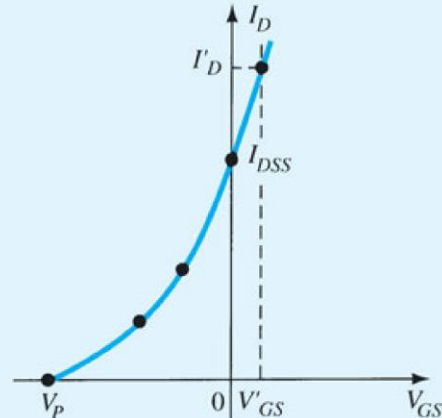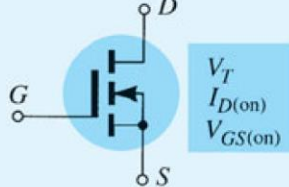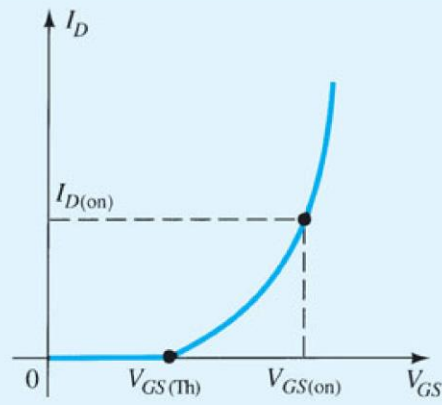Type	Symbol and Basic Relationships	Transfer Curve	Input Resistance and Capacitance
JFET (<i>n</i> -channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$		$R_i > 100 \text{ M}\Omega$ $C_i: (1 - 10) \text{ pF}$
MOSFET depletion type (<i>n</i> -channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$		$R_i > 10^{10} \Omega$ $C_i: (1 - 10) \text{ pF}$
MOSFET enhancement type (<i>n</i> -channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = k (V_{GS} - V_{GS(Th)})^2$ $I_D = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$		$R_i > 10^{10} \Omega$ $C_i: (1 - 10) \text{ pF}$

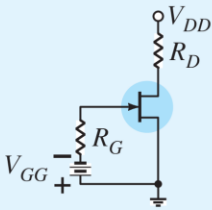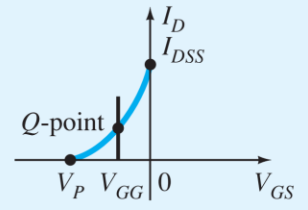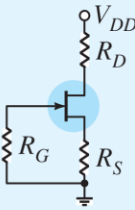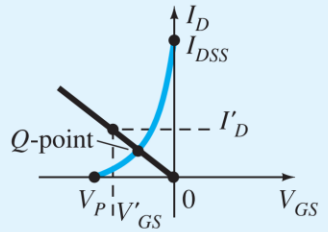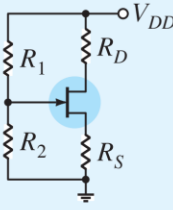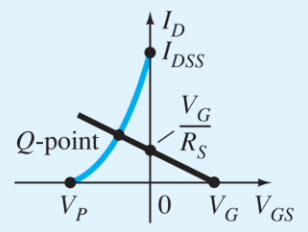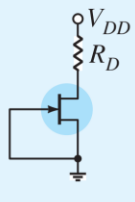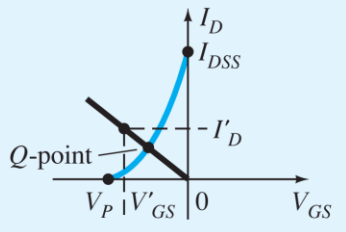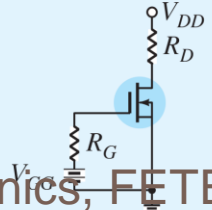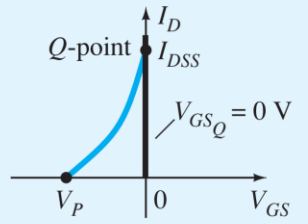Type	Configuration	Pertinent Equations	Graphical Solution
JFET Fixed-bias		$V_{GS_Q} = -V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
JFET Self-bias		$V_{GS} = -I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
JFET Voltage-divider bias		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
JFET ($R_D = 0 \Omega$)		$V_{GS} = -I_D R_S$ $V_D = V_{DD}$ $V_S = I_D R_S$ $V_{DS} = V_{DD} - I_S R_S$	
JFET Special case ($V_{GS_Q} = 0 \text{ V}$)		$V_{GS_Q} = 0 \text{ V}$ $I_{D_Q} = I_{DSS}$	

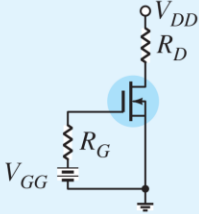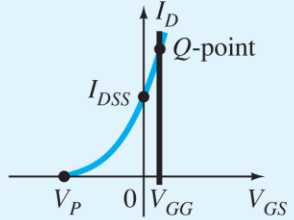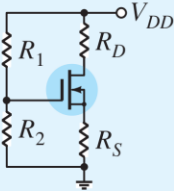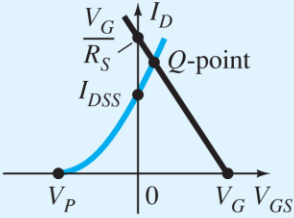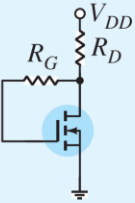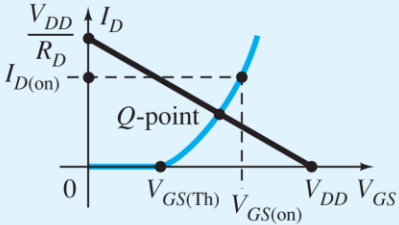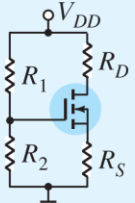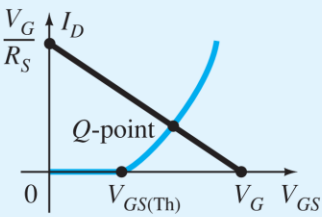Depletion-type MOSFET Fixed-bias (and MESFETs)		$V_{GS_Q} = +V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
Depletion-type MOSFET Voltage-divider bias (and MESFETs)		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_S R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
Enhancement type MOSFET Feedback configuration (and MESFETs)		$V_{GS} = V_{DS}$ $V_{GS} = V_{DD} - I_D R_D$	
Enhancement type MOSFET Voltage-divider bias (and MESFETs)		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$	

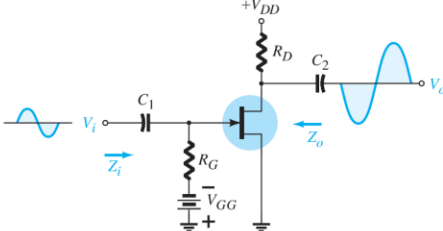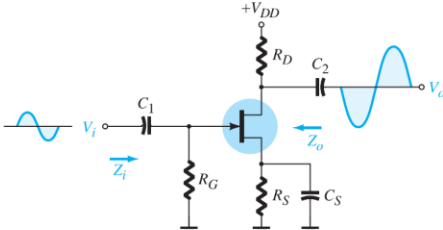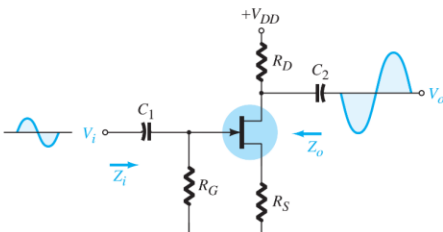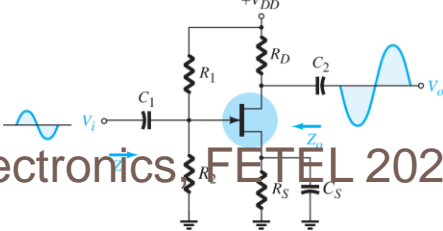Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
Fixed-bias [JFET or D-MOSFET] 	High (10 M Ω) $= R_G$	Medium (2 k Ω) $= R_D \parallel r_d$ $\cong R_D$ ($r_d \cong 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D$ ($r_d \cong 10 R_D$)
Self-bias bypassed R_S [JFET or D-MOSFET] 	High (10 M Ω) $= R_G$	Medium (2 k Ω) $= R_D \parallel r_d$ $\cong R_D$ ($r_d \cong 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D$ ($r_d \cong 10 R_D$)
Self-bias unbypassed R_S [JFET or D-MOSFET] 	High (10 M Ω) $= R_G$	$= \frac{\left[1 + g_m R_S + \frac{R_S}{r_d}\right] R_D}{1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d}}$ $= R_D$ ($r_d \cong 10 R_D$ or $r_d = \infty$)	Low (-2) $= \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$ $\cong \frac{g_m R_D}{1 + g_m R_S}$ ($r_d \cong 10 (R_D + R_S)$)
Voltage-divider bias [JFET or D-MOSFET] 	High (10 M Ω) $= R_1 \parallel R_2$	Medium (2 k Ω) $= R_D \parallel r_d$ $\cong R_D$ ($r_d \cong 10 R_D$)	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D$ ($r_d \cong 10 R_D$)

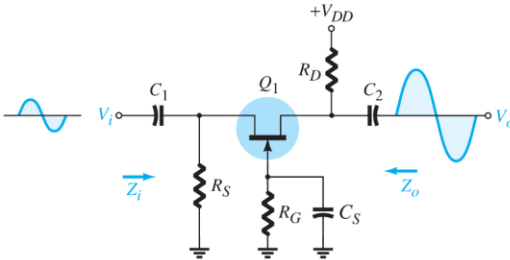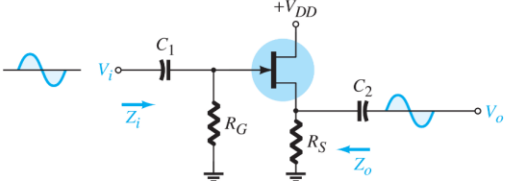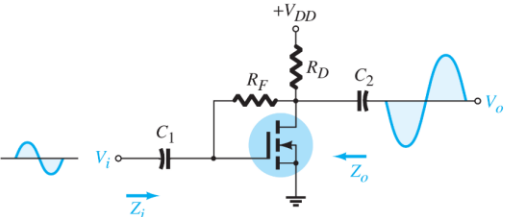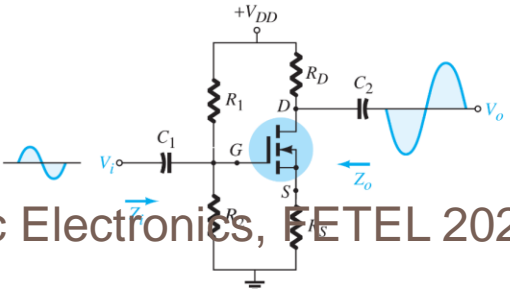Configuration	Z_i	Z_o	$A_v = \frac{V_o}{V_i}$
Common-gate [JFET or D-MOSFET] 	Low (1 k Ω) $= R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$ $\cong R_S \parallel \frac{1}{g_m} \quad (r_d \geq 10 R_D)$	Medium (2 k Ω) $= R_D \parallel r_d$ $\cong R_D \quad (R_D \geq 10 R_D)$	Medium (+10) $= \frac{g_m R_D + \frac{R_D}{r_d}}{1 + \frac{R_D}{r_d}}$ $\cong g_m R_D \quad (r_d \geq 10 R_D)$
Source-follower [JFET or D-MOSFET] 	High (10 M Ω) $= R_G$	Low (100 k Ω) $= r_d \parallel R_S \parallel 1/g_m$ $\cong R_S \parallel 1/g_m \quad (r_d \geq 10 R_S)$	Low (<1) $= \frac{g_m(r_d \parallel R_S)}{1 + g_m(r_d \parallel R_S)}$ $\cong \frac{g_m R_S}{1 + g_m R_S} \quad (r_d \geq 10 R_S)$
Drain-feedback bias E-MOSFET 	Medium (1 M Ω) $= \frac{R_F + r_d \parallel R_D}{1 + g_m(r_d \parallel R_D)}$ $\cong \frac{R_F}{1 + g_m R_D} \quad (r_d \geq 10 R_D)$	Medium (2 k Ω) $= R_F \parallel r_d \parallel R_D$ $\cong R_D \quad (R_F, r_d \geq 10 R_D)$	Medium (-10) $= -g_m(R_F \parallel r_d \parallel R_D)$ $\cong -g_m R_D \quad (R_F, r_d \geq 10 R_D)$
Voltage-divider bias E-MOSFET 	Medium (1 M Ω) $= R_1 \parallel R_2$	Medium (2 k Ω) $= R_D \parallel r_d$ $\cong R_D \quad (r_d \geq 10 R_D)$	Medium (-10) $= -g_m(r_d \parallel R_D)$ $\cong -g_m R_D \quad (r_d \geq 10 R_D)$

Admittance is defined as

$$Y \equiv \frac{1}{Z}$$

where

Y is the admittance, measured in siemens, Dẫn nạp
Z is the impedance, measured in ohms

$$Y = G + jB$$

here

Y is the admittance, measured in siemens.

G is the conductance, measured in siemens. Độ dẫn

B is the susceptance, measured in siemens. Điện nạp