

dce 2016



Digital Systems

Tran Ngoc Thinh
 HCMC University of Technology
<http://www.cse.hcmut.edu.vn/~tnthin>

BK TP.HCM

dce 2016

Boolean Constants and Variables

- Boolean algebra is an important tool in describing, analyzing, designing, and implementing digital circuits.
- Boolean algebra allows only two values; 0 and 1.
- Logic 0 can be: false, off, low, no, open switch.
- Logic 1 can be: true, on, high, yes, closed switch.
- Three basic logic operations: OR, AND, and NOT.

BK TP.HCM

dce 2016

Truth Tables


- A truth table describes the relationship between the input and output of a logic circuit.
- The number of entries corresponds to the number of inputs. For example a 2-input table would have $2^2 = 4$ entries. A 3-input table would have $2^3 = 8$ entries.

BK TP.HCM

dce 2016

Truth Tables

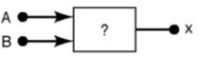- Examples of truth tables with 2, 3, and 4 inputs.



(a)

A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

(b)

A	B	C	x
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(c)

BK TP.HCM

dce 2016 OR Operation With OR Gates

- The Boolean expression for the OR operation is

$$X = A + B$$
 - This is read as "x equals A or B."
 - $X = 1$ when $A = 1$ or $B = 1$.
- Truth table, circuit symbol and timing diagram for a two input OR gate:

A	B	$x = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

5

dce 2016 OR Operation With OR Gates

- The OR operation is similar to addition but when $A = 1$ and $B = 1$, the OR operation produces $1 + 1 = 1$.
- In the Boolean expression

$$x = 1 + 1 + 1 + 1 = 1$$
 - We could say that x is true (1) when A is true (1) OR B is true (1) OR C is true (1) OR D is true (1).
- In general, the output of an **OR gate** is **HIGH** whenever **one or more inputs** are **HIGH**

A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

6

dce 2016 OR Operation With OR Gates

- There are many examples of applications where an output function is desired when one of multiple inputs is activated.

7

dce 2016 Review Questions

- What is the only set of input conditions that will produce a LOW output for any OR gate?
 - all inputs LOW
- Write the Boolean expression for a six-input OR gate
 - $X = A + B + C + D + E + F$
- If the A input in previous example is permanently kept at the 1 level, what will the resultant output waveform be?
 - constant HIGH

8

dce 2016 **AND Operations with AND gates**

- The Boolean expression for the AND operation is $X = A \cdot B$
 - This is read as "x equals A and B."
 - $x = 1$ when $A = 1$ and $B = 1$.
- Truth table and circuit symbol for a two input AND gate are shown. Notice the difference between OR and AND gates.

A	B	$x = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

9

dce 2016 **AND Operation With AND Gates**

- The AND operation is similar to multiplication.
- In the Boolean expression $X = A \cdot B \cdot C$
 - $X = 1$ only when $A = 1$, $B = 1$, and $C = 1$.
- The output of an AND gate is **HIGH** only when **all** inputs are **HIGH**.

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

10

dce 2016 **Review Questions**

- What is the only input combination that will produce a HIGH at the output of a five-input AND gate?
 - all 5 inputs = 1
- What logic level should be applied to the second input of a two-input AND gate if the logic signal at the first input is to be inhibited(prevented) from reaching the output?
 - A LOW input will keep the output LOW
- True or false: An AND gate output will always differ from an OR gate output for the same input conditions.
 - False

11

dce 2016 **NOT Operation**

- The Boolean expression for the NOT operation is $X = \bar{A}$ $X = A'$
- This is read as:
 - x equals NOT A, or
 - x equals the inverse of A, or
 - x equals the complement of A
- Truth table, symbol, and sample waveform for the NOT circuit.


A	$x = \bar{A}$
0	1
1	0

Presence of small circle always denotes inversion

12


Describing Logic Circuits Algebraically

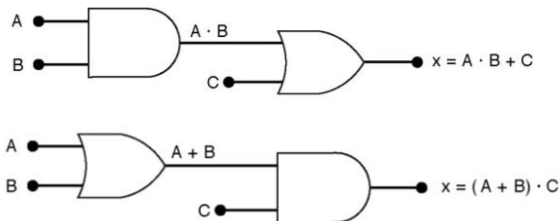- The three basic Boolean operations (OR, AND, NOT) can describe any logic circuit.
- Examples of Boolean expressions for logic circuits:




Describing Logic Circuits Algebraically

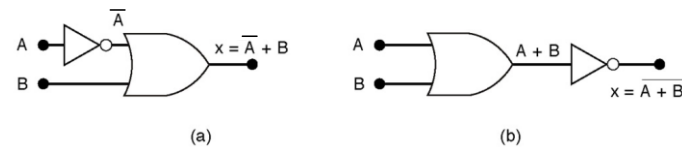- The output of an inverter is equivalent to the input with a bar over it. Input A through an inverter equals A' .
- Examples using inverters.



More Examples

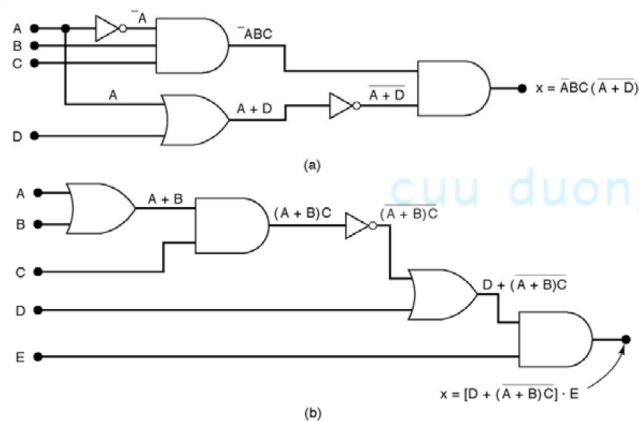

Evaluating Logic Circuit Outputs

- Rules for evaluating a Boolean expression:
 - Perform all inversions of single terms.
 - Perform all operations within parenthesis.
 - Perform AND operation before an OR operation unless parenthesis indicate otherwise.
 - If an expression has a bar over it, perform the operations inside the expression and then invert the result.

Evaluating Logic Circuit Outputs

- Evaluate Boolean expressions by substituting values and performing the indicated operations:

$A = 0, B = 1, C = 1, \text{ and } D = 1$


$$\begin{aligned} x &= \overline{A}BC(\overline{A+D}) \\ &= \overline{0} \cdot 1 \cdot 1 \cdot \overline{(0+1)} \\ &= 1 \cdot 1 \cdot 1 \cdot \overline{(0+1)} \\ &= 1 \cdot 1 \cdot 1 \cdot \overline{1} \\ &= 1 \cdot 1 \cdot 1 \cdot 0 \\ &= 0 \end{aligned}$$



17

Evaluating Logic Circuit Outputs

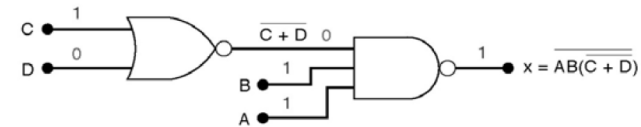
- Output logic levels can be determined directly from a circuit diagram.
- Technicians frequently use this method.
- The output of each gate is noted until a final output is found.



18

Implementing Circuits From Boolean Expressions

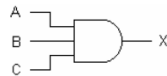- It is important to be able to draw a logic circuit from a Boolean expression.
- The expression $x = A \cdot B \cdot C$




could be drawn as a three input AND gate.

- A more complex example such as

$$y = AC + \overline{B}C + \overline{A}BC$$

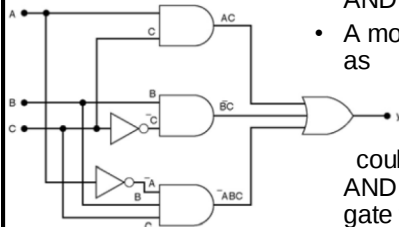could be drawn as two 2-input AND gates and one 3-input AND gate feeding into a 3-input OR gate. Two of the AND gates have inverted inputs.




19

Example

- Draw the circuit diagram to implement the expression

$$x = (A + B)(\overline{B} + C)$$

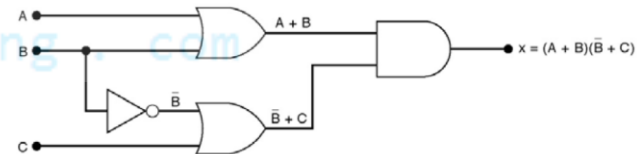


20

Review Question

- Draw the circuit diagram that implements the expression


$$x = \overline{A}BC\overline{(A+D)}$$

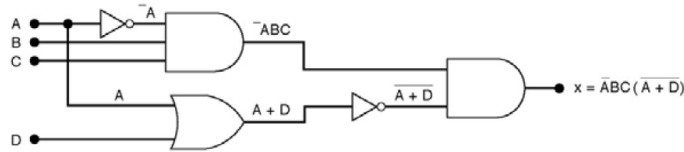using gates having no more than three inputs.




NOR Gates and NAND Gates

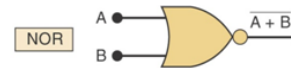- Combine basic AND, OR, and NOT operations.
- The NOR gate is an inverted OR gate. An inversion "bubble" is placed at the output of the OR gate.
- The Boolean expression is $x = \overline{A + B}$



A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

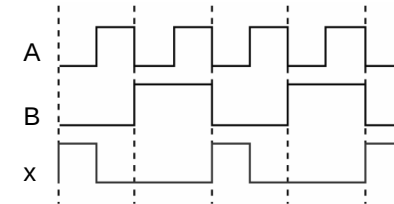


NOR Gates and NAND Gates

- The NAND gate is an inverted AND gate. An inversion "bubble" is placed at the output of the AND gate.
- The Boolean expression is $x = \overline{AB}$



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

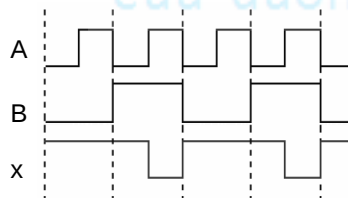


Laws of Boolean Algebra


- Commutative Laws
- Associative Laws
- Distributive Law

dce 2016 Commutative Laws of Boolean Algebra

$A + B = B + A$

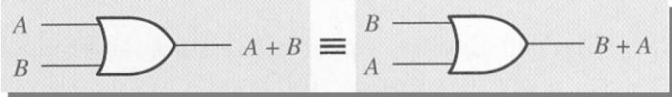


$A \cdot B = B \cdot A$

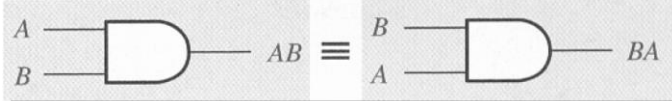


dce 2016

dce 2016 Associative Laws of Boolean Algebra

$A + (B + C) = (A + B) + C$

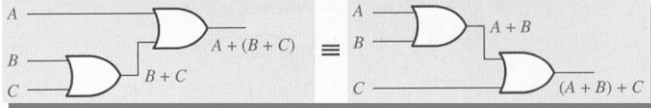

$A \cdot (B \cdot C) = (A \cdot B) \cdot C$

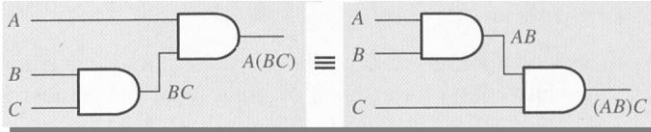


dce 2016

dce 2016 Distributive Laws of Boolean Algebra

$A \cdot (B + C) = A \cdot B + A \cdot C$

$A(B + C) = AB + AC$

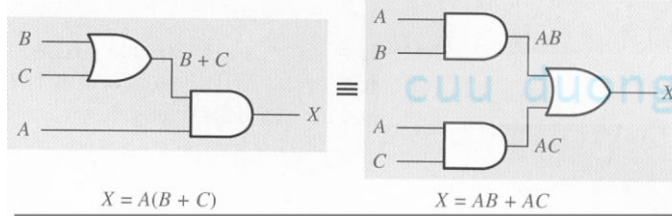

dce 2016

dce 2016 Rules of Boolean Algebra

1. $A + 0 = A$	7. $A \cdot A = A$
2. $A + 1 = 1$	8. $A \cdot \bar{A} = 0$
3. $A \cdot 0 = 0$	9. $\bar{\bar{A}} = A$
4. $A \cdot 1 = A$	10. $A + AB = A$
5. $A + A = A$	11. $A + \bar{A}B = A + B$
6. $A + \bar{A} = 1$	12. $(A + B)(A + C) = A + BC$

dce 2016

dce 2016 Rules of Boolean Algebra

Rule 1 $X = A + 0 = A$

Rule 2 $X = A + 1 = 1$

Rule 3 $X = A \cdot 0 = 0$

Rule 4 $X = A \cdot 1 = A$

OR Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

AND Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

dce 2016 Rules of Boolean Algebra

Rule 5 $X = A + A = A$

Rule 6 $X = A + \bar{A} = 1$

Rule 7 $X = A \cdot A = A$

Rule 8 $X = A \cdot \bar{A} = 0$

OR Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

AND Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

dce 2016 Rules of Boolean Algebra

Rule 9 $\bar{\bar{A}} = A$

Rule 10: $A + AB = A$

AND Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

OR Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

equal

dce 2016 Rules of Boolean Algebra

Rule 11: $A + A'B = A + B$

Rule 12: $(A + B)(A + C) = A + BC$

equal

dce 2016 Examples

- Simplify the expression

$$y = A\bar{B}D + A\bar{B}\bar{D}$$

$$y = A\bar{B}$$

$$z = (\bar{A} + B)(A + B)$$

$$z = B$$

$$x = ACD + \bar{A}BCD$$

$$x = ACD + BCD$$

$$y = A\bar{C} + AB\bar{C}$$

$$y = A\bar{C}$$

33

dce 2016 DeMorgan's Theorems

- Theorem 1: When the OR sum of two variables is inverted, it is equivalent to inverting each variable individually and ANDing them.

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

- Theorem 2: When the AND product of two variables is inverted, it is equivalent to inverting each variable individually and ORing them.

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

34

dce 2016 DeMorgan's Theorems

- A NOR gate is equivalent to an AND gate with inverted inputs.
- A NAND gate is equivalent to an OR gate with inverted inputs.

For N variables, DeMorgan's theorem is expressed as:





$$\overline{ABC \dots N} = \bar{A} + \bar{B} + \bar{C} + \dots + \bar{N} \quad \text{and} \quad \overline{\bar{A} + \bar{B} + \bar{C} + \dots + \bar{N}} = \bar{A} \bar{B} \bar{C} \dots \bar{N}$$

Applying DeMorgan's theorem to the expression $\overline{ABC + DEF}$ we get:

$$\begin{aligned} \overline{ABC + DEF} &= (\overline{ABC}) (\overline{DEF}) \\ &= (\bar{A} + \bar{B} + \bar{C}) (\bar{D} + \bar{E} + \bar{F}) \end{aligned}$$

35

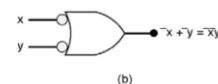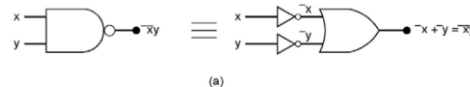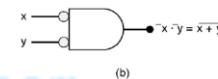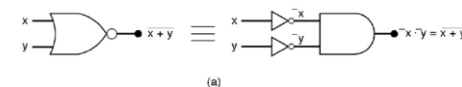
dce 2016 Implications of DeMorgan's Theorems



36

Implications of DeMorgan's Theorems

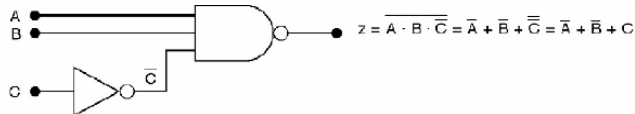- Determine the output expression for the below circuit and simplify it using DeMorgan's Theorem



- Use DeMorgan's theorems to convert below expression to an expression containing only single-variable inversions

$$y = \overline{A + \overline{B} + \overline{CD}}$$

$$y = \overline{A} \overline{B} (C + \overline{D})$$

Example of DeMorgan's Theorems

$$F = \overline{XY} + \overline{P.Q}$$

$$F = \overline{X} + \overline{Y} + \overline{P} + \overline{Q}$$

- Simplify the expression
- $$z = (\overline{A} + C)(B + \overline{D})$$
- to one having only single variables inverted.

$$z = A\overline{C} + \overline{B}D$$

Examples

- Simplify the expressions

$$- z = (A' + B)(A+B)$$

- De Morgan's

$$- z = ((a'+c) \cdot (b+d'))'$$

Examples

- Simplify the expressions

$$\begin{aligned} - z &= (A' + B)(A+B) \\ &= A'A + A'B + AB + BB = 0 + (A'+A)B + B = B \end{aligned}$$

- De Morgan's

$$\begin{aligned} - z &= ((a'+c) \cdot (b+d'))' \\ &= (a'+c)' + (b+d')' = ac' + b'd \end{aligned}$$

Exercises


- Simplify the expressions
 - a) $x = (M + N)(\bar{M} + P)(\bar{N} + \bar{P})$
 - b) $z = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{B}\bar{C}D$

De Morgan's


- | | | |
|-----------------------------------|--|---|
| (a) $\overline{A\bar{B}\bar{C}}$ | (d) $\overline{A + B}$ | (g) $\overline{A(B + \bar{C})D}$ |
| (b) $\overline{A + \bar{B}C}$ | (e) $\overline{\bar{A}B}$ | (h) $\overline{(M + \bar{N})(\bar{M} + N)}$ |
| (c) $\overline{A\bar{B}C\bar{D}}$ | (f) $\overline{\bar{A} + \bar{C} + \bar{D}}$ | (i) $\overline{\bar{A}BCD}$ |

Universality of NAND and NOR Gates

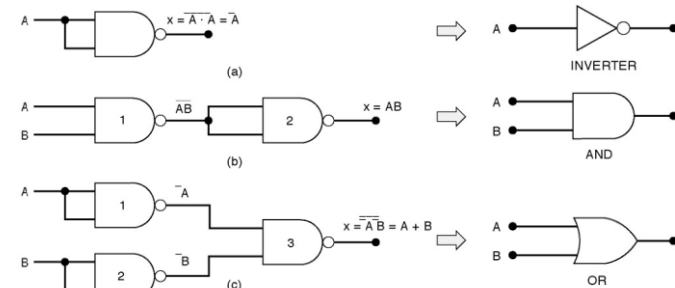- NAND or NOR gates can be used to create the three basic logic expressions (OR, AND, and INVERT)



Universality of NAND and NOR Gates

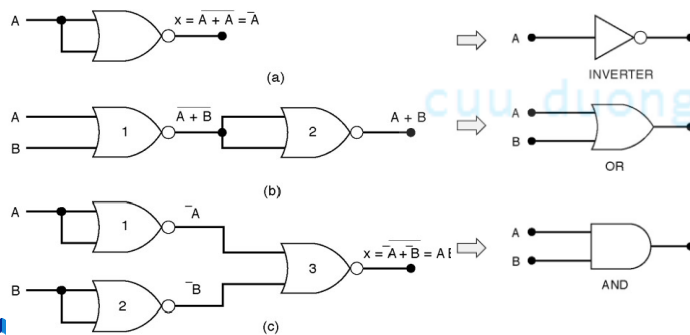

Alternate Logic-Gate Representations

- To convert a standard symbol to an alternate:
 - Invert each input and output (add an inversion bubble where there are none on the standard symbol, and remove bubbles where they exist on the standard symbol).
 - Change a standard OR gate to an AND gate, or an AND gate to an OR gate.

dce 2016 Alternate Logic-Gate Representations

- Standard and alternate symbols for various logic gates and inverter

AND: $A \cdot B$ $\equiv$ $\overline{\overline{A \cdot B}} = \overline{A + B}$

OR: $A + B$ $\equiv$ $\overline{\overline{A + B}} = \overline{A \cdot B}$

NAND: $\overline{A \cdot B}$ $\equiv$ $\overline{\overline{\overline{A \cdot B}}} = \overline{A + B}$

NOR: $\overline{A + B}$ $\equiv$ $\overline{\overline{\overline{A + B}}} = \overline{A \cdot B}$

INV: $\overline{A}$ $\equiv$ $\overline{\overline{A}}$

CUU DƯƠNG THÂN CÔNG . COM

45

dce 2016 Alternate Logic-Gate Representations

- The equivalence can be applied to gates with any number of inputs.
- No standard symbols have bubbles on their inputs. All of the alternate symbols do.
- The standard and alternate symbols represent the same physical circuitry.

CUU DƯƠNG THÂN CÔNG . COM

46

dce 2016 Alternate Logic-Gate Representations

- Active high – an input or output has no inversion bubble.
- Active low – an input or output has an inversion bubble.
- An AND gate will produce an active output when all inputs are in their active states.
- An OR gate will produce an active output when any input is in an active state.

CUU DƯƠNG THÂN CÔNG . COM

47

dce 2016 Alternate Logic-Gate Representations

- Interpretation of the two NAND gate symbols.

(a) Output goes LOW only when all inputs are HIGH. LOW state is the active state.

(b) Output is HIGH when any input is LOW. HIGH state is the active state.

CUU DƯƠNG THÂN CÔNG . COM

48

dce 2016 Alternate Logic-Gate Representations

- Interpretation of the two OR gate symbols.

(a)

Output goes HIGH when any input is HIGH.

(b)

Output goes LOW only when all inputs are LOW.

49

dce 2016 Which Gate Representation to Use

- Using alternate and standard logic gate symbols together can make circuit operation clearer.
- When possible choose gate symbols so that bubble outputs are connected to bubble input and nonbubble outputs are connected to nonbubble inputs.

50

dce 2016 Which Gate Representation to Use

- When a logic signal is in the active state (high or low) it is said to be **asserted**.
- When a logic signal is in the inactive state (high or low) it is said to be **unasserted**.
- A bar over a signal means asserted (active) low.
- The absence of a bar over a signal means asserted (active) high.

51

dce 2016 Which Gate Representation to Use

(a) Original circuit using standard NAND symbols; (b) equivalent representation where output Z is active-HIGH; (c) equivalent representation where output Z is active-LOW; (d) truth table.

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

(d)

52

dce 2016 Example

Alarm is activated when Z goes high. Modify the circuit so that it represents the circuit operation more effectively.

53

dce 2016 Example

Z activates another circuit when it goes low. Convert Z to Active-Low

54

dce 2016 Methods of describing logic circuits

Boolean expression
 $\text{warning_light} = \text{driver_present} \cdot \text{buckled_up} \cdot \text{ignition_on}$
 (a)

Schematic diagram

 (b)

Truth table

driver_present	buckled_up	ignition_on	warning_light
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 (c)

Timing diagram

 (d)

(a) Boolean expression;
 (b) schematic diagram;
 (c) truth table;
 (d) timing diagram.

55

dce 2016 IEEE/ANSI Standard Logic Symbols

- Rectangular symbols represent logic gates and circuits.
- Dependency notation inside symbols show how output depends on inputs.
- A small triangle replaces the inversion bubble.

(a) (b)

56

- The three basic logic functions are AND, OR, and NOT.
- Logic functions allow us to represent a decision process.
 - If it is raining OR it looks like rain I will take an umbrella.
 - If I get paid AND I go to the bank I will have money to spend.



- Boolean Algebra: a mathematical tool used in the analysis and design of digital circuits
- OR, AND, NOT: basic Boolean operations
- OR: HIGH output when any input is HIGH
- AND: HIGH output only when all inputs are HIGH
- NOT: output is the opposite logic level as the input
- NOR: OR with its output connected to an INVERTER
- NAND: AND with its output connected to an INVERTER
- Boolean theorems and rules: to simplify the expression of a logic circuit and can lead to a simpler way of implementing the circuit
- NAND, NOR: can be used to implement any of the basic Boolean operations



cuu duong than cong . com

cuu duong than cong . com