

Chapter 6: System Realization Using Operational Amplifiers


cuu duong than cong . com

1. Basic Circuits of Operational Amplifiers ◀
2. First order systems
3. Second order systems

Basic Circuits of Operational Amplifiers:


- Inverting amplifier:

$$H(s) = -\frac{R_f}{R}$$

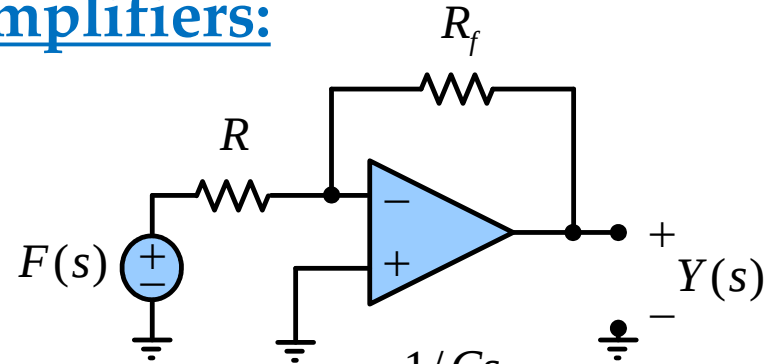


- Inverting integrator:

$$H(s) = -\frac{1}{RCs}$$

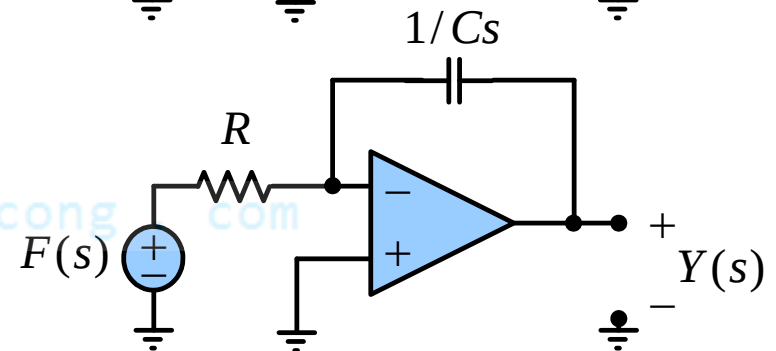

- Summing amplifier:

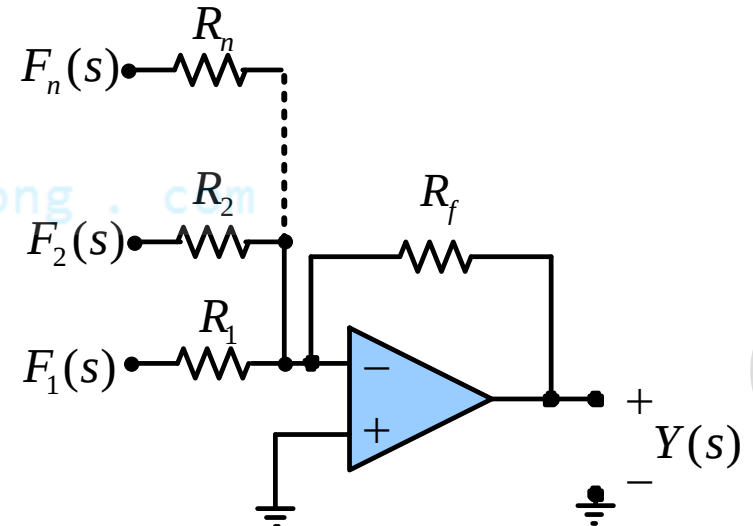
$$Y(s) = -R_f \left[\frac{F_1(s)}{R_1} + \frac{F_2(s)}{R_2} + \dots + \frac{F_n(s)}{R_n} \right]$$




Basic Circuits of Operational Amplifiers:

- Example 6.01: Using op-amp circuits, realize the canonical form of the transfer function:

$$H(s) = \frac{2s + 5}{s^2 + 4s + 10}$$

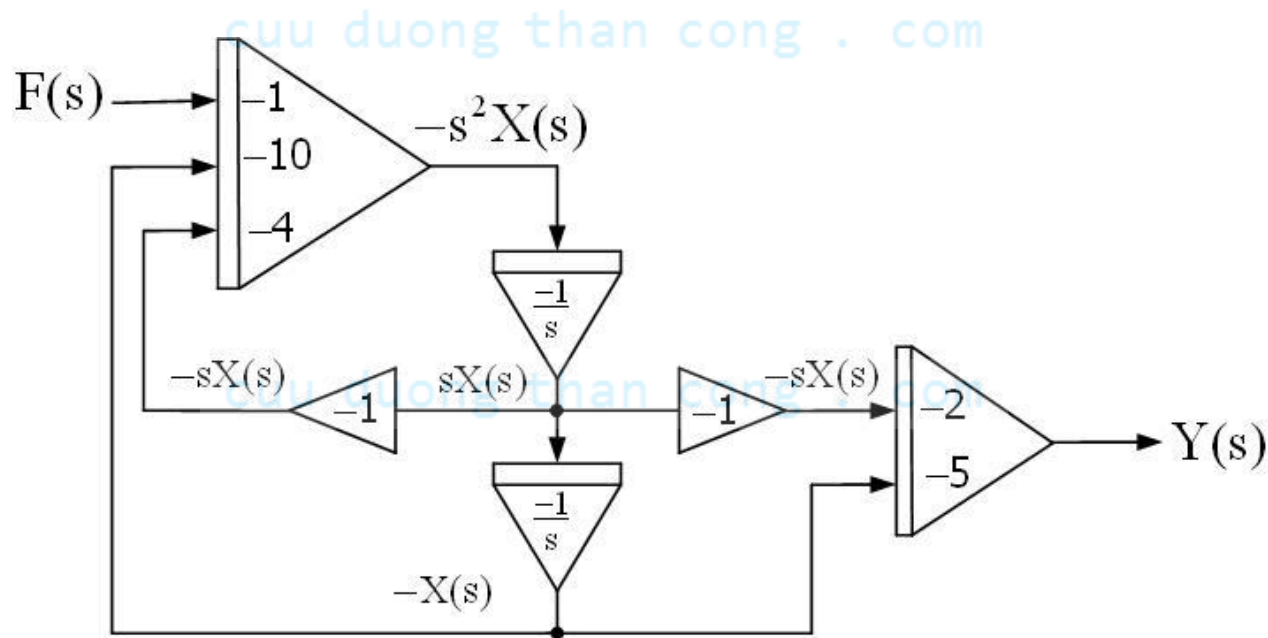

Basic Circuits of Operational Amplifiers:

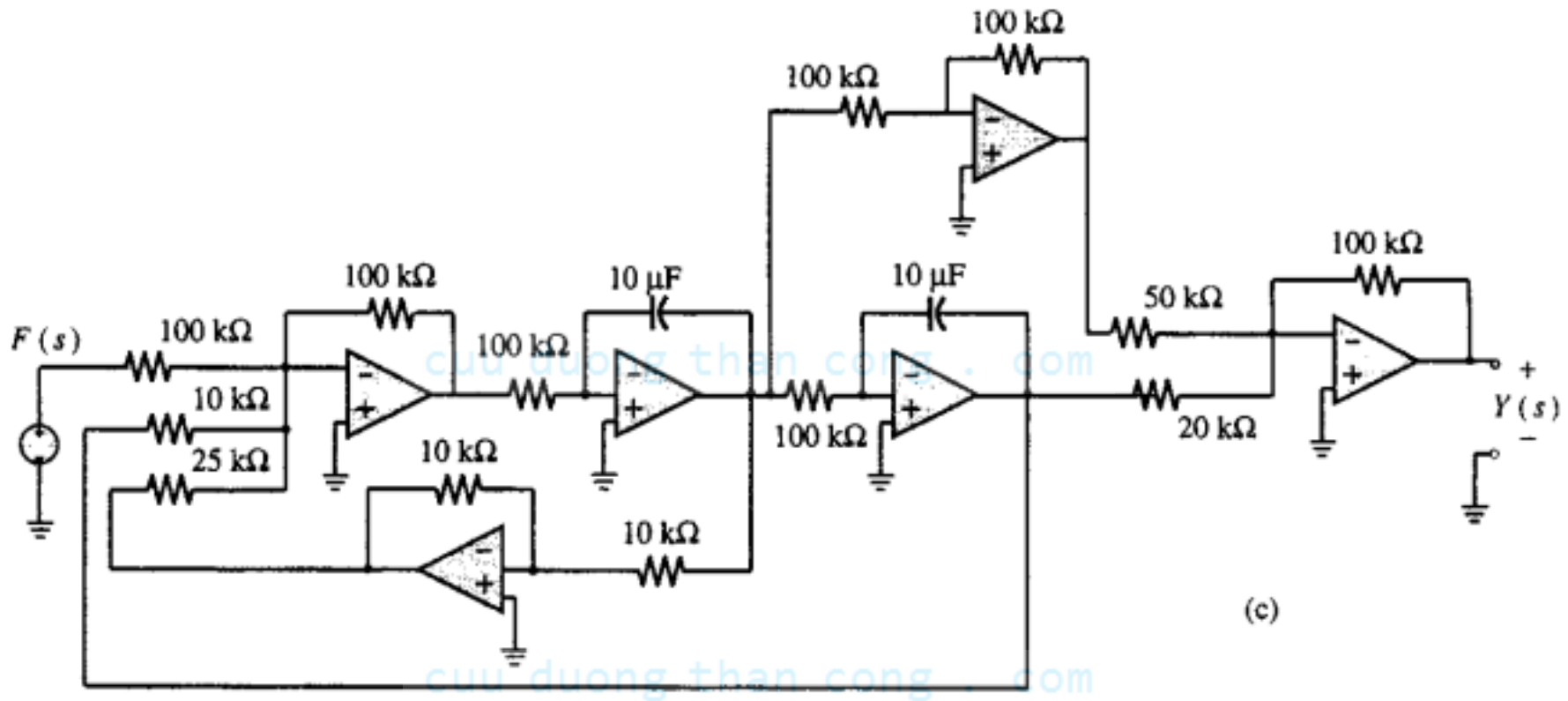

Chapter 6: System Realization Using Operational Amplifiers

cuu duong than cong . com


1. Basic Circuits of Operational Amplifiers
2. First order systems
3. Second order systems

First order systems:

- Type 1

$$H(s) = \frac{ka}{s+a}$$

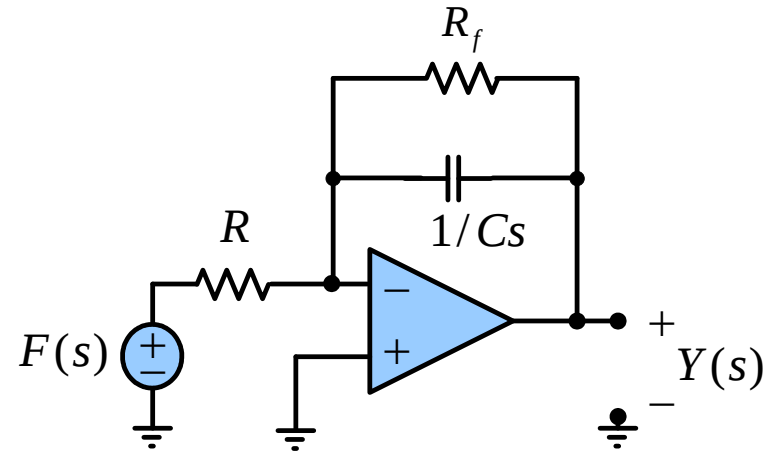
$$k = -\frac{R_f}{R}; \quad a = \frac{1}{R_f C}$$



- Type 2

$$H(s) = \frac{k(s+a)}{s+b}$$


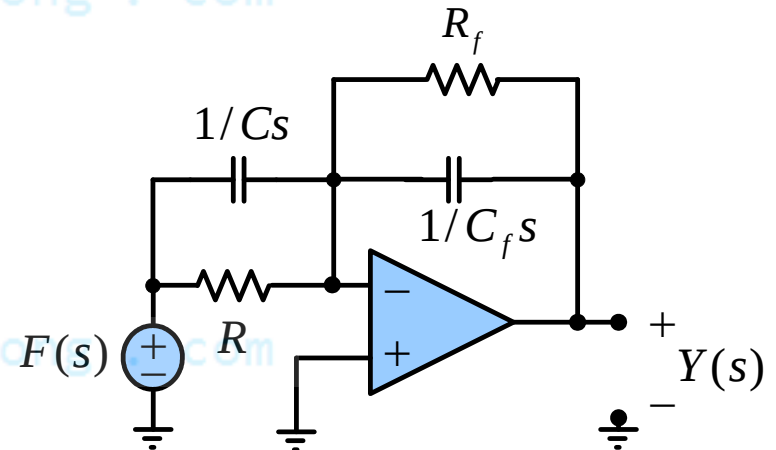
$$k = -\frac{C}{C_f}; \quad a = \frac{1}{R_f C_f}; \quad b = \frac{1}{RC}$$



First order systems:

• Example 6.02

$$H(s) = \frac{s+2}{s+5}$$

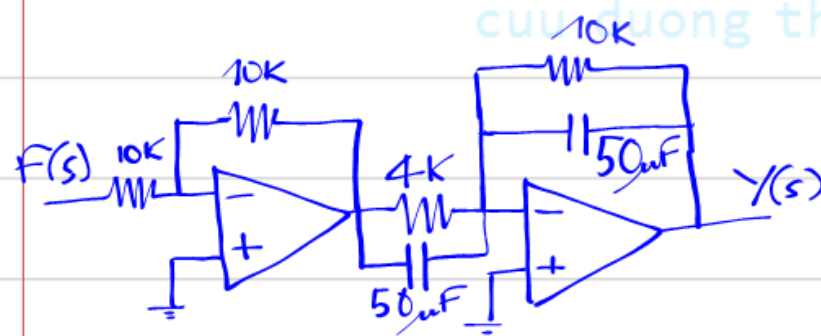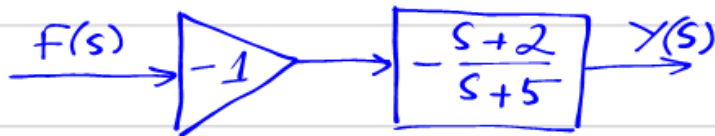

Inverting amplifier:

$$H(s) = -1 = -\frac{R_f}{R}$$

$$\Rightarrow R_f = R = 10K$$

First order system

$$a = 2 = \frac{1}{R_f \cdot C_f}$$



$$R_f = 10K \Rightarrow C_f = 50\mu F$$

$$k = -1 = -\frac{C}{C_f} \Rightarrow C = C_f = 50\mu F ; b = 5 = \frac{1}{RC} \Rightarrow R = 4K$$

First order systems:

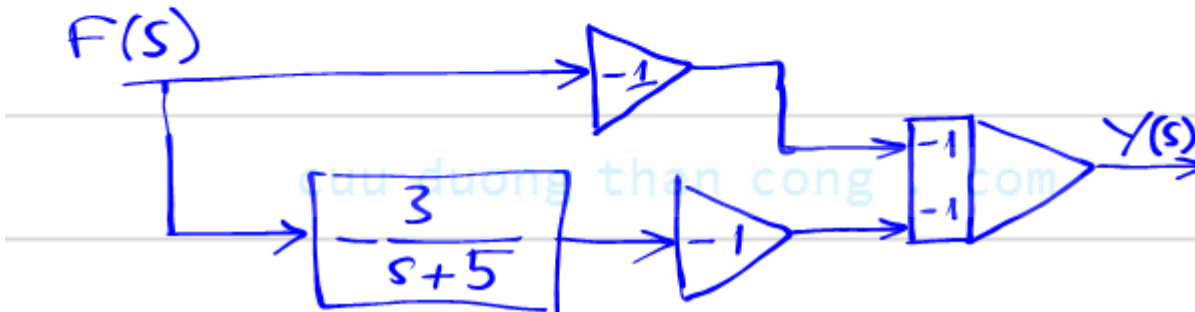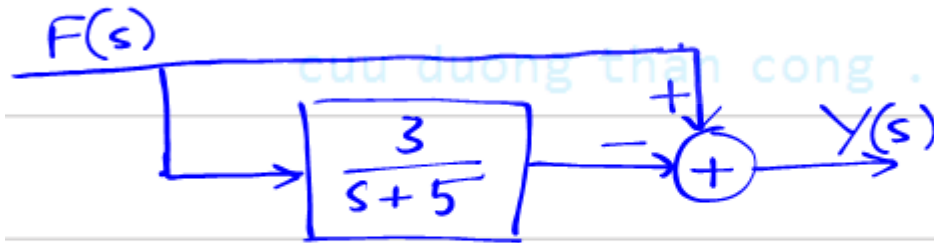
- *Example 6.02 (cont)*

$$H(s) = \frac{s+2}{s+5} = 1 - \frac{3}{s+5}$$



First order systems:

- Example 6.02 (cont)

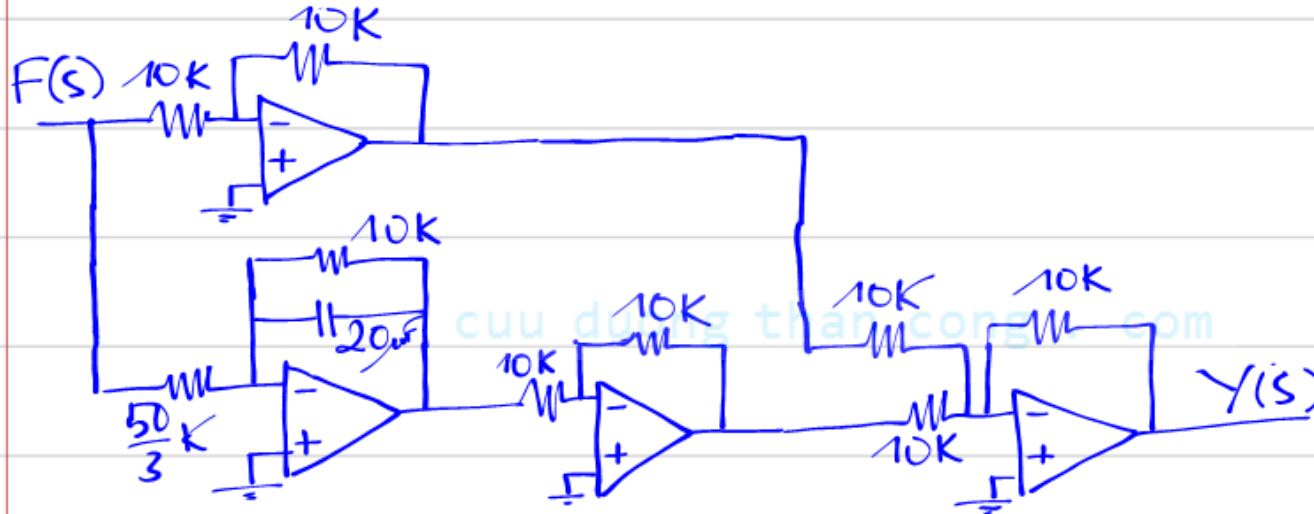

First order system: $a = \frac{1}{R_f \cdot C} = 5$, $R_f = 10K \Rightarrow C = 20\mu F$

$$K = -\frac{3}{5} = -\frac{R_f}{R} \Rightarrow R = \frac{50}{3} K$$

Chapter 6: System Realization Using Operational Amplifiers

cuu duong than cong . com


1. Basic Circuits of Operational Amplifiers
2. First order systems
3. Second order systems

Second order systems:

Lowpass filter

- Type 1:

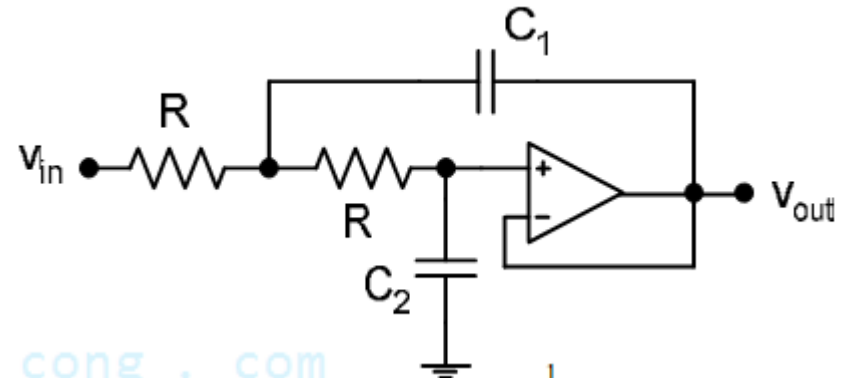
$$H(s) = \frac{1}{s^2 + \frac{2}{RC_1}s + \frac{1}{R^2C_1C_2}}$$



- Type 2:

$$H(s) = \frac{-ka_0}{s^2 + a_1s + a_0}; a_0 = \frac{1}{R_2R_3C_1C_2}$$

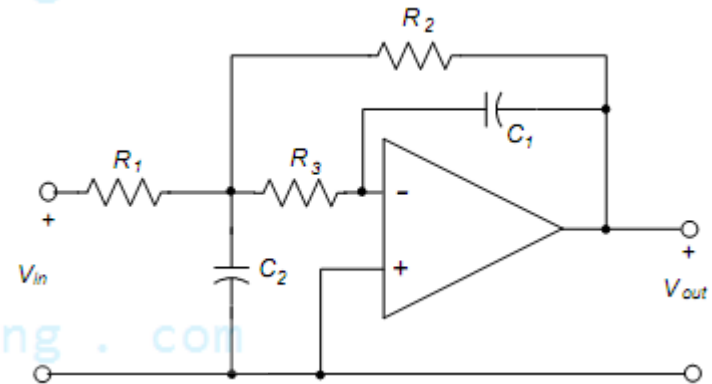
$$k = \frac{R_2}{R_1}; a_1 = \frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$



Second order systems:

Bandpass filter
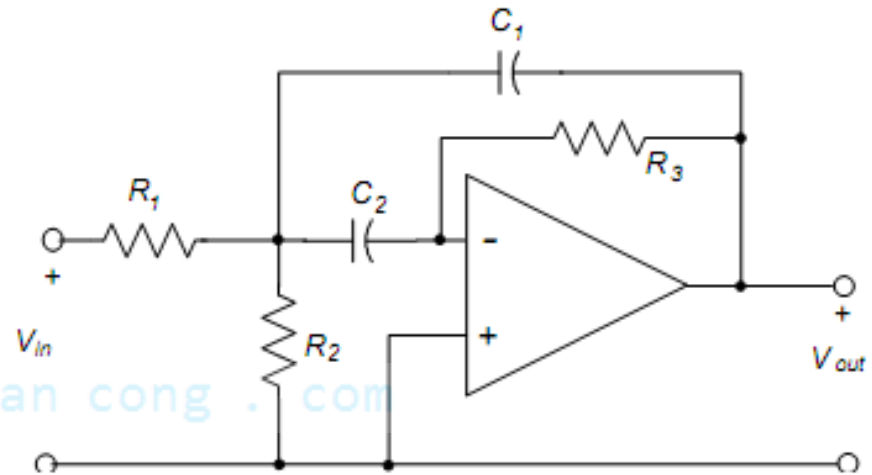
$$H(s) = \frac{-ka_1s}{s^2 + a_1s + a_0}$$



$$a_0 = \frac{1}{R_3 C_1 C_2} \left(\frac{1}{R_1} + \frac{1}{R_2} \right); \quad a_1 = \frac{C_1 + C_2}{R_3 C_1 C_2}$$


$$k = \frac{R_3 C_2}{R_1 (C_1 + C_2)};$$

Second order systems:

Highpass filter

- Type 1
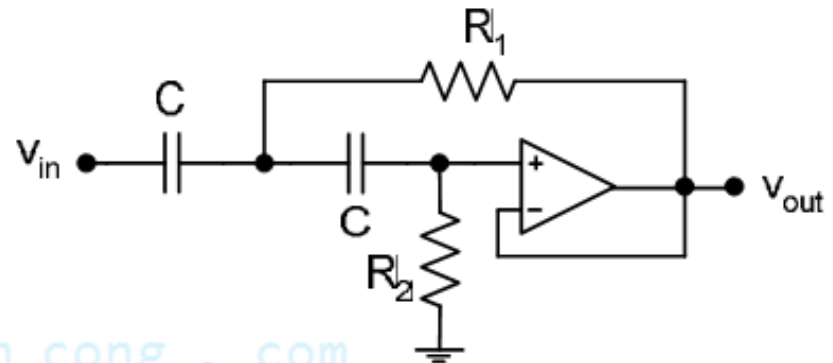
$$H(s) = \frac{s^2}{s^2 + \frac{2}{R_2 C} s + \frac{1}{R_1 R_2 C^2}}$$



- Type 2

$$H(s) = \frac{-ks^2}{s^2 + a_1 s + a_0}; a_0 = \frac{1}{R_1 R_2 C_2 C_3}$$

$$k = \frac{C_1}{C_2}; a_1 = \frac{C_1 + C_2 + C_3}{R_2 C_2 C_3}$$

